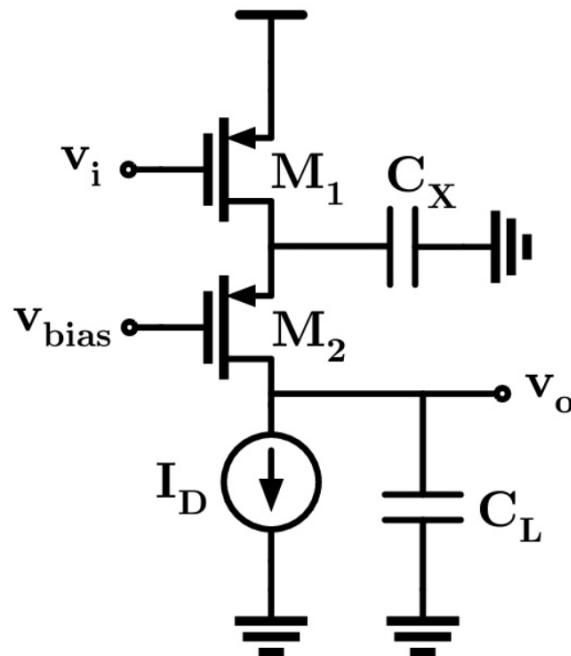


Problem 1 - Cascode Frequency Response


In this problem you will analyze the frequency response of the cascode amplifier below. Consider only the C_{gd} and C_{gs} of each transistor. Assume all transistors have the same small signal parameters and parasitic capacitances. Express your answers symbolically. You may assume that C_L , C_{gd} , and C_{gs} are all on the same order of magnitude, and $g_m r_o \gg 1$.



- (a) Compute the DC gain $A_v = \frac{v_o}{v_i}$ and DC output impedance R_{out} .

We will ignore the body effect
for this part.


Small-Signal Model

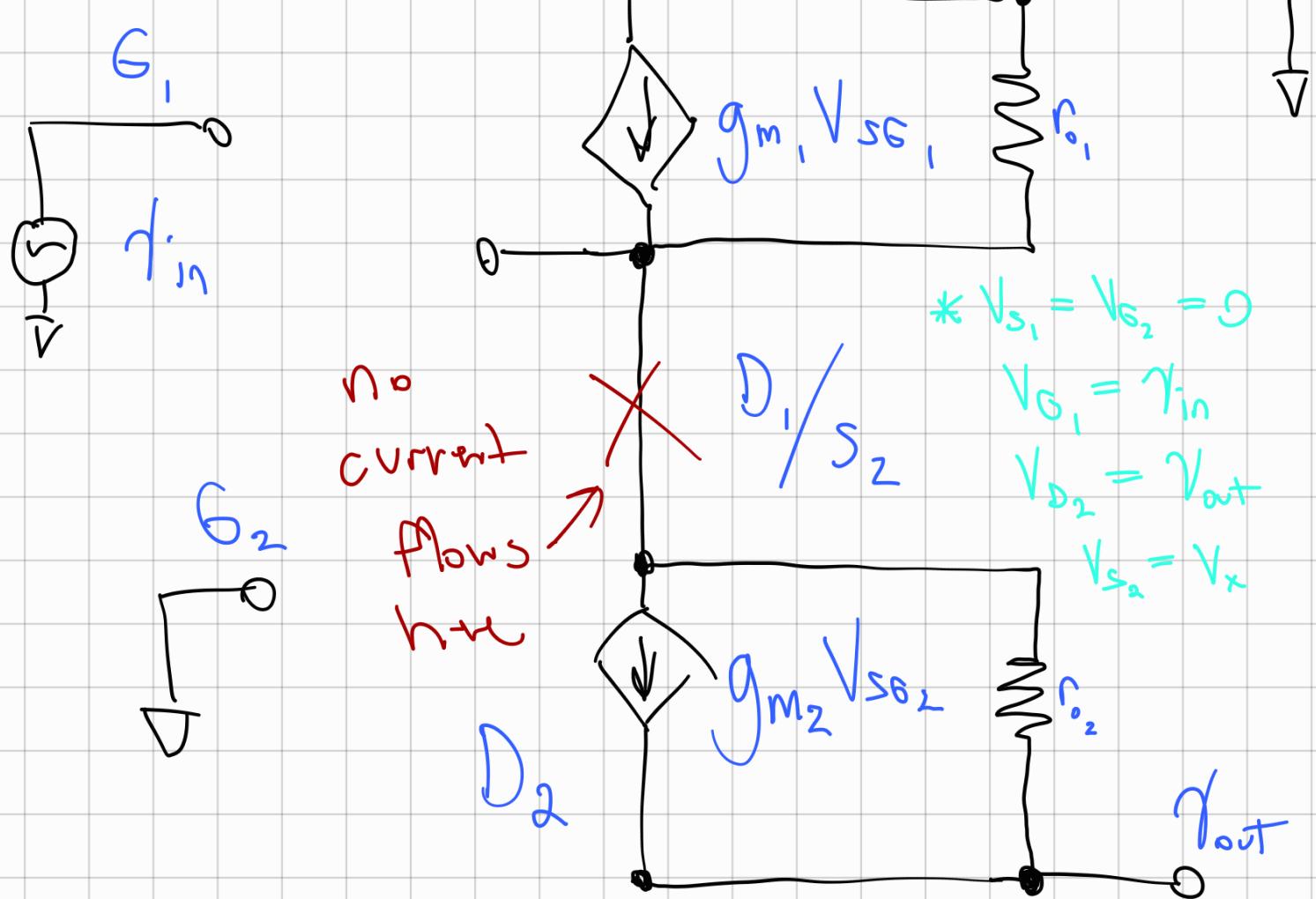

$$\Rightarrow \frac{V_{out}}{r_{o_1}} + g_m V_{in} = 0$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = -g_m r_o$$

Applying a Test Source to the Output

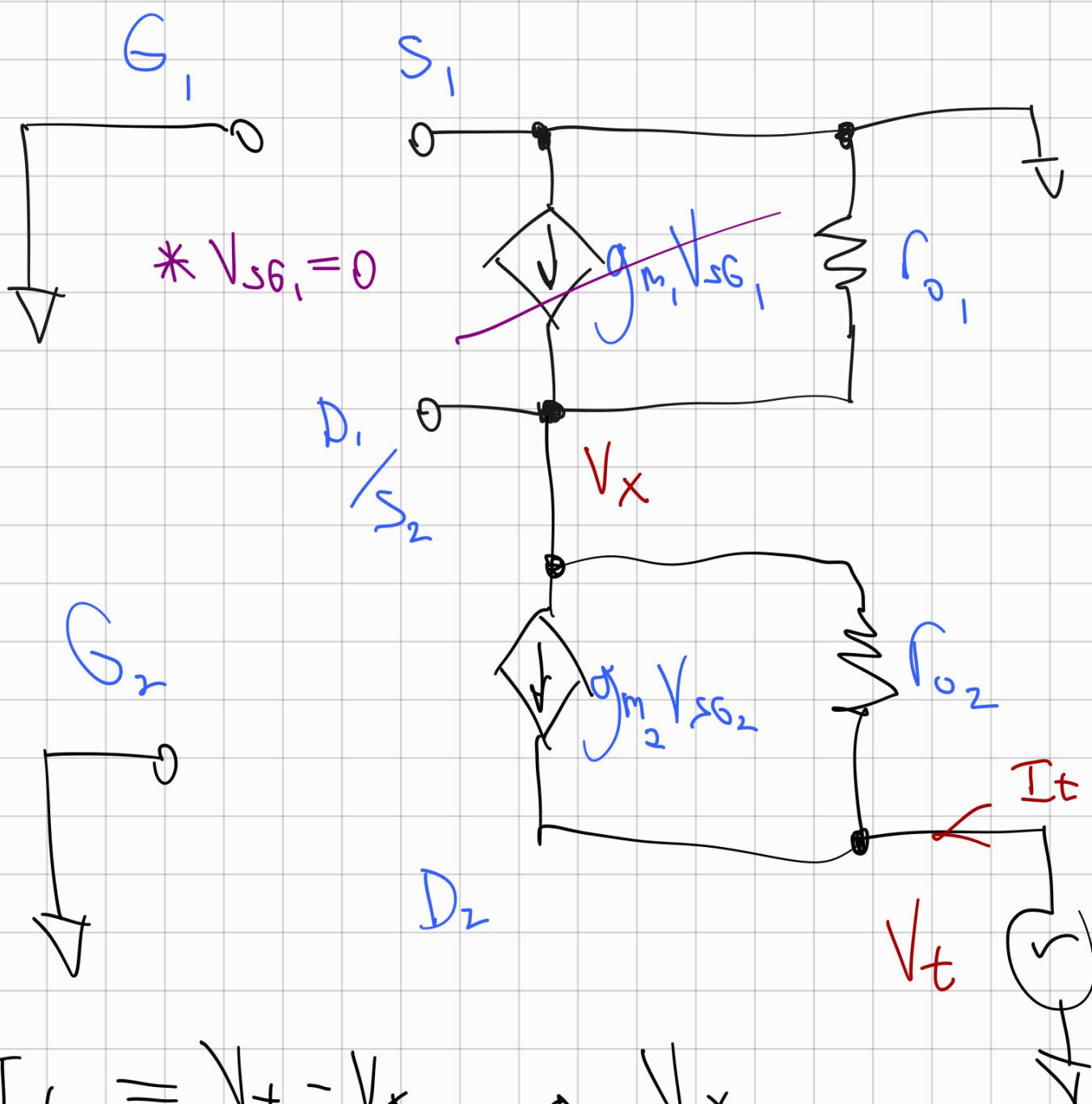

$$I_t = \frac{V_t - V_x}{r_{o2}} - g_{m2} V_x$$

$$= \frac{1}{r_{o2}} V_t - \left(g_{m2} + \frac{1}{r_{o2}} \right) V_x \quad (1)$$

$$\boxed{I_t = \frac{V_x}{r_{o1}} \cdot r_{o1} \left(g_{m2} + \frac{1}{r_{o2}} \right)} \quad (2)$$

⇒ Add Eq. 1 + Eq. 2

$$\frac{1}{r_{o_2}} I_t = \left(\frac{1}{r_{o_2}} \right) V_t - \left(g_{m_2} + \frac{1}{r_{o_2}} \right) V_x$$

$$+ \left(r_{o_1} g_{m_2} + \frac{r_{o_1}}{r_{o_2}} \right) I_t = 0 V_t + \left(g_{m_2} + \frac{1}{r_{o_2}} \right) V_x$$


$$= \left(1 + r_{o_1} g_{m_2} + \frac{r_{o_1}}{r_{o_2}} \right) I_t = \frac{1}{r_{o_2}} V_t$$

$$V_t = \left(r_{o_2} + r_{o_1} r_{o_2} g_{m_2} + r_{o_1} \right) I_t$$


• • •


$$R_{out} = r_{o_1} + r_{o_2} \left(1 + g_{m_2} r_{o_1} \right)$$

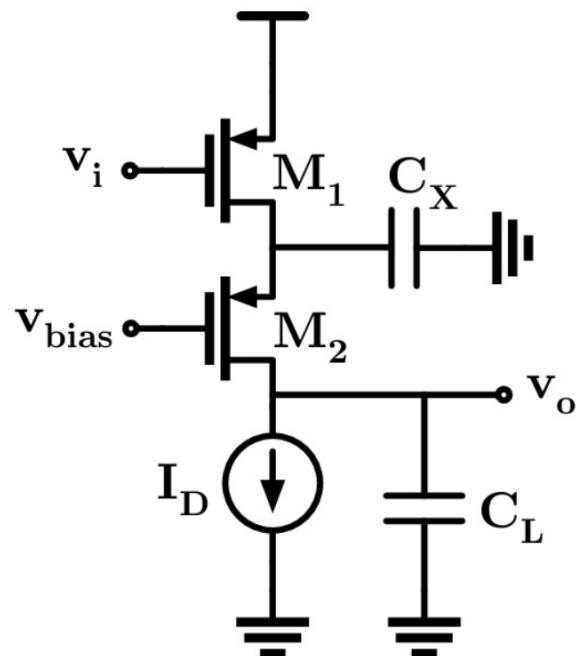In this problem you will analyze the frequency response of the cascode amplifier below. Consider only the C_{gd} and C_{gs} of each transistor. Assume all transistors have the same small signal parameters and parasitic capacitances. Express your answers symbolically. You may assume that C_L , C_{gd} , and C_{gs} are all on the same order of magnitude, and $g_m r_o \gg 1$.



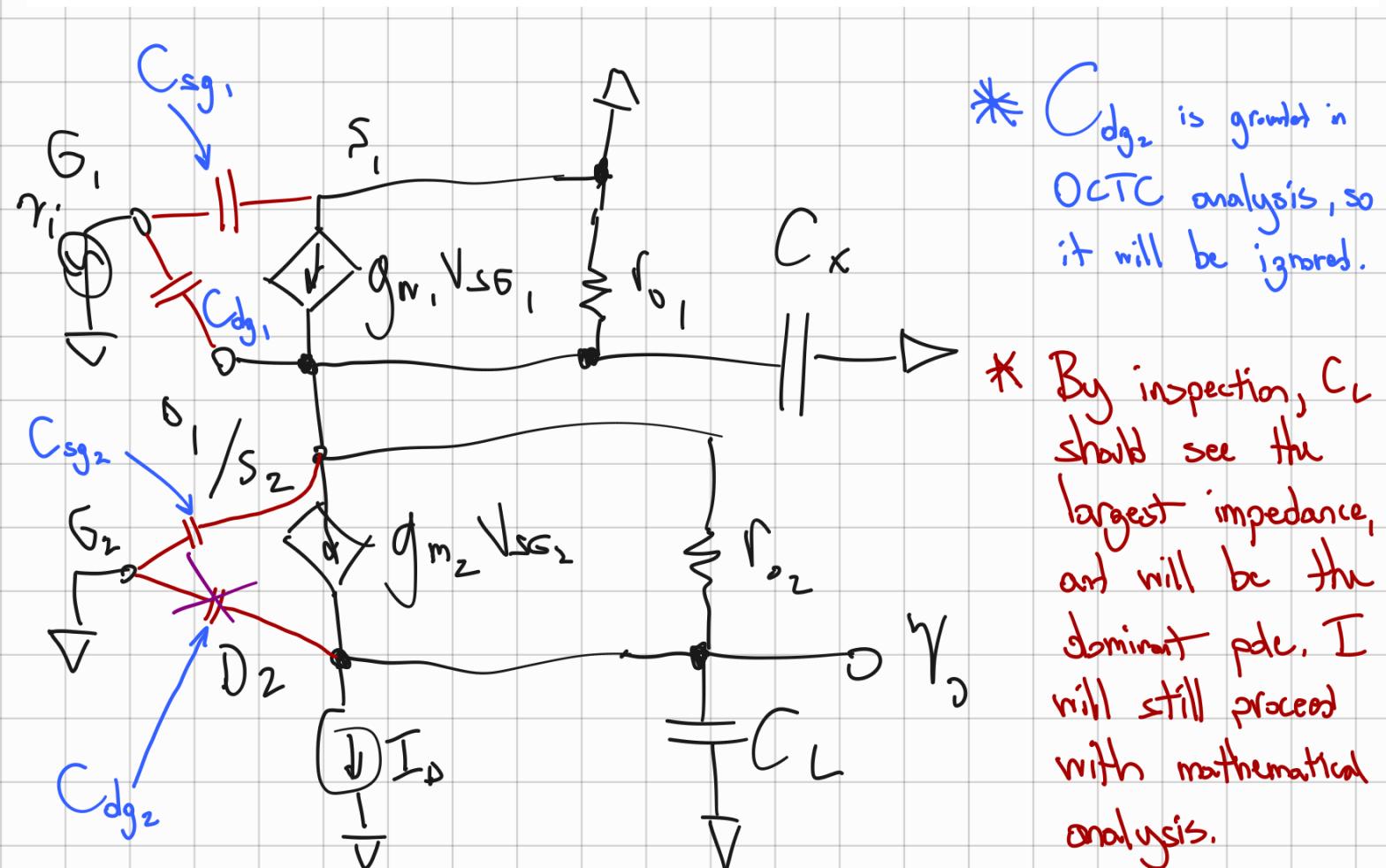- (b) Use OCTC to estimate the bandwidth of the amplifier in terms of circuit parameters. Under reasonable assumptions, which time constant would dominate the OCTC calculation?



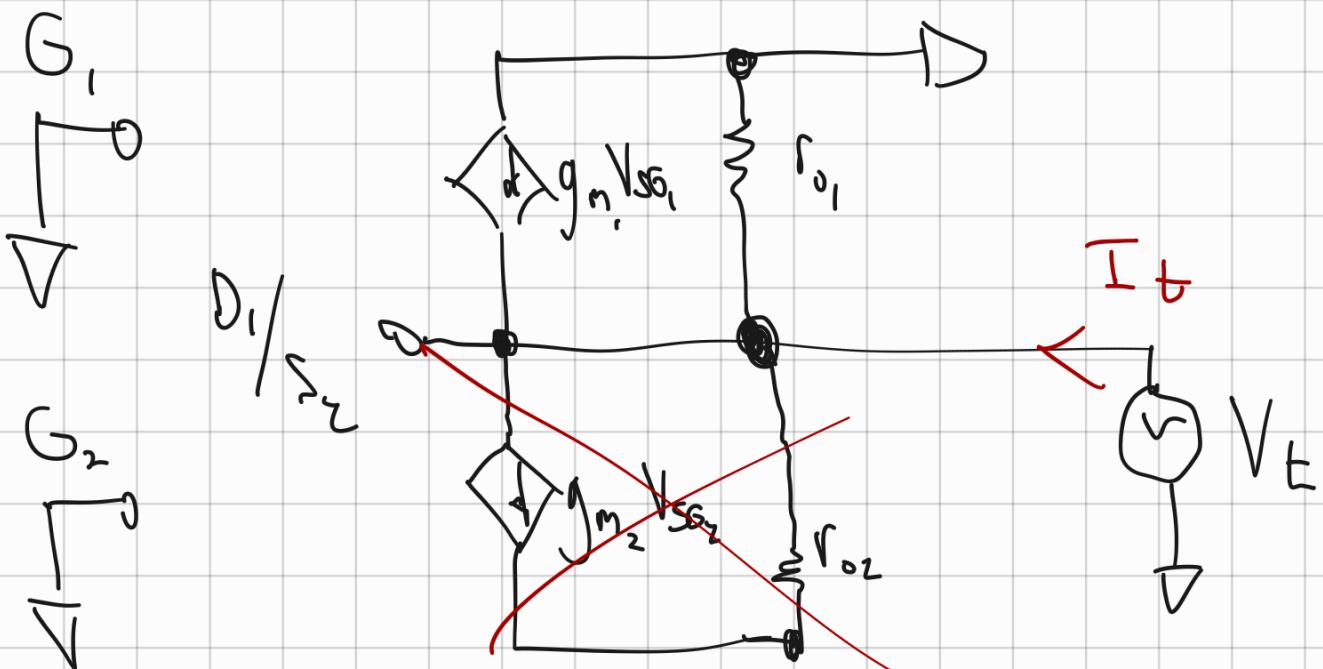


$$\underline{C_x} : I_t = \frac{\sqrt{t}}{r_{o1}} - g_{m1} \sqrt{G_1}$$

$$\Rightarrow \frac{\sqrt{t}}{I_t} = r_{o1} \quad \dots$$

$$R_{C_x} = r_{o1}$$

$C_d g_1$:

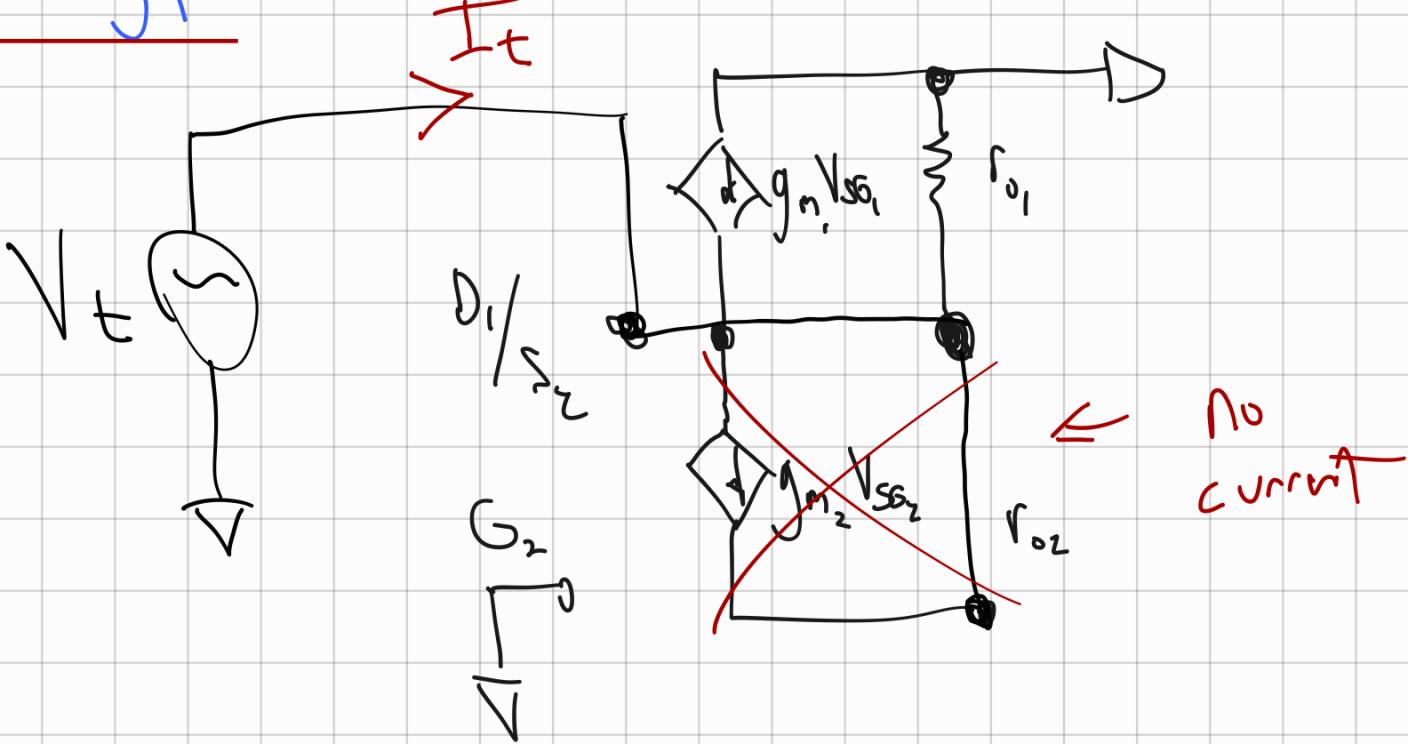

$$\Rightarrow I_t = \frac{\sqrt{t}}{r_{o_1}} - g_{m_1} \sqrt{s_{g_1}}$$


$$= \frac{\sqrt{t}}{r_{o_1}} + g_{m_1} \sqrt{t}$$

$$= \sqrt{t} \left(\frac{1}{r_{o_1}} + g_{m_1} \right)$$

$$\Rightarrow \frac{\sqrt{t}}{I_t} = \frac{r_{o_1}}{1 + g_{m_1} r_{o_1}} \underset{\text{red}}{=} \frac{\sqrt{r_{o_1}}}{r_{o_1}} \frac{1}{g_{m_1}}$$

$\bullet \bullet$
 $R_{C_{dg_1}} = \frac{1}{g_{m_1}}$

$C_L \parallel C_{dg_2}$:

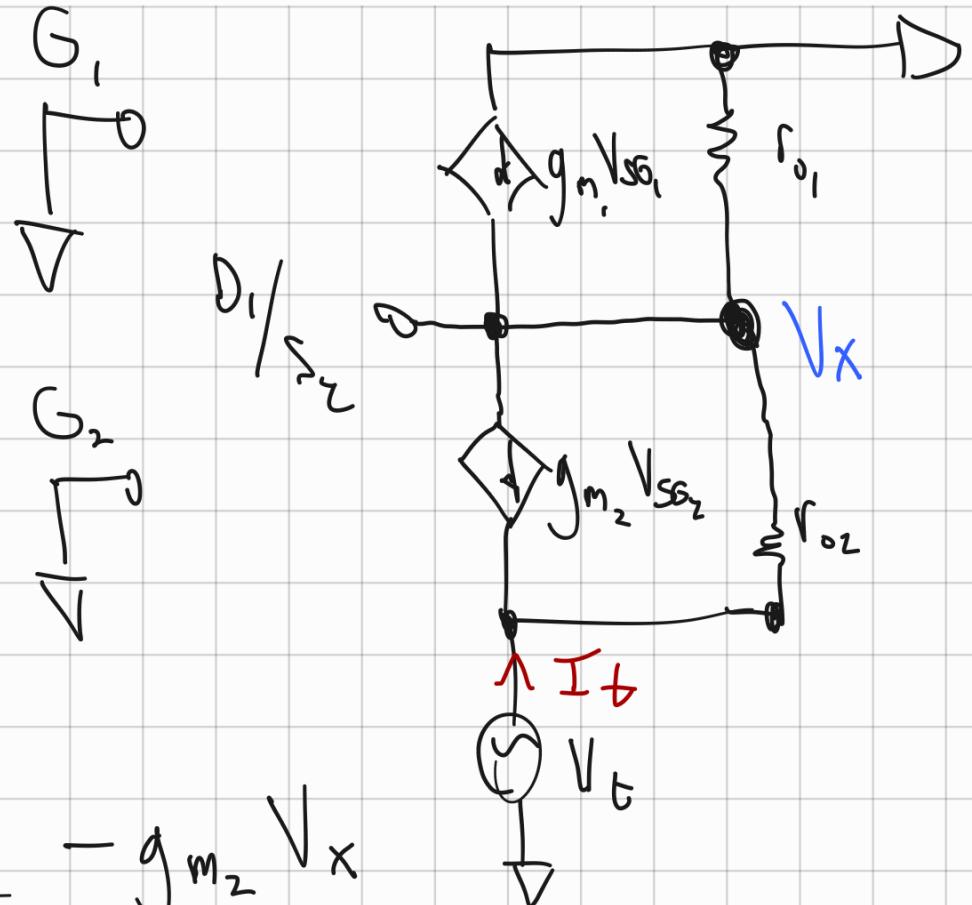

$$I_t = \frac{V_t - V_x}{r_{o2}} - g_{m2} V_x$$

$$= \frac{V_t}{r_{o2}} - V_x \left(g_{m2} + \frac{1}{r_{o2}} \right)$$

$$I_t = \frac{V_x}{r_{o1}} \Rightarrow V_x = I_t \cdot r_{o1}$$


$$\Rightarrow I_t = \frac{V_t}{r_{o2}} - I_t \left(\frac{r_{o1}}{g_{m2}} + \frac{r_{o1}}{r_{o2}} \right)$$

$$\Rightarrow I_t \left(1 + \frac{r_{o1}}{g_{m2}} + \frac{r_{o1}}{r_{o2}} \right) = \frac{V_t}{r_{o2}}$$

$$\Rightarrow I_t \left(r_{o_1} + r_{o_2} + \frac{r_{o_1}}{g_m 2} \right) = V_t$$

$$\Rightarrow R_{C_{sg_1} \parallel C_{dg_2}} = \frac{r_{o_1} + g_m 2 (r_{o_1} + r_{o_2})}{g_m 2}$$


C_{sg_1} :

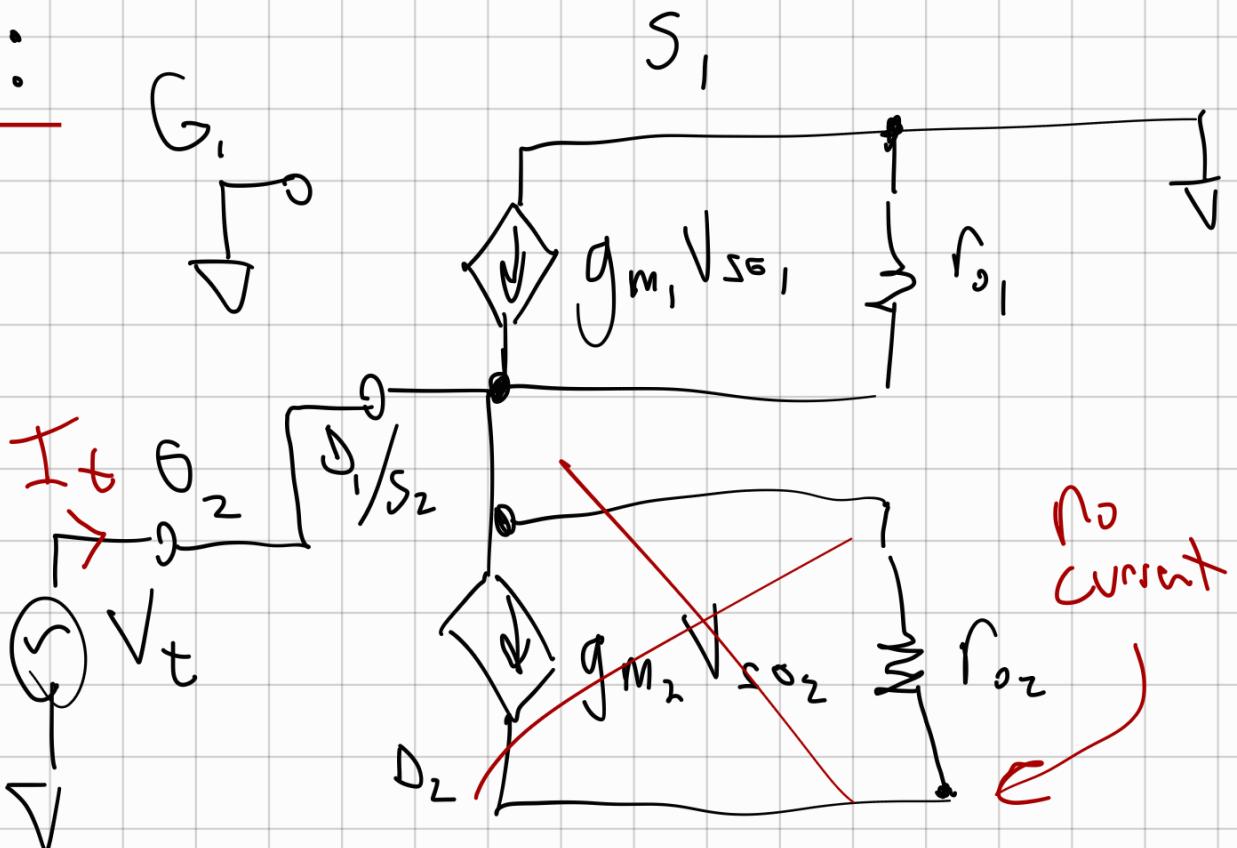

$$\Rightarrow I_t = \frac{V_t}{r_{o_1}} - g_m 1 V_{SG_1}$$

$$\therefore R_{C_{sg_1}} = r_{o_1}$$

C_{sg_2} :

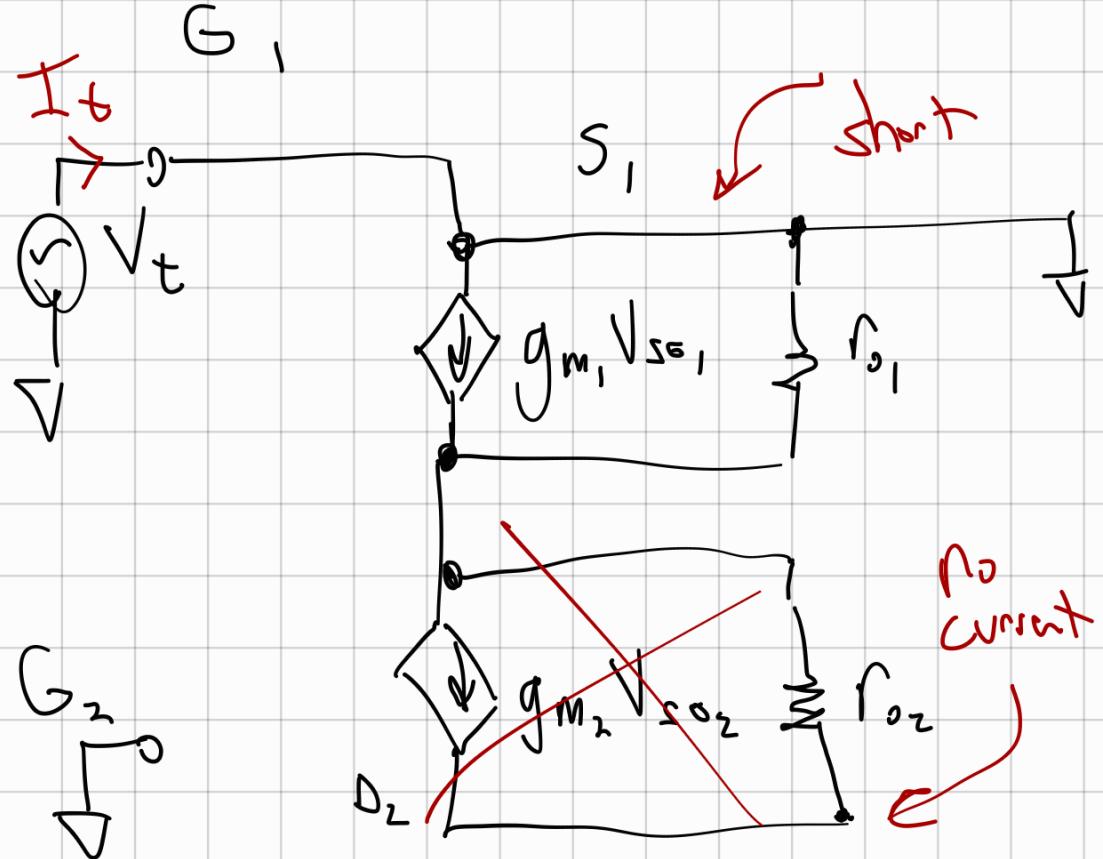

$$\Rightarrow I_t = \infty$$

* $R_{C_{sg_2}} = 0$


Overall 3dB Bandwidth

$$W_o = \frac{1}{(R_{C_{sg_1}} \cdot C_{sg_1}) + (R_{C_L} \parallel C_{dg_2} \cdot (C_L + C_{dg_2})) + (R_{C_{dg_1}} \cdot C_{dg_1})}$$

$C_L \parallel C_{dg_2}$ is the dominant pole.

$$\Rightarrow \frac{g_{m_2}}{g_{m_2}} \left(\frac{r_{o_1}}{g_{m_2}} + r_{o_1} + r_{o_2} \right) \gg r_{o_1} \\ \gg \frac{1}{g_{m_2}}$$

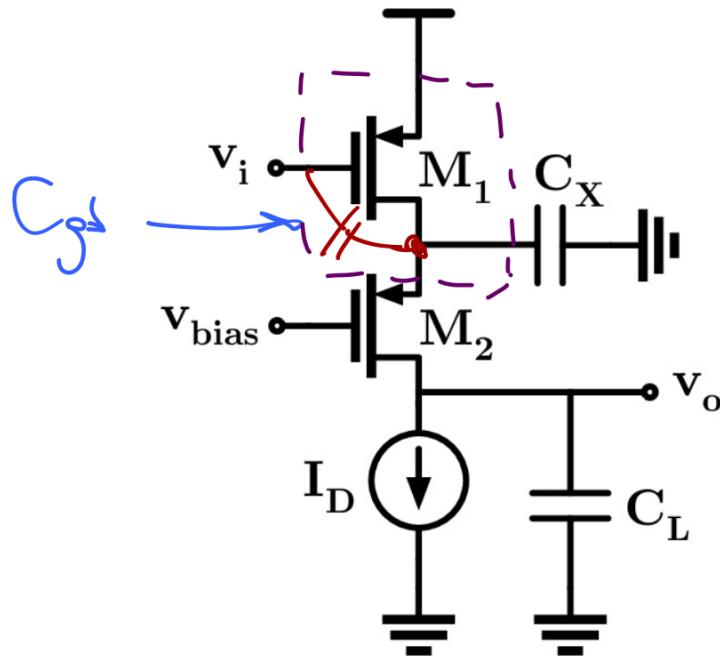
In this problem you will analyze the frequency response of the cascode amplifier below. Consider only the C_{gd} and C_{gs} of each transistor. Assume all transistors have the same small signal parameters and parasitic capacitances. Express your answers symbolically. You may assume that C_L , C_{gd} , and C_{gs} are all on the same order of magnitude, and $g_m r_o \gg 1$.




- (c) The transfer function $H(s) = v_o(s)/v_i(s)$ of this circuit has one zero. Estimate the zero frequency.

Hint: It is possible to find the zero without finding the entire $H(s)$. Calculate the equivalent G_m of the top transistor with C_{gd} included.

Two-port model

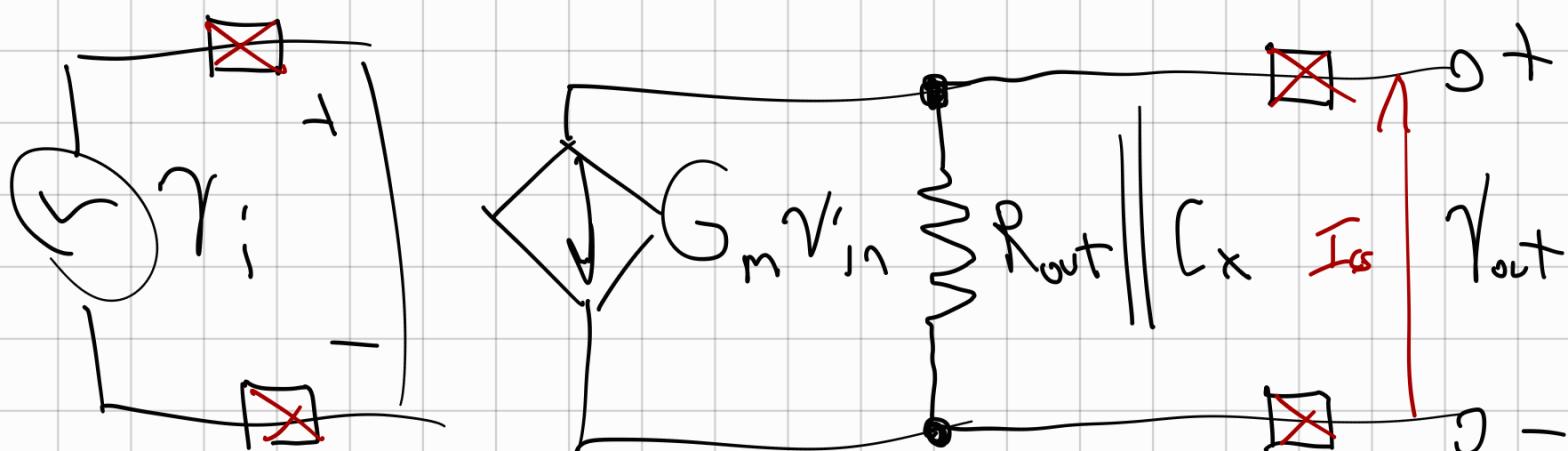

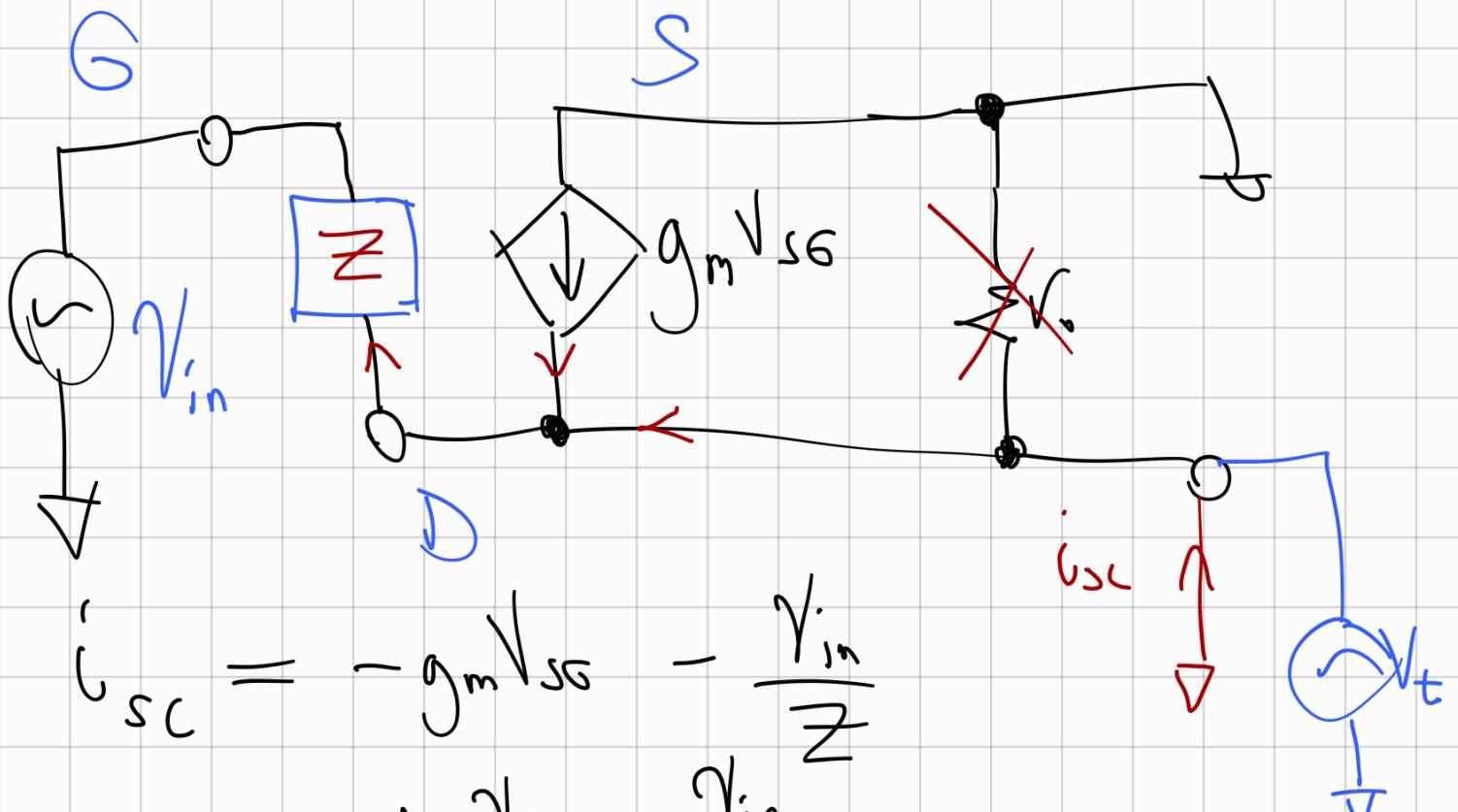

$$= V_{in} \left(g_m - s C_{gd} \right)$$

$$I_{SC} = G_m V_{in}$$

$$\Rightarrow G_m = g_m - s C_{gd}$$

$$i_t = \frac{V_t}{r_o} + \frac{V_t}{\frac{1}{Z}} = V_t \left(\frac{1}{r_o} + s C_{gd} \right)$$

$$\Rightarrow R_{out} = \frac{r_o}{1 + s C_{gd} r_o} \parallel C_x$$

$$\begin{aligned}
 &= \frac{r_o}{sC_x} \\
 &\quad + \frac{1 + s r_o C_{gd}}{sC_x} \\
 &\quad + \frac{r_o}{sC_x} \\
 &= \left(\frac{r_o}{sC_x} \right) \left(1 + \frac{s r_o C_{gd}}{sC_x} \right) + \left(\frac{s r_o C_x + 1 + s r_o C_{gd}}{sC_x} \right) \\
 &= \boxed{\frac{r_o}{1 + s r_o (C_x + C_{gd})}} \quad R_{out}
 \end{aligned}$$

$$G_m \cdot R_{out} = \frac{r_o (g_m - s C_{gd})}{1 + s r_o (C_x + C_{gd})}$$

$$H(s) = g_m r_o \left(\frac{1 - s \frac{f_o C_{gd}}{g_m r_o}}{1 + s r_o (C_x + C_{gd})} \right)$$

Zero Frequency:


$$\frac{g_m}{C_{gd}}$$

Problem 2 - Current Amplifier

Figure below shows the schematic of a current input, current output amplifier. The input DC current is set such that M_1 is at the onset of saturation ($V_{DS} = V_{GS} - V_{TH}$). You may use the square-law model for the transistors with the following parameters.

$$\lambda = 0, \gamma = 0, |V_{TH}| = 0.5V, V_{DD} = 2V$$
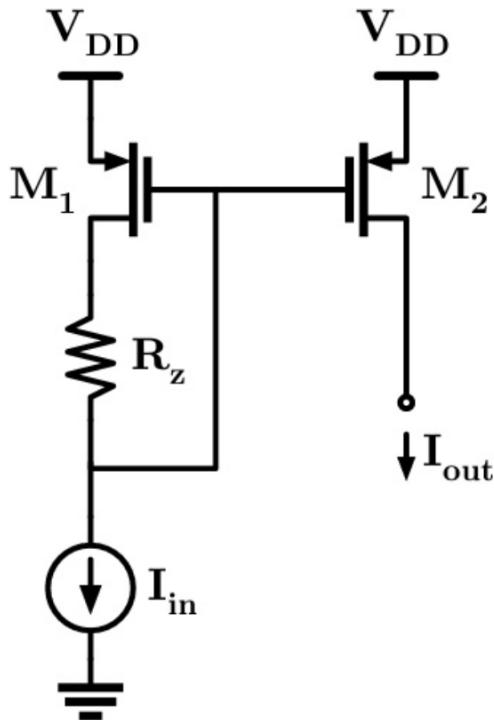
$$W_2 = A \times W_1, (\frac{W}{L})_1 = 10, k' = \mu_p C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$$



- (a) We want to pick an R_z such that $R_z = \frac{1}{g_{m1}}$. What is this R_z value? What is the DC voltage at the gate of M_1 ?

We want to relate the following two equations:

$$\frac{V_{GS}}{R_z} = I_{in} \quad \& \quad g_m = \sqrt{2 \cdot k' \cdot \frac{W}{L} \cdot I_{in}}$$

We are given that: $V_{SD} = V_{SG} - V_T$

Rearranging $\Rightarrow \cancel{V_S - V_D} = \cancel{V_S - V_D} - V_T$

$$\Rightarrow V_D = V_G + V_T$$

$$\Rightarrow \cancel{V_G + V_T} - \cancel{V_G} = \underline{\underline{I_{in}}}$$

R_Z

$$\Rightarrow \frac{V_T}{R_Z} = \underline{\underline{I_{in}}}$$

$$\Rightarrow \frac{V_T}{\frac{1}{g_m}} = \underline{\underline{I_{in}}}$$

$$\Rightarrow g_m V_T = \underline{\underline{I_{in}}}$$

$$\Rightarrow g_m = \frac{\underline{\underline{I_{in}}}}{V_T}$$

continued...

$$\Rightarrow \frac{I_{in}}{\sqrt{T}} = \sqrt{2 \cdot k' \cdot \frac{W}{L} \cdot I_{in}}$$

$$\Rightarrow \left(\frac{I_{in}}{\sqrt{T}} \right)^2 = 2k' \cdot \frac{W}{L} \cdot I_{in}$$

$$\Rightarrow I_{in}^2 = 2k' \frac{W}{L} \cdot \sqrt{T}^2 \cdot I_{in}$$

$$I_{in} = \phi = 0.5 \text{ mA}$$

$$\Rightarrow R_Z = \frac{\sqrt{T}}{I_{in}} = \frac{0.5 \text{ V}}{0.5 \text{ mA}}$$

$$\therefore R_Z = 1 \text{ k}\Omega$$

DC Voltage at Gate of M₁

$$\Rightarrow g_n = \frac{1}{R_Z} = \frac{W}{L} k' (V_{SD} - V_T)$$

$$\Rightarrow (V_{SG} - V_T) = \frac{1}{R_Z W k'}$$

$$\Rightarrow V_{SG} = \frac{1}{R_Z W k'} + V_T$$

$$= \frac{1}{1K \cdot 10 \cdot 100 \times 10^{-4} + 2,5}$$

$$= 1,5$$


$$\Rightarrow V_{SG} = V_{DD} - V_0 = 1,5$$

$$\Rightarrow V_G = V_{DD} - 1,5$$

$$\therefore \therefore V_G = 0,5 \text{ V}$$

$$\lambda = 0, \gamma = 0, |V_{TH}| = 0.5V, V_{DD} = 2V$$
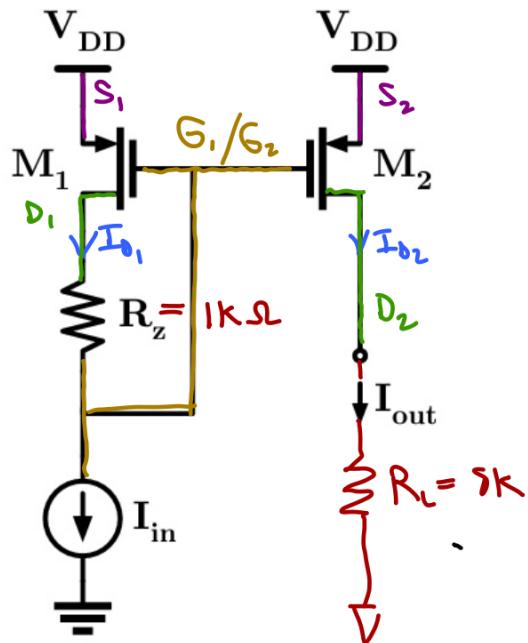
$$W_2 = A \times W_1, (\frac{W}{L})_1 = 10, k' = \mu_p C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$$




- (b) If R_z is instead chosen to be $1 \text{ k}\Omega$, and M_2 drives an $8 \text{ k}\Omega$ resistor to ground as its load, what is the maximum output current that this amplifier can supply without any devices entering triode? (You may assume the input current source itself works as long as the voltage across it is $>0 \text{ V}$)

$$I_{D2,\text{sat}} = \left(\frac{AW_1}{2L_1} \right) k' \left(V_{SG_2} - V_T \right)^2 = \frac{V_{D2}}{R_D} \quad (1)$$

$$I_{D1,\text{sat}} = \left(\frac{W}{2L} \right) k' \left(V_{SG_1} - V_T \right)^2 = \frac{V_{D1}}{R_z} \quad (2)$$

$$I_{D2,\text{tri}} = \left(\frac{AW_1}{L_1} \right) k' \left(V_{SG_2} - V_T - \frac{V_{SD_2}}{2} \right) V_{SD_2} = \frac{V_{D2}}{R_D} \quad (3)$$
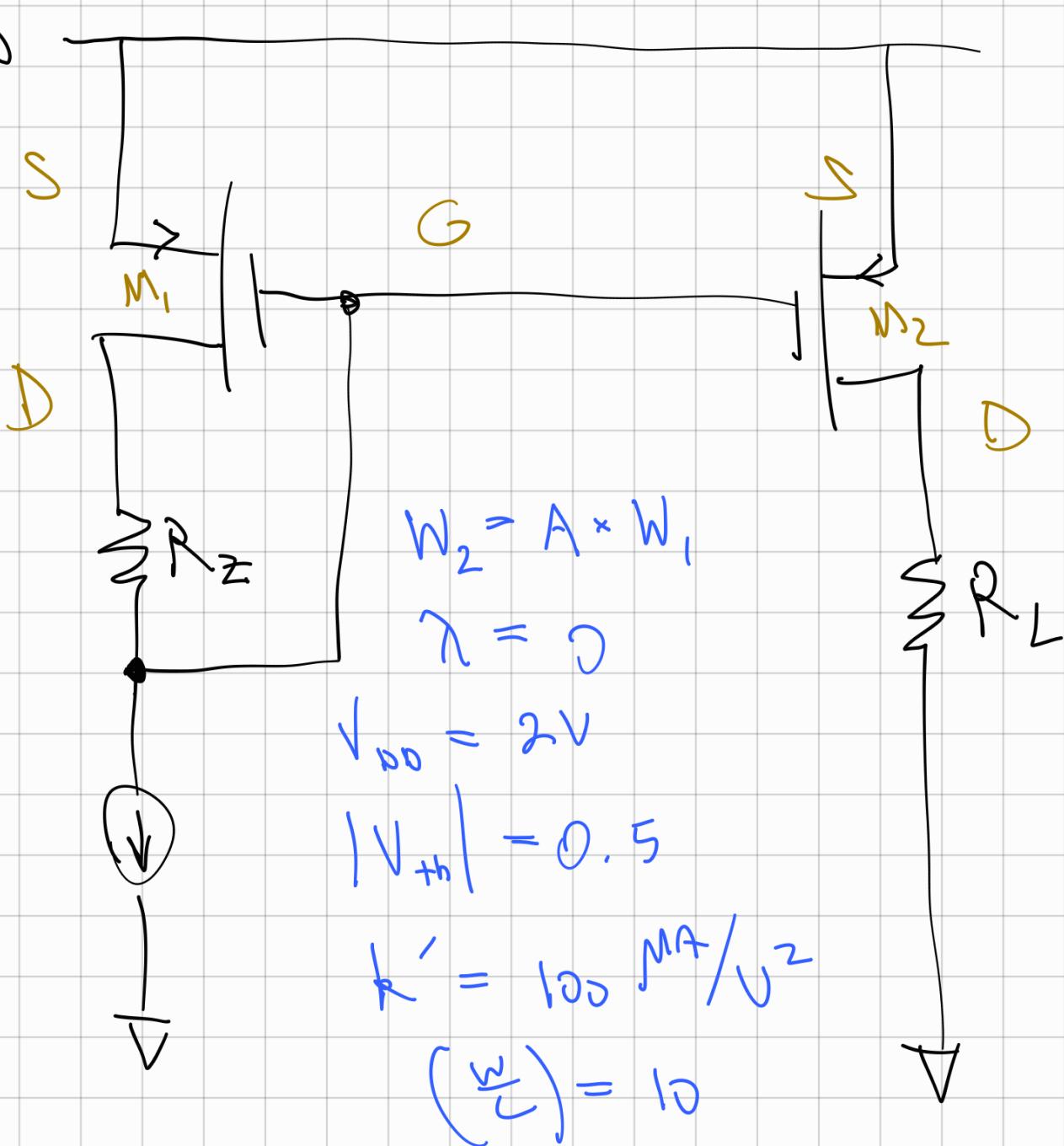
$$I_{D1,\text{tri}} = \left(\frac{W}{L} \right) k' \left(V_{SG_1} - V_T - \frac{V_{SD_1}}{2} \right) V_{SD_1} = \frac{V_{D1}}{R_z} \quad (4)$$



M_1 : $A_S i_{in} \rightarrow 0 \rightarrow \uparrow$

$$\cancel{V_{SG1}} - V_T < V_{S01}$$

$$= \cancel{V_{SG1}} - R_Z \cdot I_{in}$$

$$\Rightarrow I_{in} < \frac{V_T}{R_Z} \quad \begin{array}{l} \text{(upper bound)} \\ \text{for } I_{in} \#1 \end{array}$$

α

$I_{in, MAX}$

M2: $V_{SG_2} > V_{SG_2} - V_T$

$$V_{dd} - I_{out} \cdot R_L > V_{SG_2} - V_T$$

$$\Rightarrow I_{out} \cdot R_L < V_{dd} - V_{SG_2} + V_T$$


* Assuming both M_1 and M_2 in saturation, $I_{out} = A \cdot I_{in}$

$$\Rightarrow A \cdot I_{in} R_L < V_{dd} - V_{SG_2} + V_T$$

* $V_{SG_2} = V_{SO_1}$

* $I_{in} = \frac{1}{2} k' \left(\frac{W}{L}\right) \left(V_{SG_1} - V_T\right)^2$

$$\Rightarrow V_{SG_1} = f(I_{in})$$

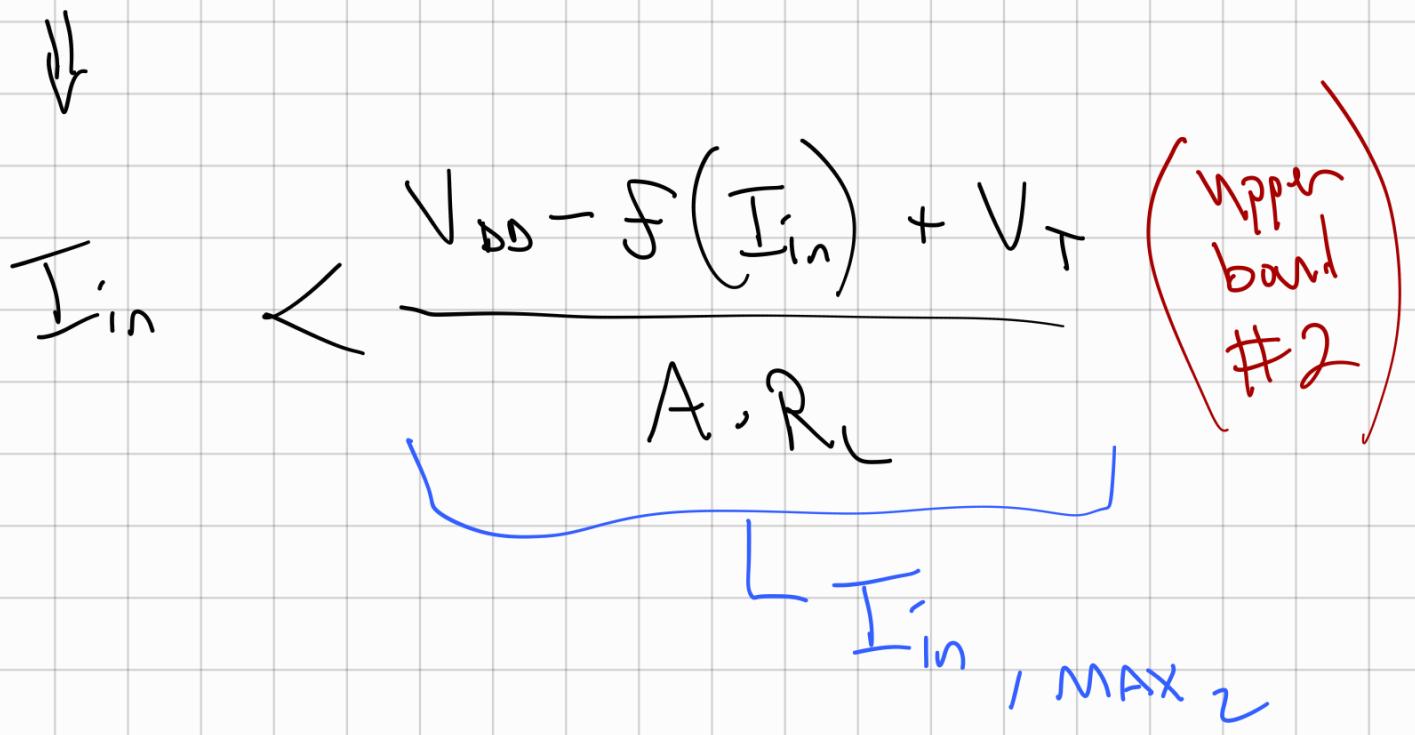

$$\Rightarrow A \uparrow \rightarrow I_{in, \text{MAX}_2} \downarrow$$

$$A \downarrow \rightarrow I_{in, \text{MAX}_1} \uparrow$$

$$\Rightarrow A_o; I_{in, \text{MAX}_1} = I_{in, \text{MAX}_2}$$

$$A > A_o \rightarrow I_{in, \text{MAX}_2} < I_{in, \text{MAX}_1}$$

I_{in} MAX₂ limit

$$A < A_o \rightarrow I_{in, \text{MAX}_2} > I_{in, \text{MAX}_1}$$

I_{in} MAX₂ limit

$$I_{in, MAX} = \begin{cases} I_{in, MAX_2}, & A > A_o \\ I_{in, MAX_1}, & A < A_o \end{cases}$$

Solving for A_o

$$I_{in} = \left(\frac{n}{e}\right)_1 k' \left(V_{SG_1} - V_T\right)^2$$

$$\Rightarrow (\Delta V)^2 = \frac{I_{in}}{\left(\frac{n}{e}\right)_1 k'}$$

$$\Rightarrow V_{SG_1} = \frac{I_{in}}{\left(\frac{n}{e}\right)_1 k'} + V_T$$

Substitute I_{in, max_1}

$$\Rightarrow \sqrt{S_{G_1}} = \sqrt{\left(\frac{n}{c}\right)_1 k' + \frac{2V_T}{R_Z} + V_T}$$

Relate I_{in, max_1} to I_{in, max_2}

$$\Rightarrow \frac{\sqrt{I}}{R_Z} = \sqrt{V_{DD}} - \frac{\sqrt{\left(\frac{n}{c}\right)_1 k' + \frac{2V_T}{R_Z} + V_T} + V_T}{A \cdot R_L}$$

Rearranging

$$\Rightarrow A = \frac{\sqrt{V_{DD}} - \sqrt{\left(\frac{n}{c}\right)_1 k' + \frac{2V_T}{R_Z} + V_T} + V_T}{R_L \cdot V_T} \cdot R_Z$$

Plugging in Values

$$A = \frac{2 - \left[\frac{2 \cdot 0.5}{1000} + 2 \cdot 0.5 \right]}{8k \cdot 0.5}$$

1K

$$A = 0.25$$

Solve for I_{in, \max_2} in Terms of A

$$I_{in} = \frac{V_{DD} - \left[\frac{I_{in}}{\left(\frac{w}{2l}\right)_1 k'} + 2V_T \right]}{A \cdot R_L}$$

\Downarrow

$$I_{in} = \frac{2 - \left[\frac{I_{in}}{10 \cdot 100 \times 10^{-6}} + 2 \cdot 0.5 \right]}{0.25 \cdot 8k}$$

Plugging into Wolfram Alpha


$$I_{in_1} = \frac{-\sqrt{48} \frac{A+1}{A^2}}{64K} + \frac{1}{A^2} + \frac{24}{A}$$

$$I_{in_2} = \frac{+\sqrt{48} \frac{A+1}{A^2}}{64K} + \frac{1}{A^2} + \frac{24}{A}$$

I_{in_2} matches the value for $I_{in_{max}}$


Final Piecewise Solution
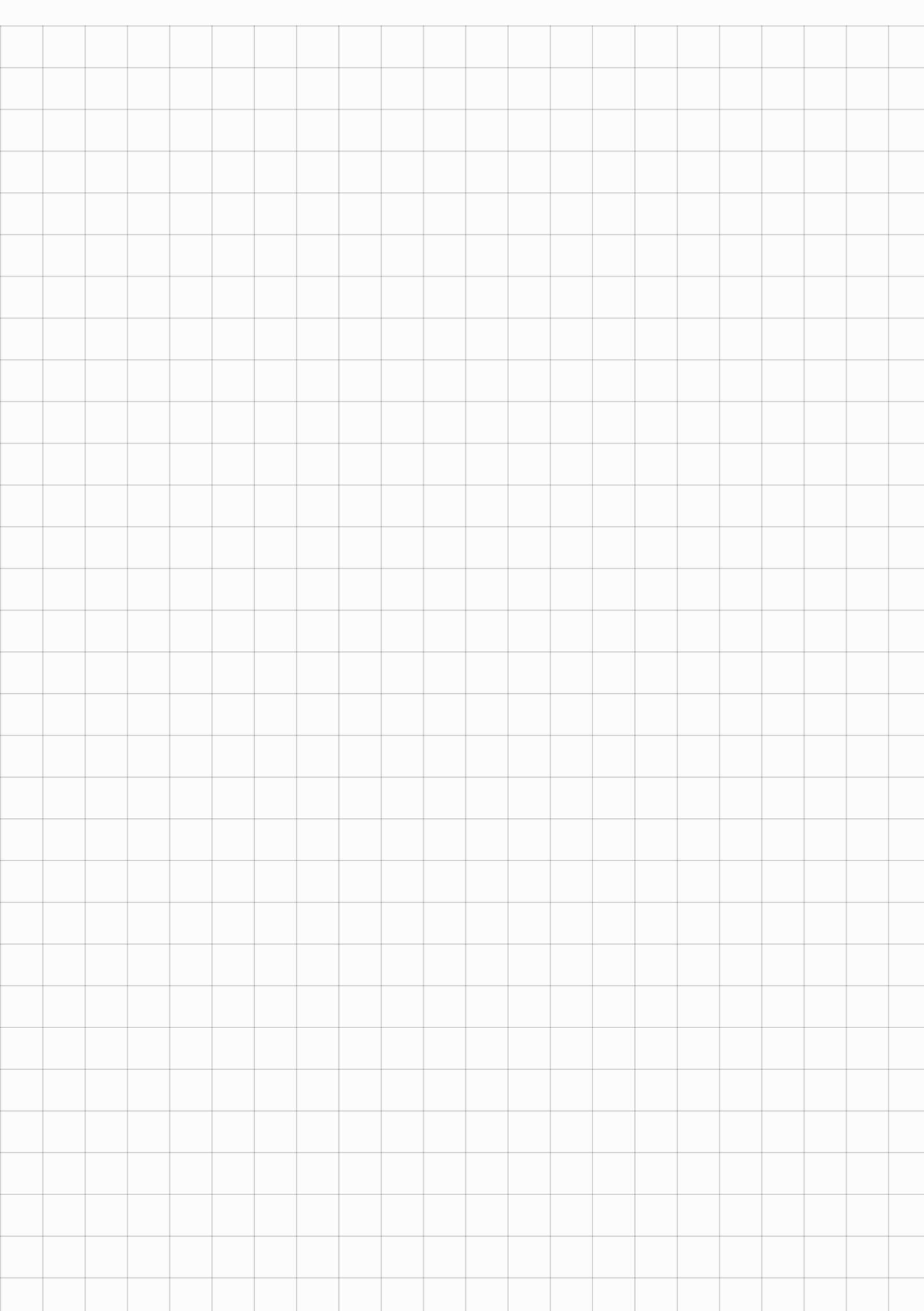
$$I_{in_{max}} = \begin{cases} 0.5A \\ \frac{\sqrt{48} \frac{A+1}{A^2}}{64K} + \frac{1}{A^2} + \frac{24}{A} \end{cases} \begin{matrix} , A < A_0 \\ , A > A_0 \end{matrix}$$




$$\lambda = 0, \gamma = 0, |V_{TH}| = 0.5V, V_{DD} = 2V$$
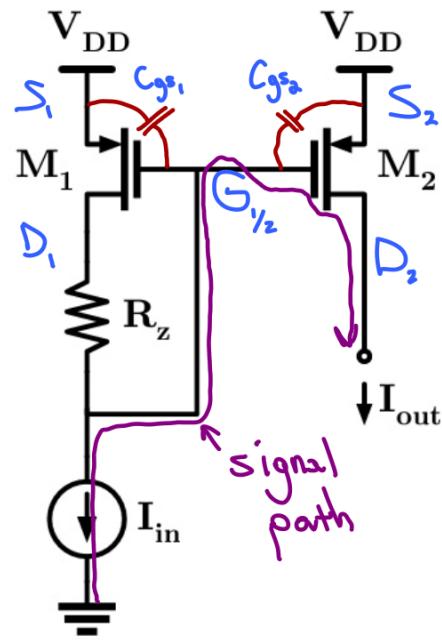
$$W_2 = A \times W_1, (\frac{W}{L})_1 = 10, k' = \mu_p C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$$




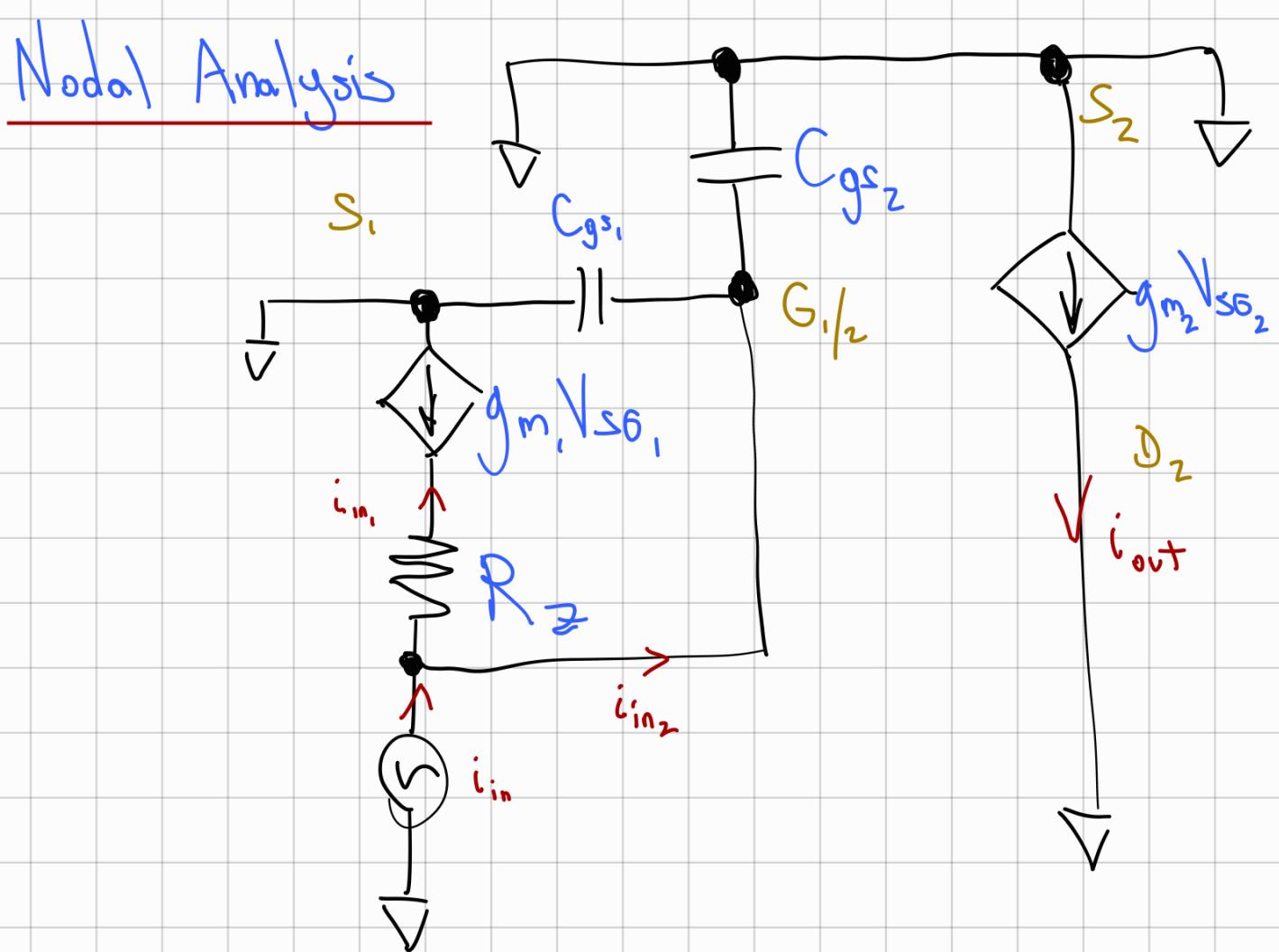- (c) Considering only the C_{gs} capacitors, derive the small signal transfer function for this amplifier $H(s) = \frac{i_{out}(s)}{i_{in}(s)}$ and draw the phase and amplitude Bode plots.



Simplified Small-Signal Model
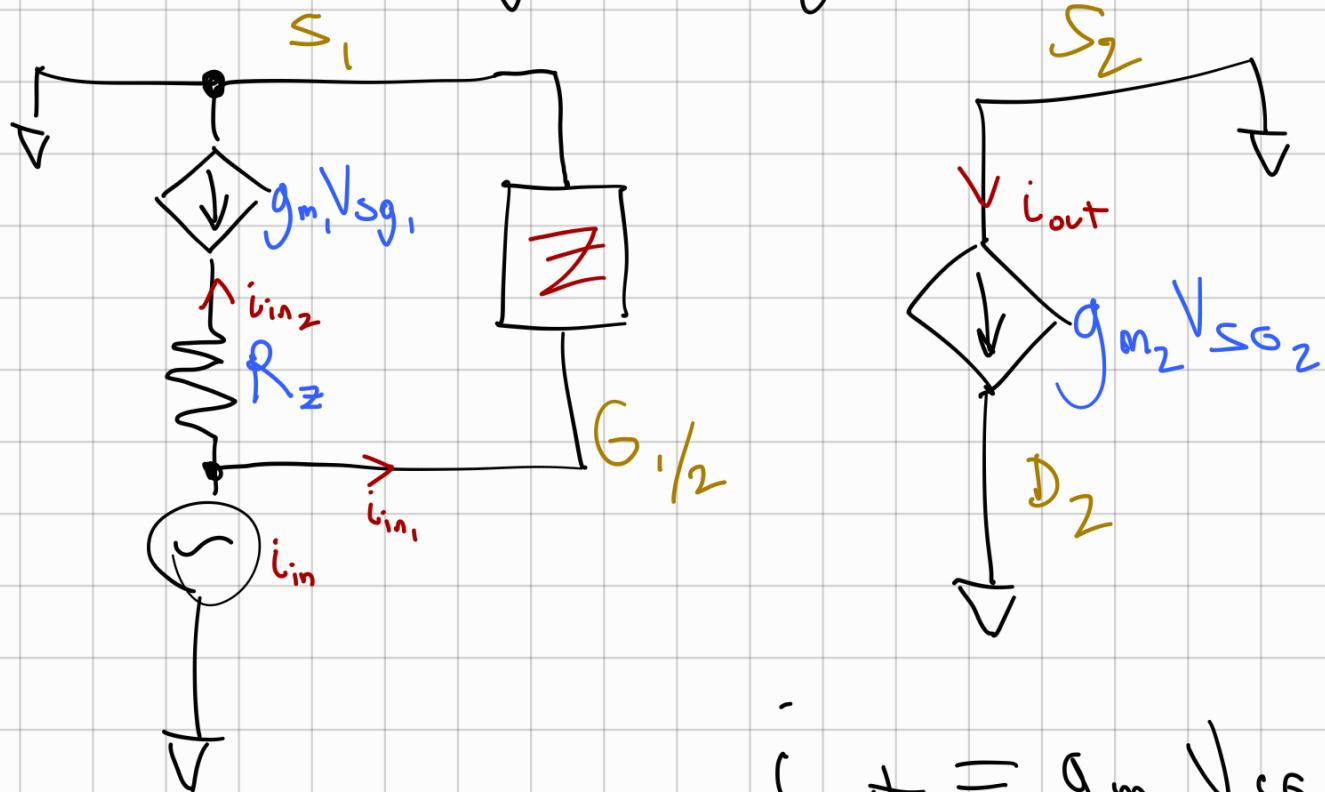
$$\text{Let } Z = C_{gs_1} \parallel C_{gs_2}$$



$$i_{out} = g_{m_2} V_{sg_2}$$

$$i_{in} = i_{in_1} + i_{in_2} = \frac{V_g}{Z} - g_{m_1} V_{sg_1}$$

$$= V_g \left(\frac{1}{Z} + g_{m_1} \right)$$

$$\frac{i_{out}}{i_{in}} = \frac{V_g - g_{m_2}}{V_g \left(\frac{1 + g_{m_1} Z}{Z} \right)}$$

$$= \frac{-g_{m_2} Z}{1 + g_{m_1} Z}$$

$$Z = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{s^2 C_{gs_1} C_{gs_2}}{\frac{1}{s C_{gs_1}} + \frac{1}{s C_{gs_2}}}$$

$$= \frac{\frac{1}{s^2 C_{gs_1} C_{gs_2}}}{\frac{C_{gs_1} + C_{gs_2}}{s C_{gs_1} C_{gs_2}}} = \frac{1}{s(C_{gs_1} + C_{gs_2})}$$

$$\Rightarrow \frac{i_{out}}{i_{in}} = \frac{-g_{m_2}}{s(C_{gs_1} + C_{gs_2})}$$

$$1 + \frac{g_{m_1}}{s(C_{gs_1} + C_{gs_2})}$$


$$\Rightarrow \frac{i_{\text{out}}}{i_{\text{in}}} = \frac{-g_{m_2}}{\frac{s(C_{gs_1} + C_{gs_2})}{g_{m_1}}}$$

$$= \frac{-g_{m_2}}{\frac{g_{m_1}}{s(C_{gs_1} + C_{gs_2})}}$$


\Rightarrow We have one LHP pole.

$$\boxed{\omega_p = \frac{g_{m_1}}{C_{gs_1} + C_{gs_2}}}$$

Bode Plot of Magnitude

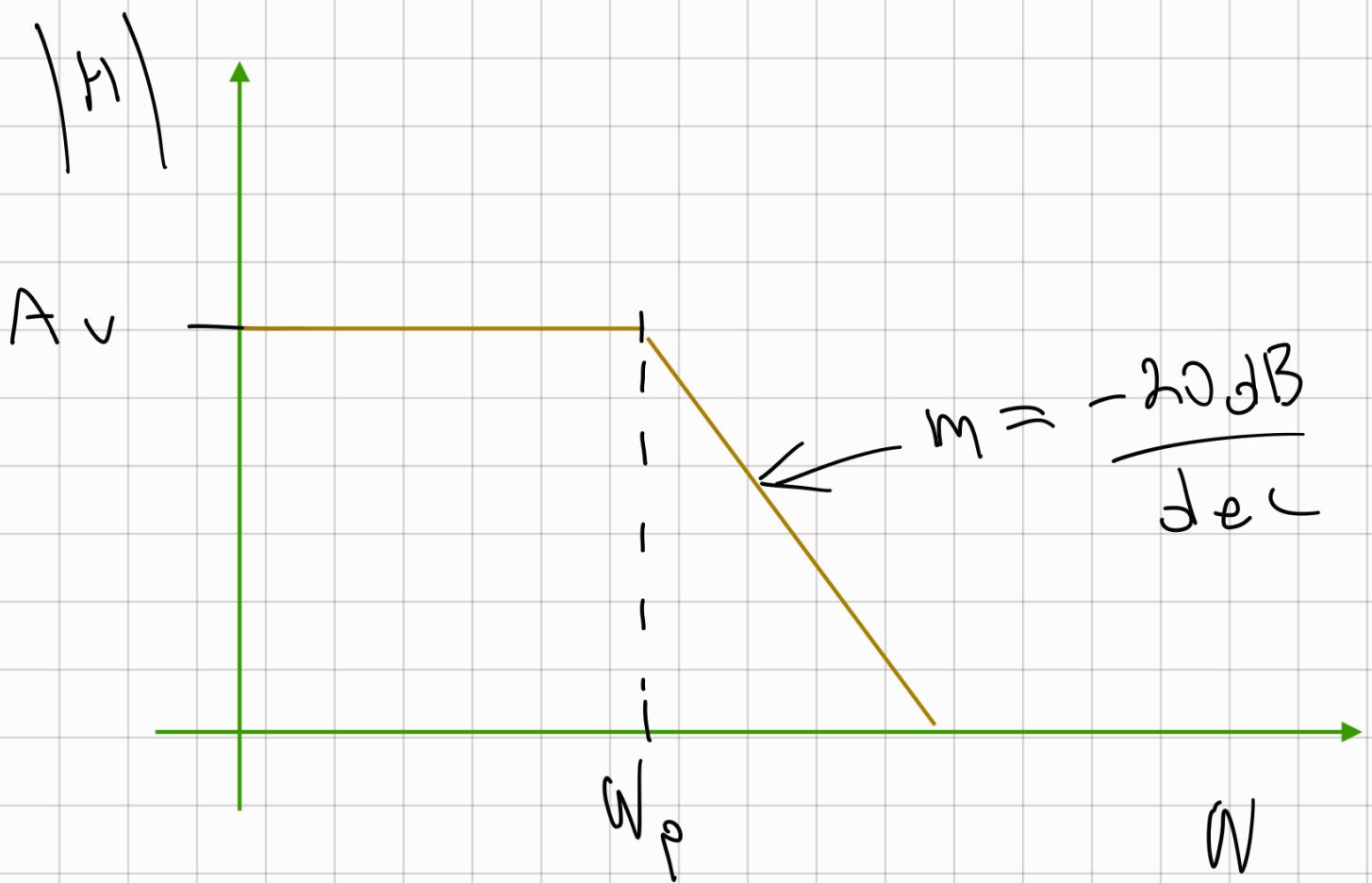


Bode Plot of Phase

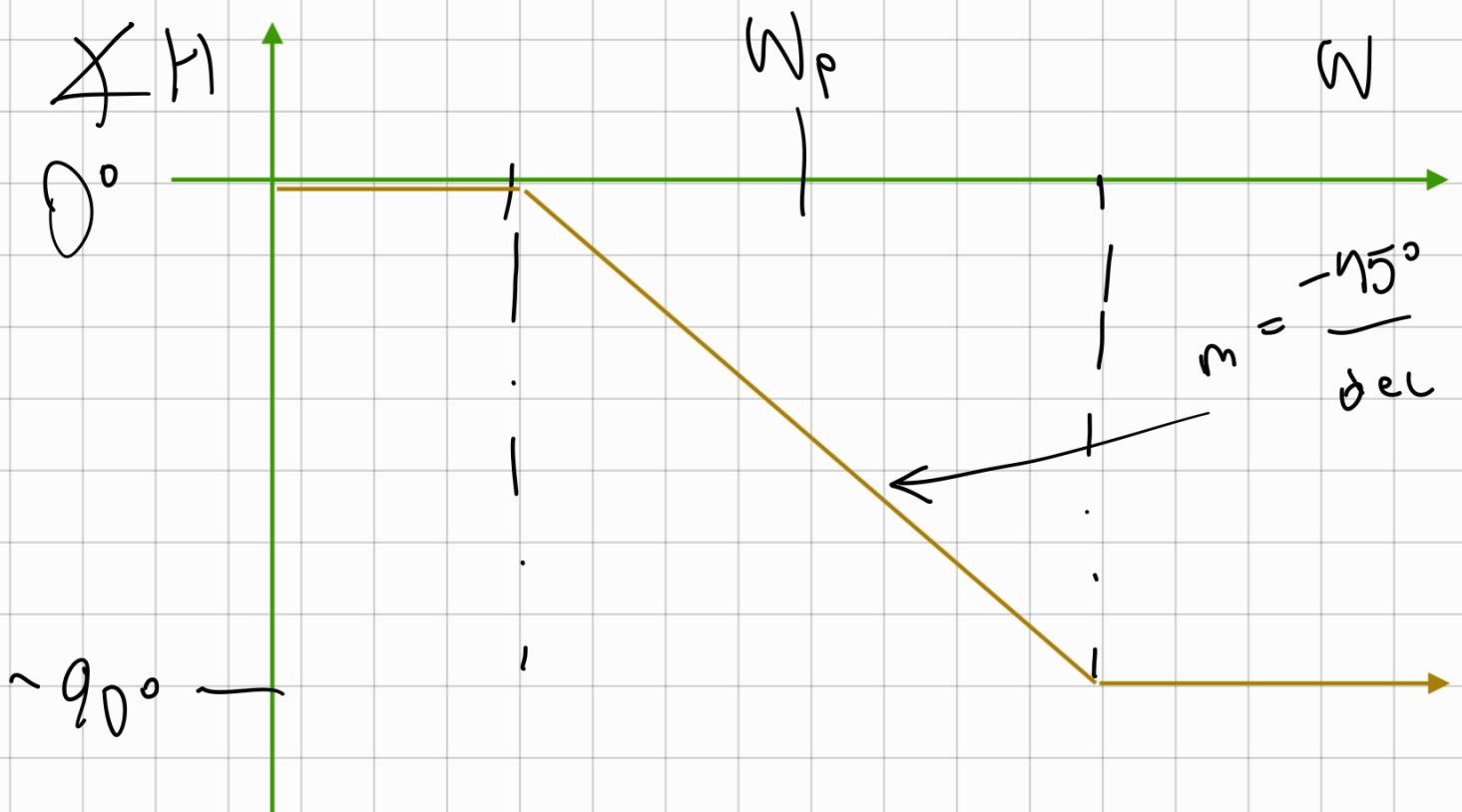


Problem 3 - Improving Current Mirrors

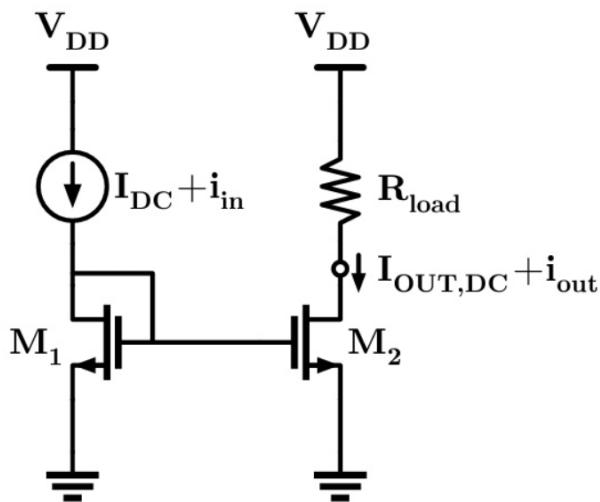- (a) For the below current mirror structure, with a small-signal input of i_{in} and an output of i_{out} , calculate the output impedance looking down from the output terminal. What would the small signal gain i_{out}/i_{in} be with a load resistor of $R_{load} = 10 \text{ k}\Omega$? $W_2 = 10 \times W_1$ and $L_2 = L_1$. Assume that I_{DC} puts M_1 in saturation, and M_1 has a g_m of $g_{m1} = 0.5 \text{ mS}$ and an r_o of $r_{o1} = 100 \text{ k}\Omega$.



Output Impedance

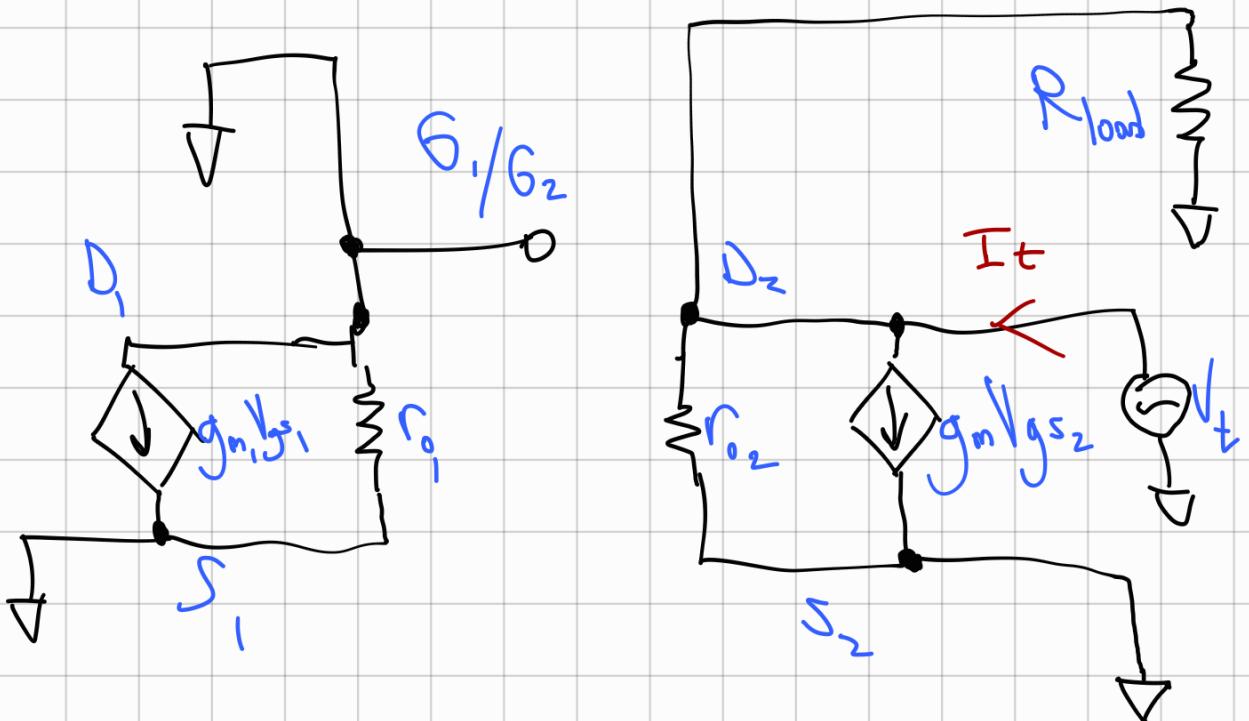

$$\frac{V_t}{R_{load}} + \frac{V_t}{r_{o2}} + g_{m2} \frac{V_t}{g_{s2}} = I_t$$

$$\Rightarrow \frac{V_t}{I_t} = R_{out}$$

$R_{out} = r_{o_2} \parallel R_{load}$


$$\Rightarrow r_{o_2} = \frac{r_{o_1}}{10} = 10K \Omega$$

$$\Rightarrow R_{out} = \frac{r_{o_2} \cdot R_{LOAD}}{r_{o_2} + R_{LOAD}} = \frac{10K \cdot 10K}{10K + 10K}$$

$$\approx 5k \Omega \leftarrow \text{Total } R_{out}$$

Small-Signal gain

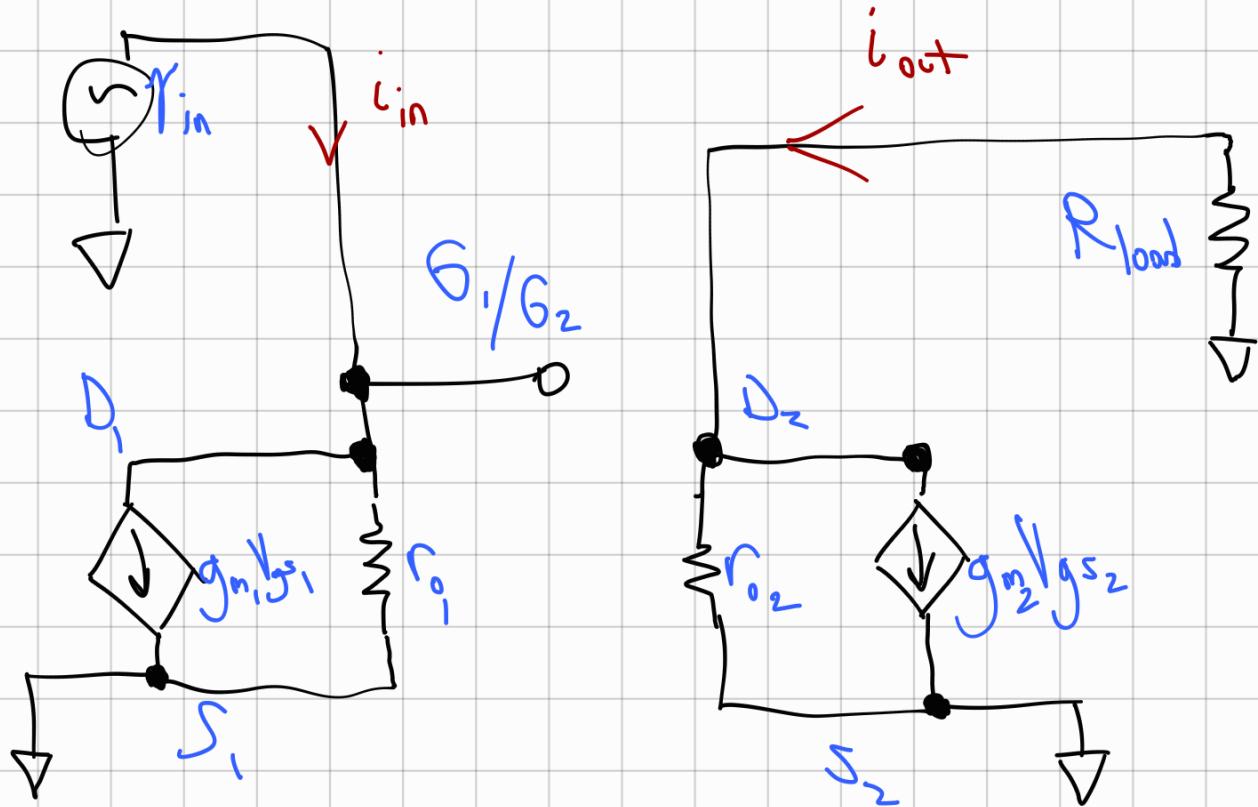* Note that: We will assume a negligible body effect, $\gamma_1 = \gamma_2$ and $M_{Cox1} = M_{Cox2}$.



$$i_{out} = \frac{-V_{D_2}}{R_{load}} \quad (1)$$

$$i_{out} = \frac{V_{D_2}}{r_{o_2}} + g_{m_2} V_{g_2} \quad (2)$$

$$i_{in} = \frac{V_{g_2}}{r_{o_1}} + g_{m_1} V_{g_2} = V_{g_2} \left(g_{m_1} + \frac{1}{r_{o_1}} \right) \quad (3)$$

Rearrange (1) \Rightarrow $V_{D_2} = -i_{out} R_{load}$ (4)

(4) into (2)

$\Rightarrow i_{out} = -i_{out} \left(\frac{R_{load}}{r_{o_2}} \right) + g_{m_2} V_{g_2} \quad (5)$

Rearrange $(2) \Rightarrow V_{g_2} = i_{in} \left(\frac{r_{o_1}}{1 + g_{m_1} r_{o_1}} \right) \quad (6)$

(6) into (5)

$$\dot{i}_{\text{out}} = -\dot{i}_{\text{out}} \left(\frac{R_{\text{load}}}{r_{o_2}} \right) + g_{m_2} \left[\dot{i}_{\text{in}} \left(\frac{r_{o_1}}{1 + g_{m_1} r_{o_1}} \right) \right]$$

$$\Rightarrow \dot{i}_{\text{out}} \left(1 + \frac{R_{\text{load}}}{r_{o_2}} \right) = \dot{i}_{\text{in}} \left(\frac{g_{m_2} r_{o_1}}{1 + g_{m_1} r_{o_1}} \right)$$

$$\Rightarrow \frac{\dot{i}_{\text{out}}}{\dot{i}_{\text{in}}} = \left(\frac{g_{m_2} r_{o_1}}{1 + g_{m_1} r_{o_1}} \right) \left(\frac{r_{o_2}}{r_{o_2} + R_{\text{load}}} \right)$$

$$\frac{\dot{i}_{\text{out}}}{\dot{i}_{\text{in}}} = \frac{g_{m_2} r_{o_1} r_{o_2}}{(1 + g_{m_1} r_{o_1})(r_{o_2} + R_{\text{load}})}$$

Find g_{m_2} : Because of the scaling ratio of current mirrors, we know that $g_{m_2} = 10 \cdot g_{m_1}$


$$\Rightarrow g_{m_2} = 10 \cdot 0.5 \text{ mS}$$

$$\therefore g_{m_2} = 5 \text{ mS}$$

$$\begin{aligned}
 \Rightarrow \frac{i_{out}}{i_{in}} &= \frac{g_{m_2} r_{o_1} r_{o_2}}{(1 + g_{m_1} r_{o_1})(r_{o_2} + R_{load})} \\
 &= \frac{(5 \times 10^{-3} S)(100 k\Omega)(10 k\Omega)}{(1 + 0.5 \times 10^{-3} S \cdot 100 k\Omega)(20000)} \\
 &= \frac{5000000}{51.2 \times 10^6} \\
 &= \frac{50000000}{1020000} \\
 &= 4.901960784
 \end{aligned}$$


$\therefore A_i \approx 4.9$

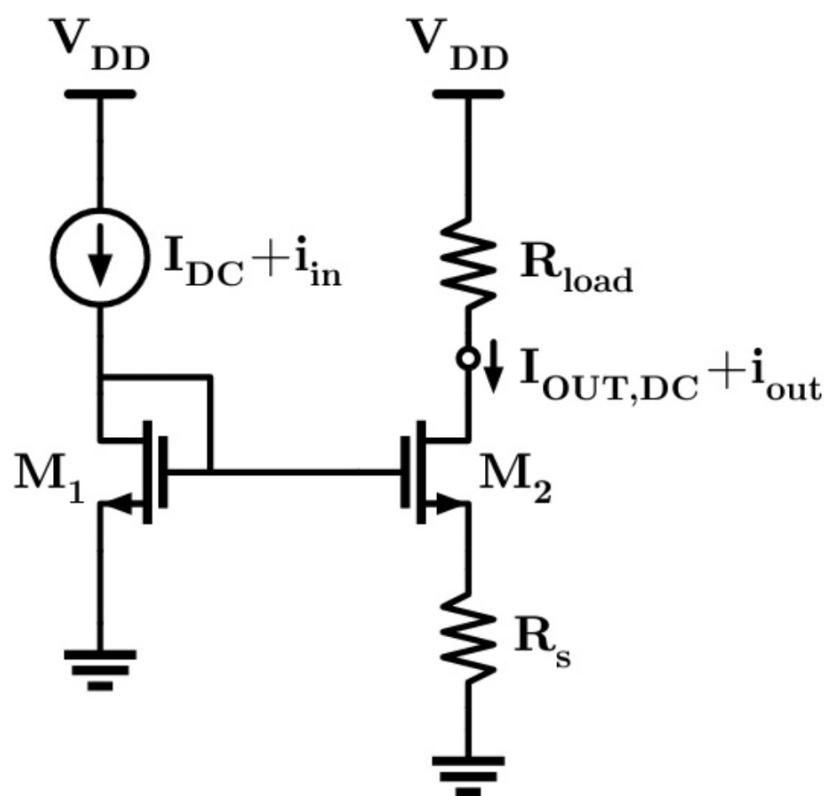- (b) Your coworker has suggested that by adding a degeneration resistor $R_s = 1 \text{ k}\Omega$, you could improve the output impedance and hence the overall gain under high impedance loads. Would the new structure work as a current mirror? Why/why not?



This would not work as a current mirror, because with the addition of R_s the V_{GS} of both transistors will not be the same.

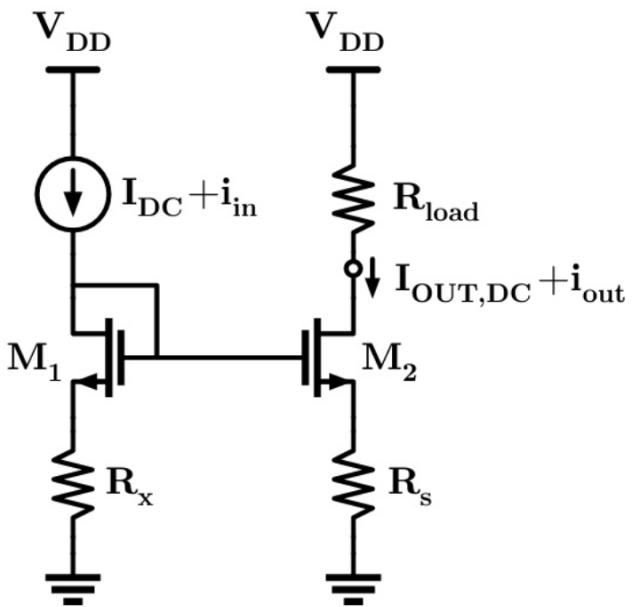- (c) You decide to improve upon the previous structure by adding an R_x . Now, for this structure to act as a current mirror, what should the value of R_x be if $R_s = 1 \text{ k}\Omega$? Compute the new small signal output impedance R_{out} for the mirror. What would the new gain i_{out}/i_{in} be with a load resistor of $R_{load} = 10 \text{ k}\Omega$?



Finding a Value for R_x


We want to match ΔV_1 to ΔV_2 for a proper current mirror. Since R_{LOAD} has no impact on ΔV_2 , and M_2 scales the current in M_1 by a factor of D , we need to reduce the value of R_x by a factor of D relative to the value of R_s .

$$\Rightarrow R_x \cdot I_{DC} = 10 \cdot I_{DC} \cdot R_s$$

continues ...

$$\Rightarrow R_x = 10 \cdot R_s = 10K \Omega$$

Small-signal Model

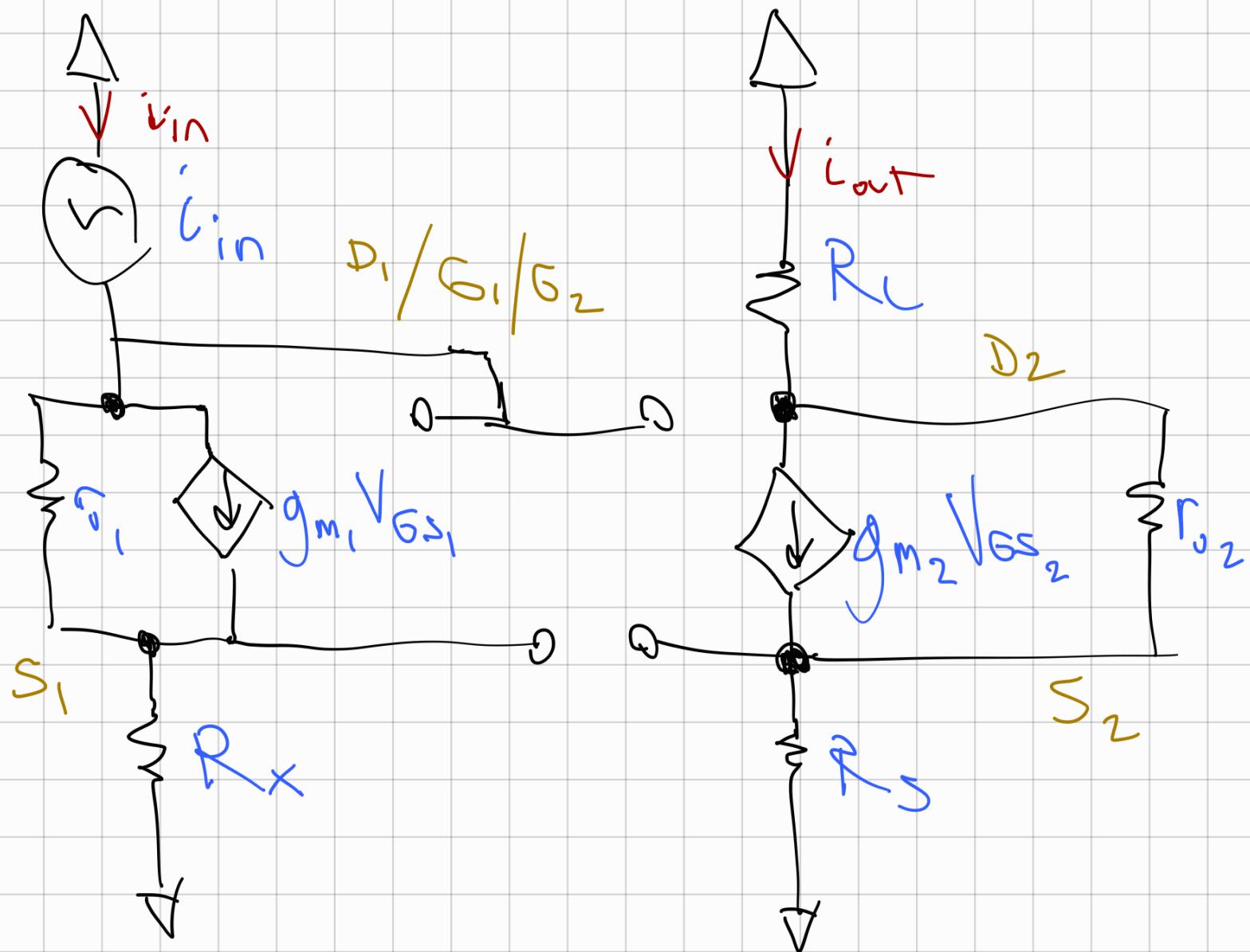

$$i_{in} = \frac{V_g}{r_{o_1}} + g_m V_{gs_1} = V_g \left(g_m + \frac{1}{r_{o_1}} \right) - g_m V_{s_1} \quad (1)$$

$$V_{in} = \frac{V_{s_1}}{R_X} \Rightarrow V_{s_1} = i_{in} \cdot R_X \quad (2)$$

$$i_{out} = \frac{V_{d_2}}{r_{o_2}} + g_{m_2} V_{gs_2} \quad (3)$$

$$i_{out} = \frac{V_{s_2}}{R_S} \Rightarrow V_{s_2} = i_{out} \cdot R_S \quad (4)$$

$$i_{out} = -\frac{V_{d_2}}{R_L} \Rightarrow V_{d_2} = -i_{out} \cdot R_L \quad (5)$$

(2) int (1)

$$\Rightarrow i_{in} = V_g \left(g_{m_1} + \frac{1}{r_{o_1}} \right) - g_{m_1} (i_{in} \cdot R_X)$$

$$\Rightarrow i_{in} \left(1 + g_{m_1} R_X \right) = V_g \left(g_{m_1} + \frac{1}{r_{o_1}} \right)$$

$$\Rightarrow i_{in} = V_g \left(\frac{1 + g_{m1} r_{o1}}{r_{o1}} \right) \left(\frac{1}{1 + g_{n1} R_x} \right) \quad (6)$$

(4) and (5) into (3)

$$\Rightarrow i_{out} = -i_{out} \left(\frac{R_L}{r_{o2}} \right) + g_{m2} V_g - g_{m2} i_{out} \cdot R_S$$

$$\Rightarrow i_{out} \left(1 + \frac{R_L}{r_{o2}} + g_{m2} R_S \right) = g_{m2} V_g$$

$$\Rightarrow i_{out} = V_g \left(\frac{r_{o2} g_{n2}}{r_{o2} + R_L + g_{m2} r_{o2} R_S} \right)$$

$$\Rightarrow \frac{i_{out}}{i_{in}} = \frac{V_g \left(\frac{r_{o2} g_{n2}}{r_{o2} + R_L + g_{m2} r_{o2} R_S} \right)}{V_g \left(\frac{1 + g_{m1} r_{o1}}{r_{o1}} \right) \left(\frac{1}{1 + g_{n1} R_x} \right)}$$

~~$$V_g \left(\frac{1 + g_{m1} r_{o1}}{r_{o1}} \right) \left(\frac{1}{1 + g_{n1} R_x} \right)$$~~

$$\frac{i_{out}}{i_{in}} = \left(\frac{r_{o_2} g_{m_2} r_{s_1} (1 + g_{m_1} R_X)}{r_{o_2} + R_L + g_{m_2} r_{o_2} R_S (1 + g_{m_1} r_{o_1})} \right)$$

$$g_{m_1} = 0.5 m$$

$$g_{m_2} = 5 m$$

$$r_{o_1} = 100 k$$

$$r_{o_2} = 10 k$$

$$R_X = 6 k$$

$$R_S = 1 k$$


$$R_L = 10 k$$

$$\frac{i_{out}}{i_{in}} = \frac{(5 \times 10^6)(6)}{20 k + 5000(5)}$$

..

$$A_i \approx 11.67$$

Output Resistance

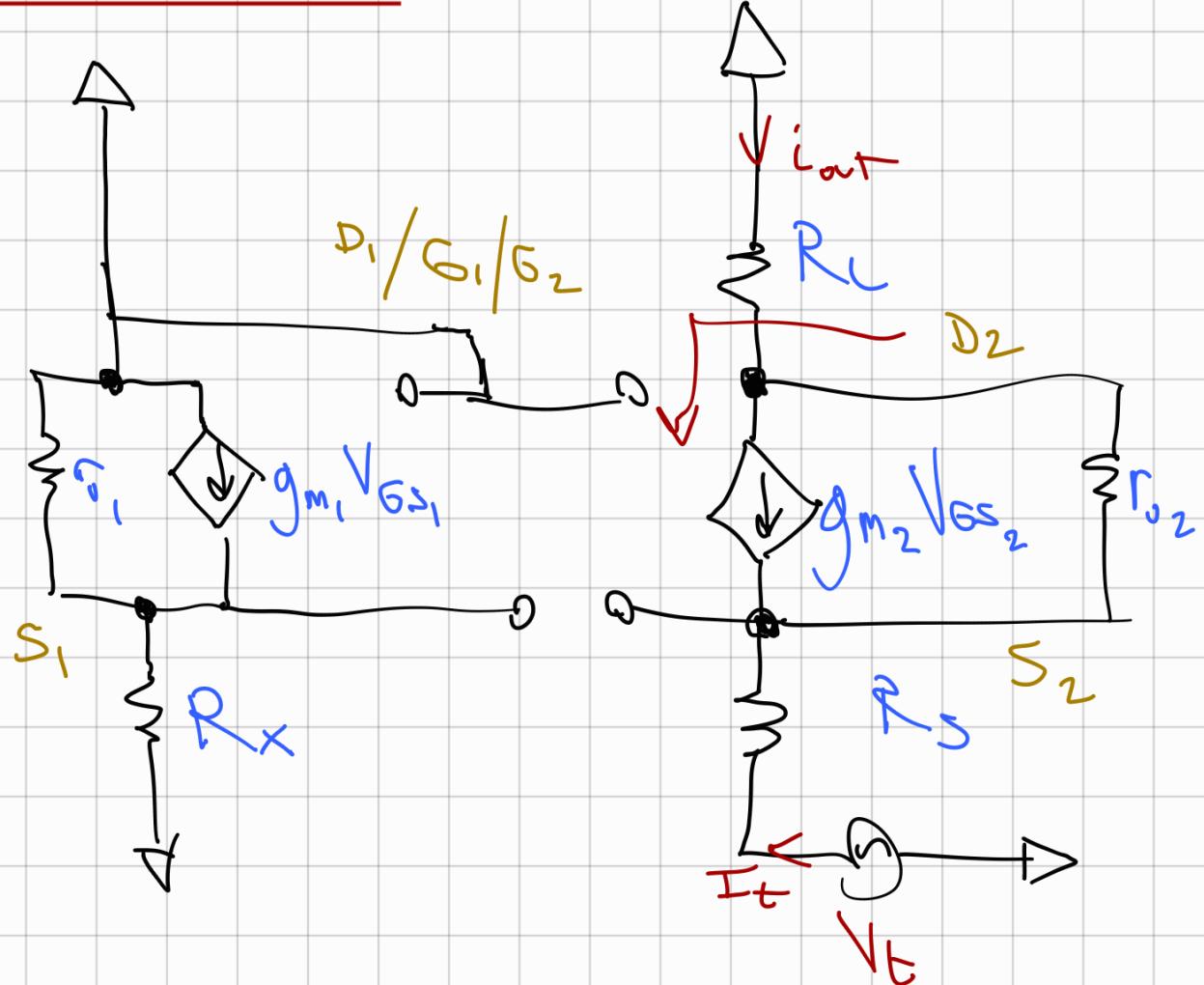

Looking down →

$$R_{th_1\theta} = g_m r_{o_2} R_S + R_J + r_s$$

$$\therefore R_{out\ total} = R_L \parallel R_{th_1\theta}$$

Numerical

$$R_{th_1\theta} = 61k\Omega \quad R_{out} = 8.6k\Omega$$