

Problem 1 - Cascode Current Mirror Biasing

Consider the wide-swing cascode current mirror in figure 1, with parameter values listed in the table. All devices are sized similarly (W) except for M_5 which has a different size (W_5).

I_B	$100 \mu A$
L	$1 \mu m$
$ k' $	$225 \mu A \cdot V^{-2}$
λ	$0.02 V^{-1}$
$ V_{TH} $	$0.6 V$
γ	0

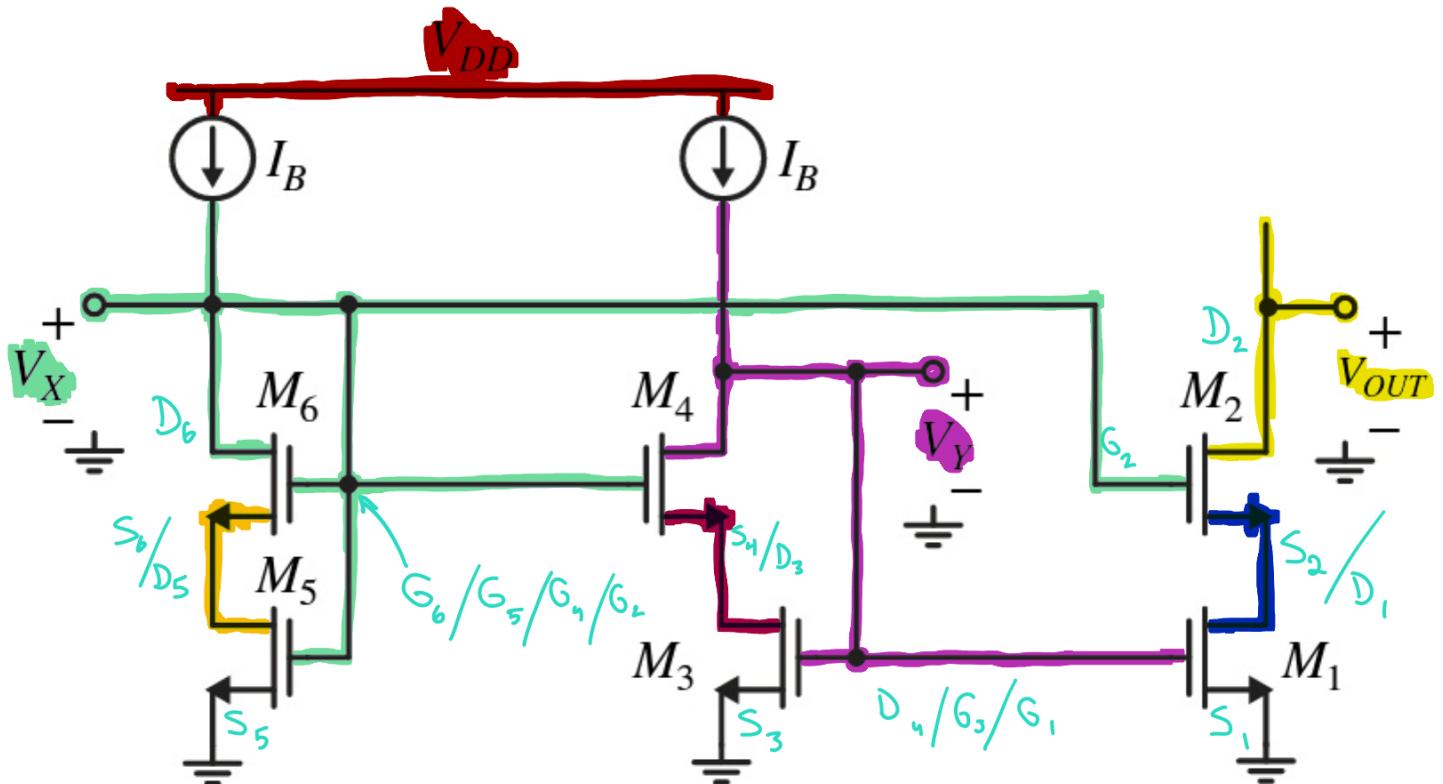


Figure 1: Circuit for problem 1

- (i) Calculate W such that the minimum output voltage for which both M_1 and M_2 are in saturation is 0.5V. Assume that M_{3-5} can provide appropriate gate biases for M_1 and M_2 . Neglect channel length modulation when performing large signal computations.

$$V_{DS_1} + V_{DS_2} = 0.5 \text{ V} = V_{out}$$

$$V_{DS_1} = 0.25 \text{ V} \Rightarrow V_{DS_2} = 0.25 \text{ V}$$

$$\Rightarrow V_{DS_2} = V_{GS_2} - V_T$$

$$\Rightarrow 0.25 \text{ V} = V_{GS_2} - 0.25 - V_T$$

$$\Rightarrow V_{GS_2} = 0.25 \text{ V} + 0.25 \text{ V} + 0.6 \text{ V}$$

$$\Rightarrow V_{GS_2} = 1.1 \text{ V}$$

$$\Rightarrow V_{GS_2} = 0.85 \text{ V}$$

$$\Rightarrow I_B = \left(\frac{W}{L}\right)_2 k' \left(V_{GS_2} - V_T\right)^2$$

$$\Rightarrow W = \frac{2 \cdot L \cdot I_B}{k' (V_{GS_2} - V_T)^2}$$

$$= \frac{1 \mu\text{m} \cdot 190 \mu\text{A} \cdot 2}{225 \mu\text{A}/\text{V}^2 (0.85\text{V} - 0.6\text{V})^2}$$

• • $W \hat{=} 19.22 \mu\text{m}$

(ii) Calculate W_5 such that the minimum output voltage in part "i" is achieved.

$$\Rightarrow V_{GS_5} = 1.1V \quad \& \quad I_{D_5} = I_{D_6} = I_B$$

$$\Rightarrow I_{D_6} = \left(\frac{W}{2L}\right)_6 k' (V_{GS_6} - V_T)^2$$

* $V_{GS_6} = V_x - V_{S_6}$ * $V_x = V_{g_2} = 1.1V$

$$\Rightarrow V_x - V_{S_6} - V_T = \sqrt{\frac{2L \cdot I_{D_6}}{k' W}}$$

$$\Rightarrow V_{S_6} = V_x - \sqrt{\dots} - V_T$$

$$= 1.1V - \frac{2 \cdot 1 \cdot 100 \mu A}{225 \mu A/V^2 \cdot 19.22} - 0.6$$

$$1.1V - 0.25V - 0.6V$$

$$\approx 0.25V$$

$$\Rightarrow V_{GS_6} = 0.85V \quad * V_{g_2} = V_{g_6} \\ = V_{g_5}$$

$$\Rightarrow V_{ds5} = V_{s_6} = 0.25V$$

$$\begin{aligned} < V_{gs5} - V_T &= 1.1V - 0.5V \\ &= 0.6V \end{aligned}$$

$\Rightarrow M_5$ is in triode.

$$\Rightarrow I_B = \left(\frac{w}{L}\right)_5 k' \left(V_{gs5} - V_{Tn} - \frac{V_{ds5}}{2} \right) V_{ds5}$$

$$\Rightarrow W_5 = \frac{I_B \cdot L_5}{k' \left(V_{gs5} - V_{Tn} - \frac{V_{ds5}}{2} \right) V_{ds5}}$$

$$= \frac{100\text{mA} \cdot 1\text{mm}}{225 \frac{\text{mA}}{\text{V}^2} \left(1.1V - 0.6V - \frac{0.25V}{2} \right) 0.25V}$$




$$= 1.74074 \times 10^{-6} \text{ m}$$

$$W_5 \approx 1.74 \text{ mm}$$

(iii) Briefly explain the function of M_4 in the circuit.

The main purpose of M_4 is to keep the V_{ds} across M_3 the same as where it is being mirrored from. This minimizes the mismatch and systematic gain error between M_1 & M_3 .

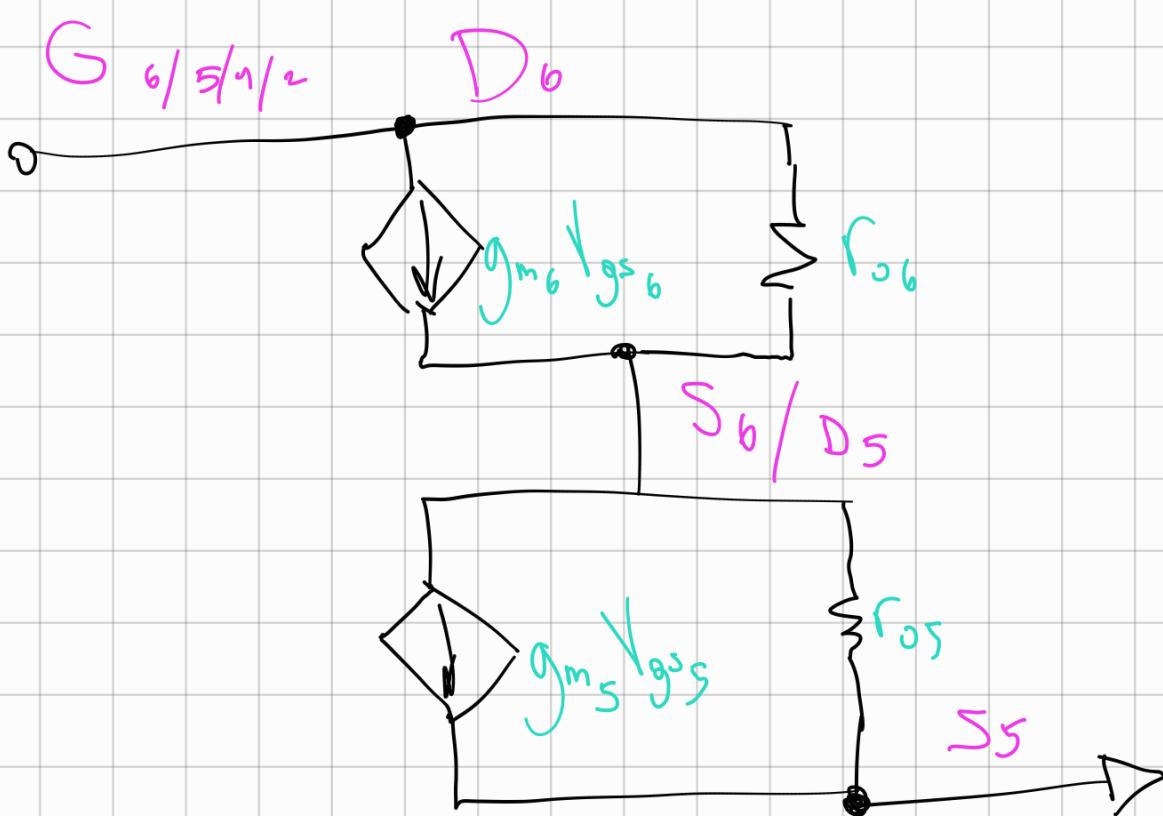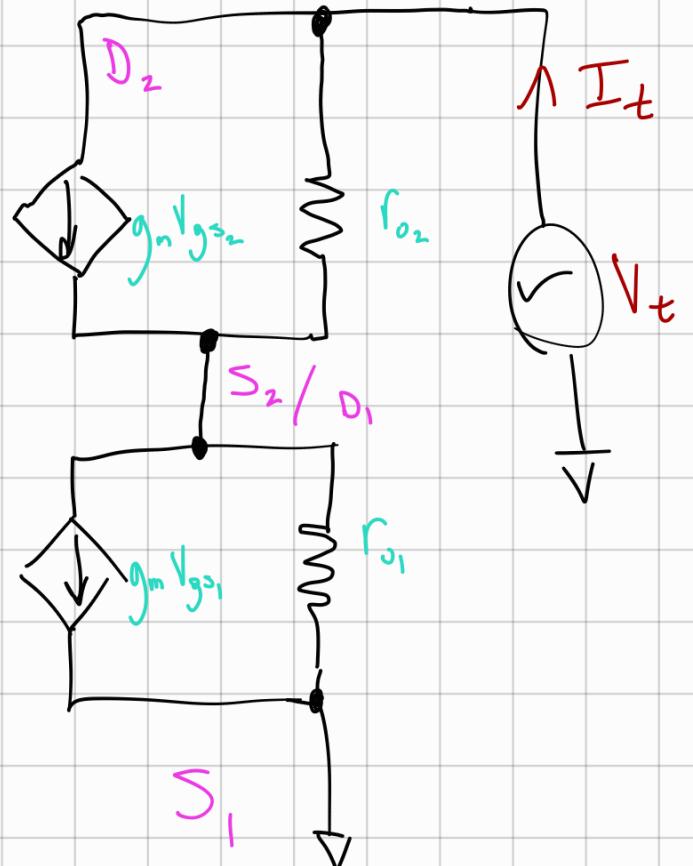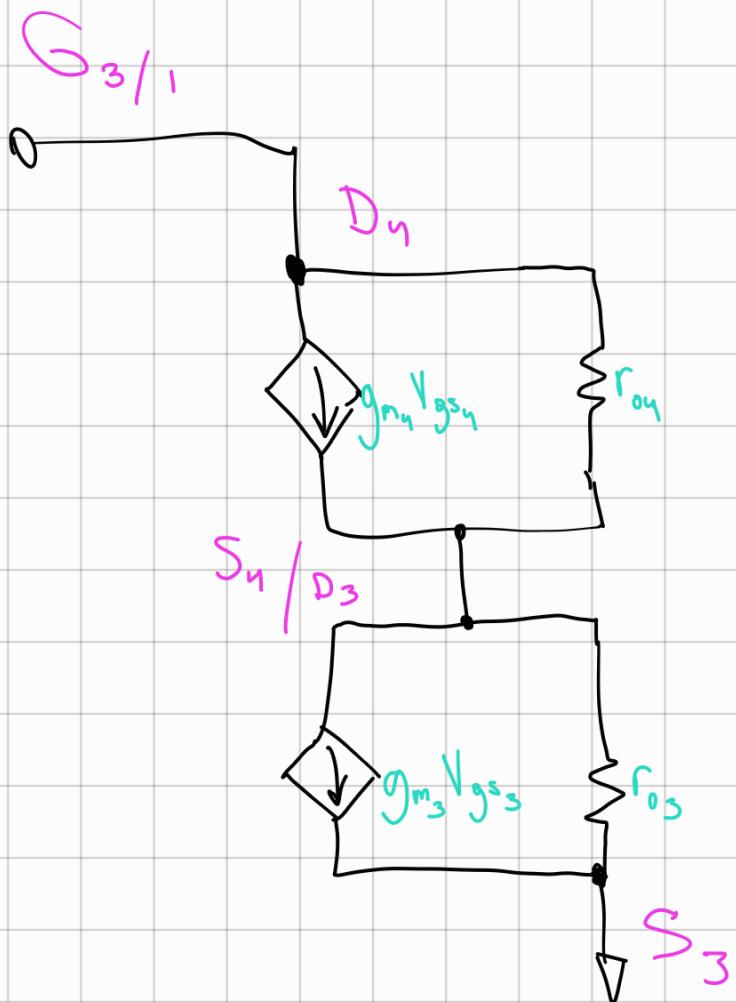- (iv) What is the small signal output resistance of this current source? [R_{OUT} is the AC resistance looking into the output port]



$$I_t = \frac{V_t}{r_{o_2}} - \frac{s_2}{r_{o_2}} + g_{m_2} V_{gs_2} = \frac{V_{s_2}}{r_{o_1}}$$

$$\Rightarrow I_t = \frac{V_t}{r_{o_2}} - \frac{1}{r_{o_2}} (I_t r_{o_1}) - g_{m_2} (I_t r_{o_1})$$

$$\Rightarrow I_t \left(1 + \frac{r_{o_1}}{r_{o_2}} + g_{m_2} r_{o_1} \right) = \frac{V_t}{r_{o_2}}$$

$$\Rightarrow \frac{V_t}{I_t} = r_{o_2} \left(\frac{r_{o_1} + r_{o_2} + g_{m_2} r_{o_1} r_{o_2}}{r_{o_2}} \right)$$

$$\Rightarrow R_{out} = r_{o_2} + r_{o_1} \left(1 + g_{m_2} r_{o_2} \right)$$

$$\Rightarrow r_o = \frac{1}{\lambda + \omega} = \frac{1}{0.02 \text{ V} \cdot 100 \mu\text{A}}$$

$$= 500 \text{ k}\Omega = r_{o_1} = r_{o_2}$$

$$\Rightarrow g_{m_2} = \frac{2 I_B}{V_{gs_5} - V_T} = \frac{2 \cdot 100 \mu\text{A}}{1.1 \text{ V} - 0.6 \text{ V}}$$


$$= 1 \times 10^{-4} \text{ S}$$

$$\Rightarrow R_{out} = 500K + 500K \left(1 + 7 \times 10^{-4} s, 500K \right)$$

$$= 10100000 \Omega$$

$$\therefore R_{out} \approx 101 M\Omega$$

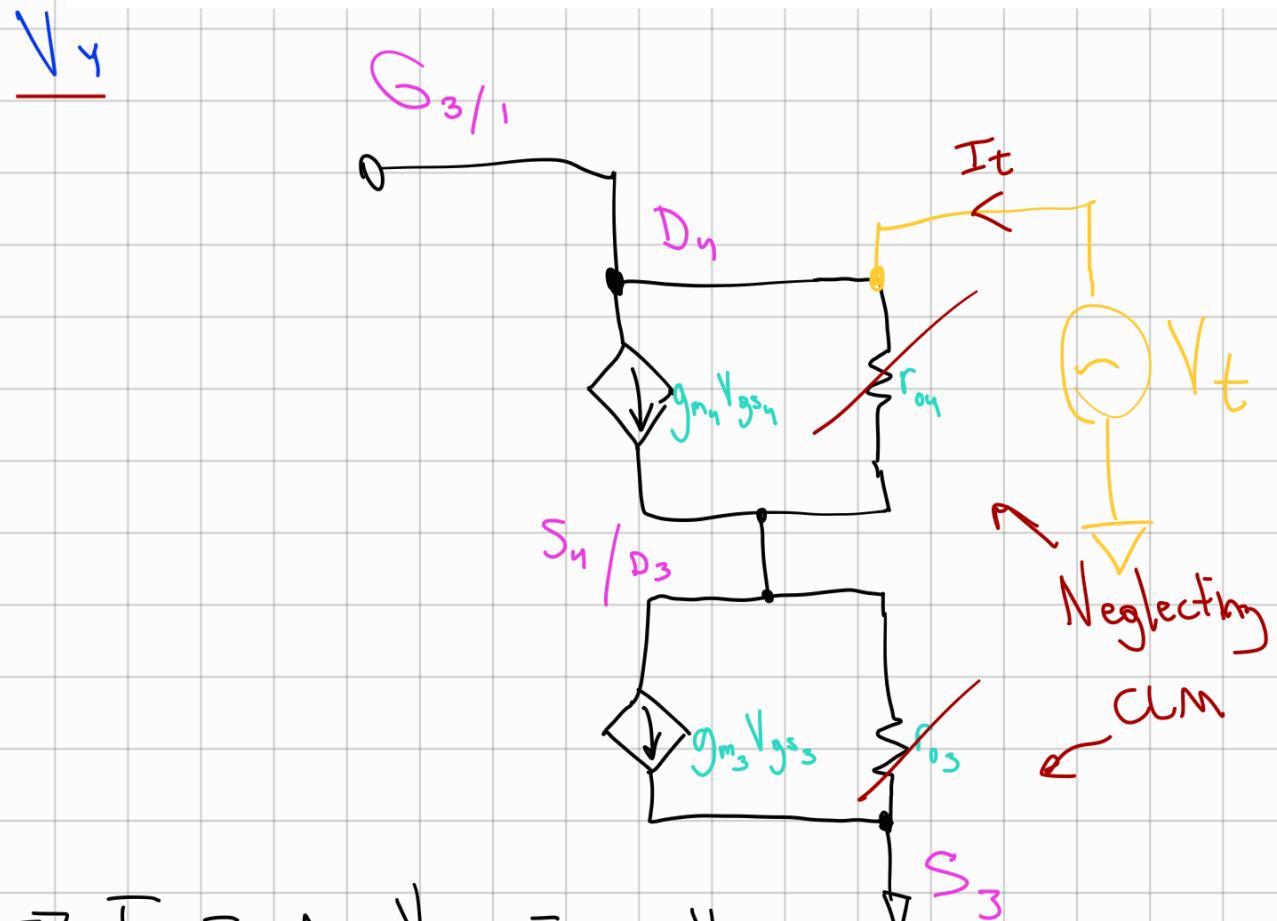- (v) What is the small signal resistance seen looking at the V_Y and V_X ports? In this part, you may neglect channel length modulation i.e. assume $\lambda = 0$.



$$\Rightarrow I_t = g_{m_1} V_{g_{s1}} = g_{m_3} V_{g_{s3}}$$


$$= -g_{m_1} V_{S_1} = g_{m_3} V_t$$

$$\Rightarrow I_t = g_{m_3} V_t \Rightarrow R_{out Y} = \frac{1}{g_{m_3}}$$

$\therefore R_{out Y} = \frac{1}{g_{m_3}} = \frac{1}{4 \times 10^{-4} S}$

$\therefore R_{out Y} = 2500 \Omega$

V_x

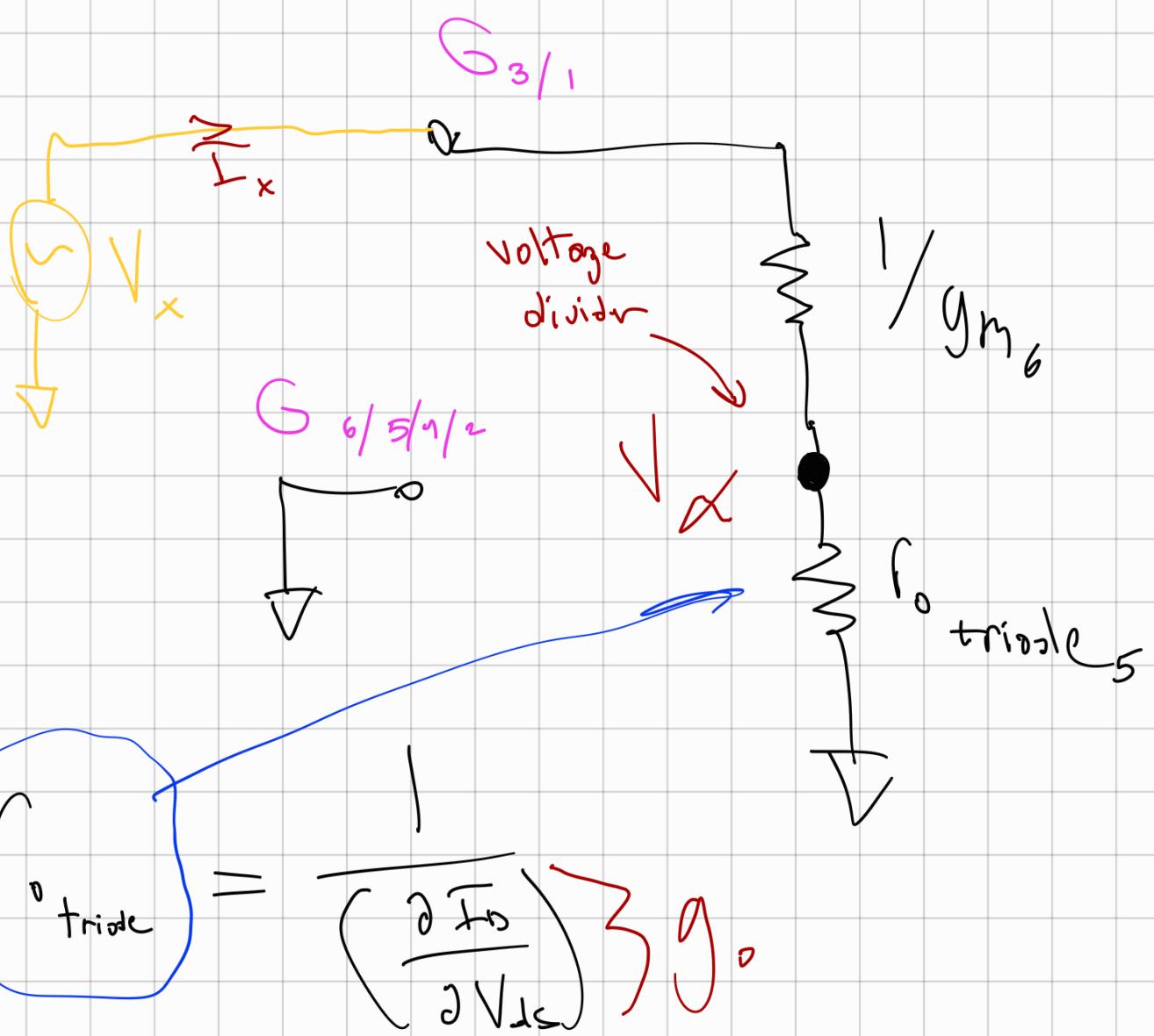

$$C_0 \text{ triode} = \frac{1}{\left(\frac{\partial I_0}{\partial V_{ds}} \right) \beta g_0}$$

$$\begin{aligned} \frac{\partial I_0}{\partial V_{ds}} &= \left[\left(\frac{w}{L} \right)_S k' \left(V_{gs5} - V_T - \frac{V_{ds5}}{2} \right) V_{ds5} \right] \\ &= \frac{\partial I_0}{\partial V_{ds}} \left[\phi \left(V_{gs5} - V_T \right) V_{ds5} - \phi \frac{V_{ds5}^2}{2} \right] \end{aligned}$$

$$= \phi(V_{gs_5} - V_T) - \frac{q}{2} V_{ds_5}$$

$$= \phi(V_{gs_5} - V_T - \frac{1}{2} V_{ds_5})$$

$$= \left(\frac{n}{c}\right)_5 k' \left(V_{gs_5} - V_T - \frac{1}{2} V_{ds_5}\right)$$

$$I_x = \frac{V_x}{\left(\frac{1}{g_{m_6}} + r_{triode_5}\right)}$$

$$= \frac{V_x}{1 + g_{m_6} r_{triode_5}}$$

$$\bullet R_{out_x} = \frac{1 + g_{m_6} r_{triode_5}}{g_{m_6}}$$

$$\Rightarrow r_o \text{ triode} = \frac{1}{\left(\frac{n}{l}\right)_S k' \left(V_{gs_S} - V_T - \frac{1}{2}V_{ds_S}\right)}$$

$$= \frac{1}{\left(\frac{4.7n\mu_m}{1\mu_m}\right) \left(225 \frac{mA}{V^2}\right) \left(1.1V - 0.6V - \frac{0.25V}{2}\right)}$$

$$\approx 2.5k\Omega$$

$$\Rightarrow g_{m_0} = g_{m_2} = 1 \times 10^{-4} S$$

$$\Rightarrow R_{out_x} = \frac{1 + (2.5k)(1 \times 10^{-4})}{1 \times 10^{-4} S}$$

. . . $R_{out_x} \approx 5k\Omega$

Problem 2 - Advanced cascode current mirrors

Figure 2 shows two cascode current mirrors featuring different biasing techniques. Assume all devices are sized similarly except for M_9 in sub-figure (b). Also assume that $I_B = 10\mu A$, $\Delta V_{1-8} = 0.1V$, $V_{TH} = 0.5V$, $\lambda = 0.1V^{-1}$, and $\gamma = 0$.

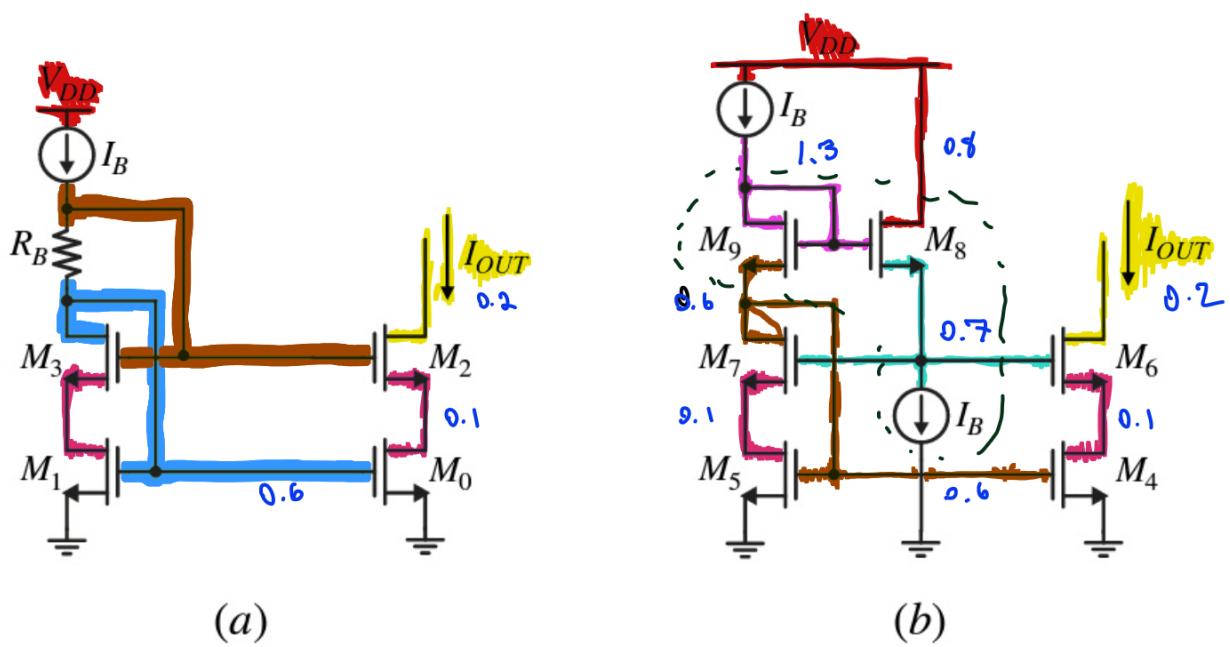


Figure 2: Circuits for problem 2

- (a) Find the value of the output current, I_{OUT} , as well as the output resistance, R_{OUT} , in both circuits in figure 2.

All of I_B goes through M_3 and M_1 .

Since it is a current mirror and

$\Delta V_1 = \Delta V_o$, the current on the mirrored side must be the same.

$$\therefore I_{out} = I_B$$

$$R_{out} = r_{o_2} + r_{o_1} \left(1 + g_m r_{o_2} \right)$$

$$r_{o_2} = r_{o_1} = \frac{1}{\beta I_B} = \frac{1}{0.1 \text{ V}^{-1} \cdot 10 \mu\text{A}} \\ \approx 1 \text{ M}\Omega$$

$$g_m = \frac{2 \cdot I_B}{\Delta V_i} = \frac{2 \cdot 10 \mu\text{A}}{0.1 \text{ V}} \\ = 2 \times 10^{-4} \text{ S}$$

$$\Rightarrow R_{out} = 1 \text{ M}\Omega + 1 \text{ M}\Omega \left(1 + 2 \times 10^{-4} \cdot 1 \text{ M} \right)$$

$$\boxed{\approx 202 \text{ M}\Omega}$$

I_{out} and R_{out} will be the same
in both circuits.

- (b) For circuit in figure 2.a, determine the value of R_B that maximizes the output voltage swing.

$$V_{out \min} = 2\Delta V \text{ & } V_{out \max} = \text{undefined}$$

\Rightarrow We want a value of R_B that satisfies the minimum output swing, and assume V_{DD} has enough headroom for the maximum half of the swing.

$$\Rightarrow V_{ds_0} = V_{gs_0} - V_T \Rightarrow 0.1 = V_{g_0} - 0.5 \Rightarrow V_{g_0} = 0.6V$$

$$\Rightarrow V_{ds_2} = V_{gs_2} - V_T \Rightarrow V_{g_2} = 0.1V + 0.1V + 0.5V = 0.7V$$

$$\Rightarrow V_{g_0} = V_{g_1} = V_{ds_3} \Rightarrow V_{R_B} = V_{g_2} - V_{ds_3}$$

$$\Rightarrow V_{R_B} = I_B \cdot R_B = V_{g_2} - V_{ds_3} = 0.7V - 0.6V = I_B \cdot R_B$$

$$\Rightarrow R_B = \frac{0.1V}{10 \mu A}$$

$$\therefore R_B = 10 k\Omega$$

- (c) If I_B is reduced by four times ($I'_B = 1/4 \times I_B$), does the circuit in "a" still function? Explain.

No. Before reducing the current, we are precisely at one ΔV between G_0 and G_2 , which is required for saturation. With a reduced current, the change in $V_{g2,3}$ will not scale the same as the change in $V_{g0,1}$, due to the fact that R_B^+ drops more than R_B^- . With a reduction of I_B by $1/4$, we have all $\Delta V \rightarrow \frac{1}{2} \Delta V$, but with different gate voltages, such that $M_{2,3}$ will not be in saturation.

- (d) Size M_9 such that the output voltage swing is maximized. Determine the size of M_9 , $(W/L)_9$, in terms of the size of other transistors.

M_8 & M_6 equally sized with the

same current. $\Rightarrow \Delta V_8 = \Delta V_6$

$$I_{D_9} = I_{D_6}$$

$$\Rightarrow k' \left(\frac{w}{l}\right)_9 (\Delta V_9)^2 = k' \left(\frac{w}{l}\right)_6 (\Delta V_6)^2$$

$$\Rightarrow \frac{w_9}{w_6} = \frac{(\Delta V_6)^2}{(\Delta V_9)^2} = \frac{0.1}{0.2}$$

$$= \frac{1}{5}$$

$$\therefore w_9 = \frac{1}{5} w_6$$

- (e) If I_B is reduced by four times ($I'_B = 1/4 \times I_B$), does the circuit in "b" still function? Explain.

This circuit will still operate as it was intended to. The biasing I_B current is forced down M_9 , M_7 , and M_5 . The mirror copies this current to force it down M_6 and M_4 . In this circuit, the bias voltages are set by the current source, and not the voltage drop across a resistor. This means the circuit will self-adjust the bias voltages independent of I_B 's value.

- (f) If the ideal current sources need a minimum of 200mV voltage headroom to operate, determine the minimum required V_{DD} for the two circuits in figure 2.

We need to have a minimum V_{DD} of the gate voltage at $M_{8/9}$, which has already been calculated, and is indicated on the schematic, and the additional 200 mV.

$$\Rightarrow V_{g_{8/9}} + 200 \text{ mV} = 1.3 \text{ V} + 0.2 \text{ V}$$

$$V_{DD \min} = 1.5 \text{ V}$$

Problem 3 - Differential Amplifiers

Consider the amplifier shown in figure 3. Assume $\lambda \neq 0$.


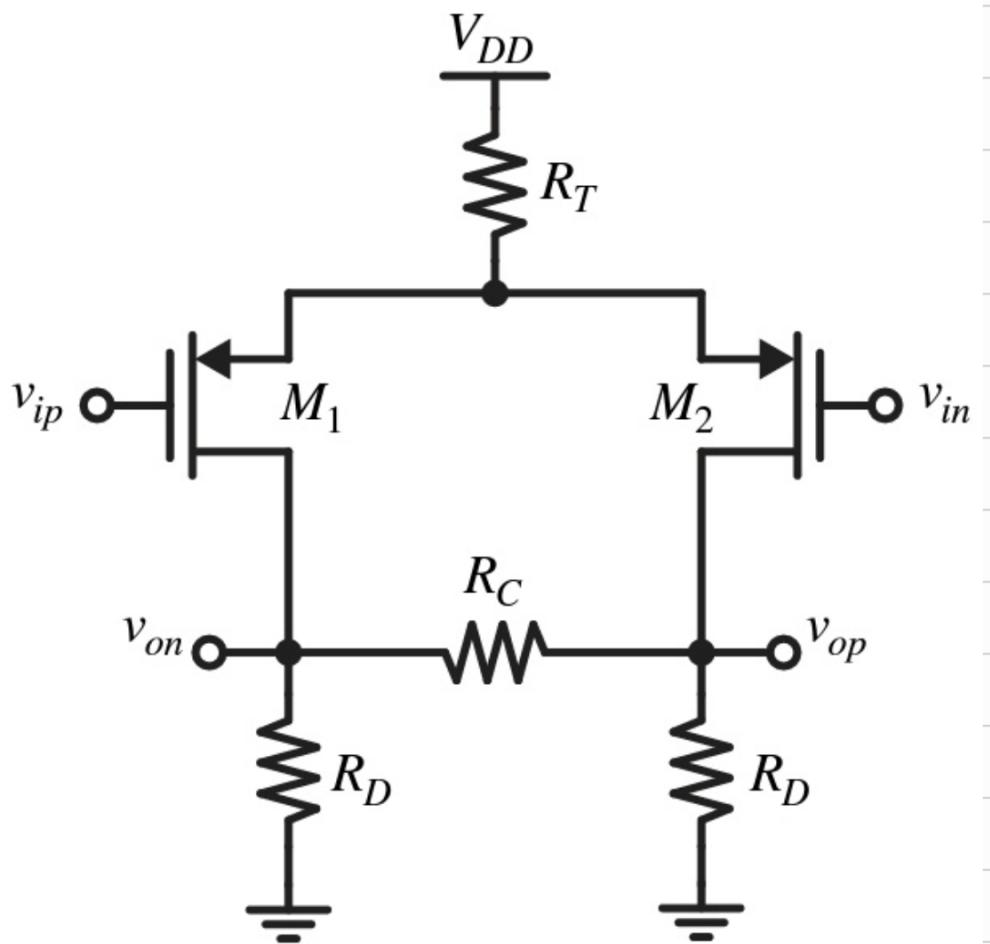


Figure 3: Diff. Amp

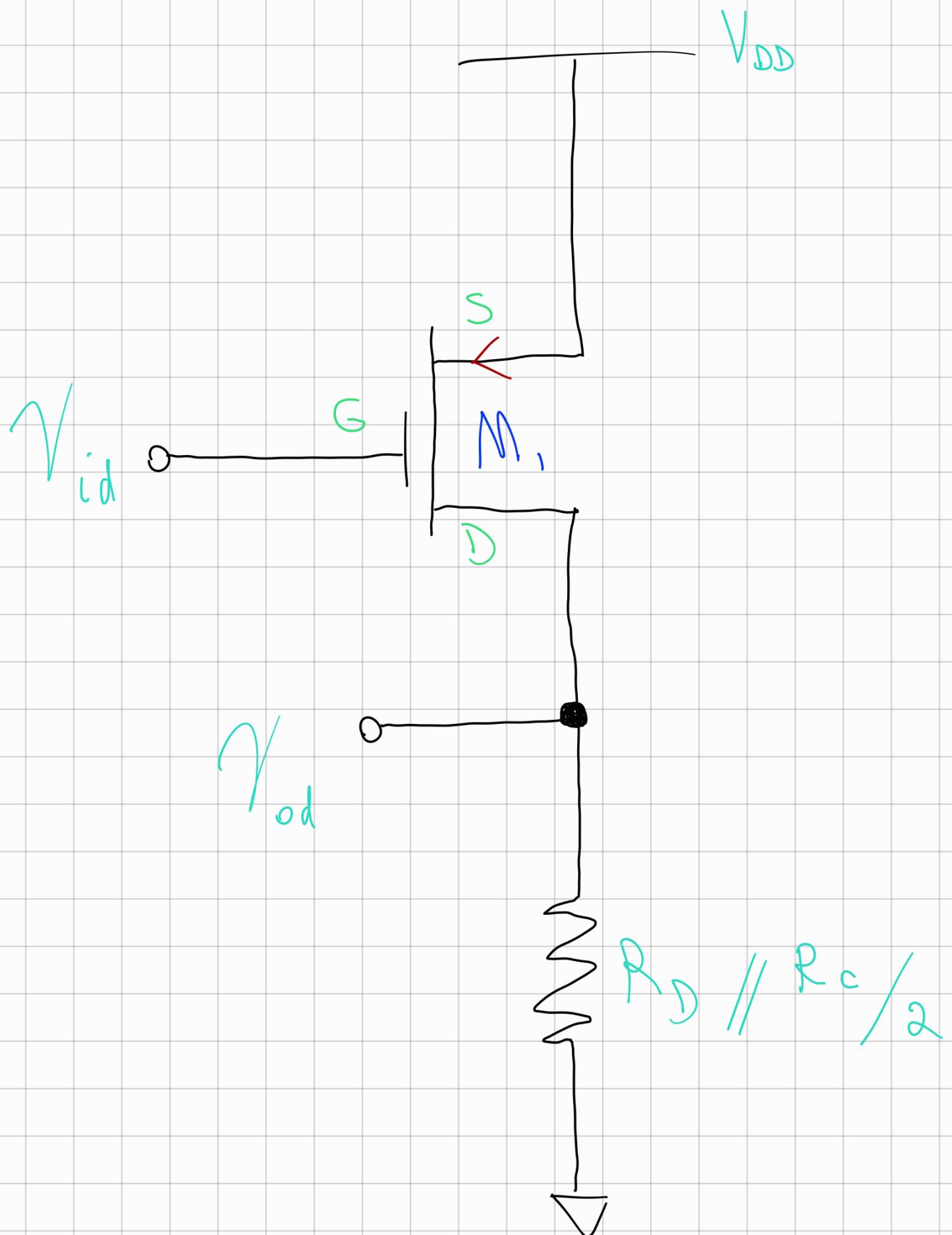(a) Draw the differential mode half circuit.



(b) Derive the symbolic differential gain of the circuit.

Gain of CS amp w/ m₀ degeneration :- $g_m \left(r_o \parallel R_D \parallel \frac{R_c}{2} \right)$

$$V_{od} = V_{op} - V_{on}$$

$$= + g_m \left(r_o \parallel R_D \parallel \frac{R_c}{2} \right) \cdot \frac{V_{ip}}{2}$$


$$- \left[- g_m \left(r_o \parallel R_D \parallel \frac{R_c}{2} \right) \cdot \frac{V_{in}}{2} \right]$$

$$= g_m \left(r_o \parallel R_D \parallel \frac{R_c}{2} \right) \left[\frac{V_{ip}}{2} + \frac{V_{in}}{2} \right]$$

* Note that : $V_{id} = \frac{V_{ip}}{2} - \left(-\frac{V_{in}}{2} \right) = \frac{V_{ip}}{2} + \frac{V_{in}}{2}$

$$\therefore \frac{V_{od}}{V_{id}} = g_m \left(r_o \parallel R_D \parallel \frac{R_c}{2} \right)$$

(c) Draw the common mode half circuit.

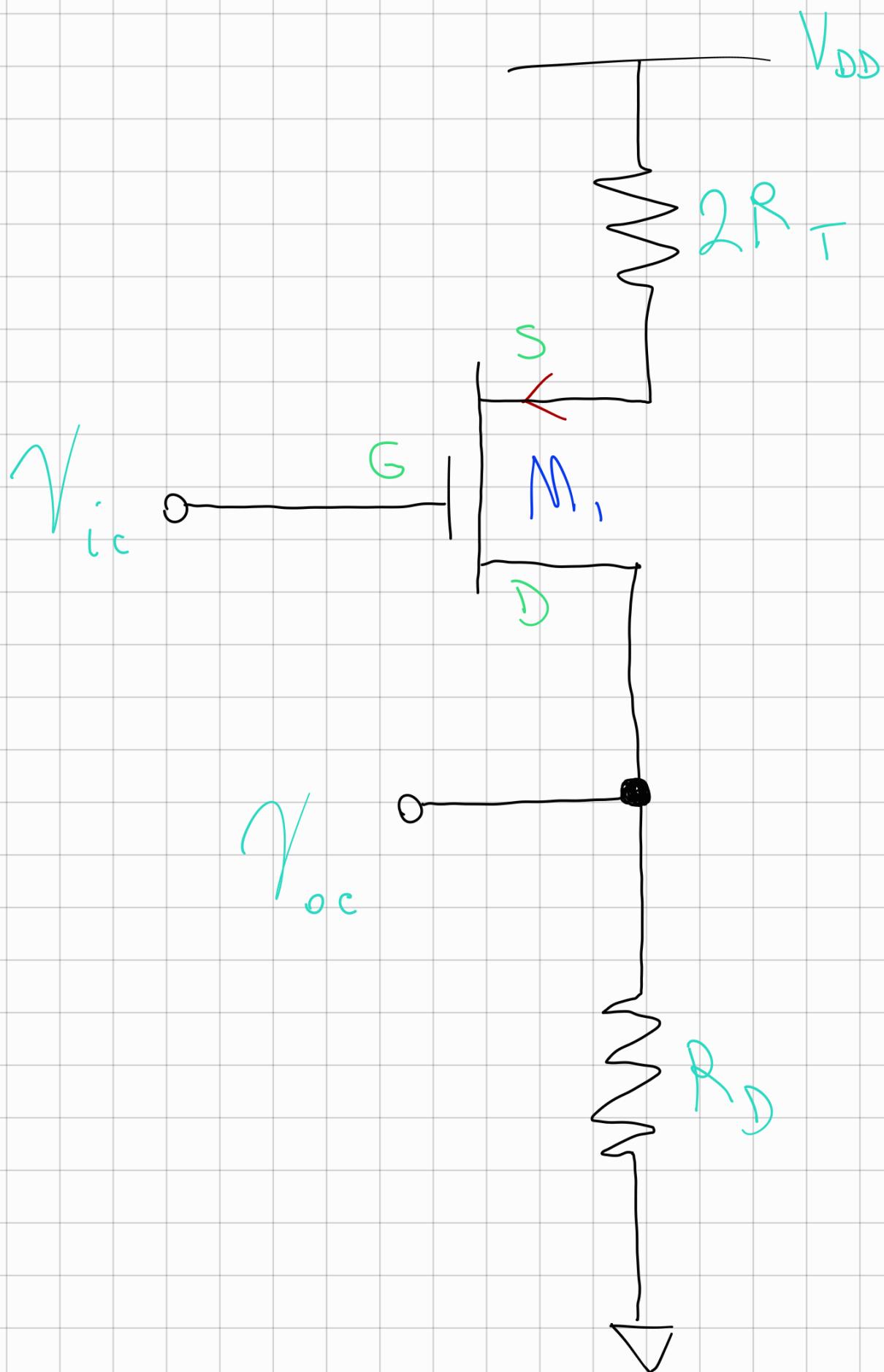

(d) Derive a symbolic expression for the common mode gain of the circuit.

Now we have a CS amplifier with source degeneration. The derivation for the gain will be the same process as the previous part, but with the appropriate gain expression

From lecture slides:

$$G_m \approx \frac{g_m}{1 + g_m R_S}$$

$$(*R_s = 2R_T)$$

$$\begin{aligned} R_{out} &= R_D \parallel R_{th,d} = R_D \parallel r_o + R_S + g_m R_S \\ &= R_D \parallel r_o + 2R_T + g_m 2R_T \end{aligned}$$

$$= R_D (r_o + 2R_T + g_m 2R_T)$$


$$R_D + r_o + 2R_T + 2g_m R_T$$

$$\Rightarrow G_m R_{\text{out}} = \frac{g_m R_o (r_o + 2R_T + 2g_m R_T)}{(1 + g_m R_o) R_o + r_o + 2R_T + 2g_m R_T}$$


$$\Rightarrow V_{oc} = -V_{on} - V_{op}$$

$$\therefore \frac{V_{oc}}{V_{ic}} = - \left[\frac{g_m R_o (r_o + 2R_T + 2g_m R_T)}{(1 + 2g_m R_T) R_o + r_o + 2R_T + 2g_m R_T} \right]$$

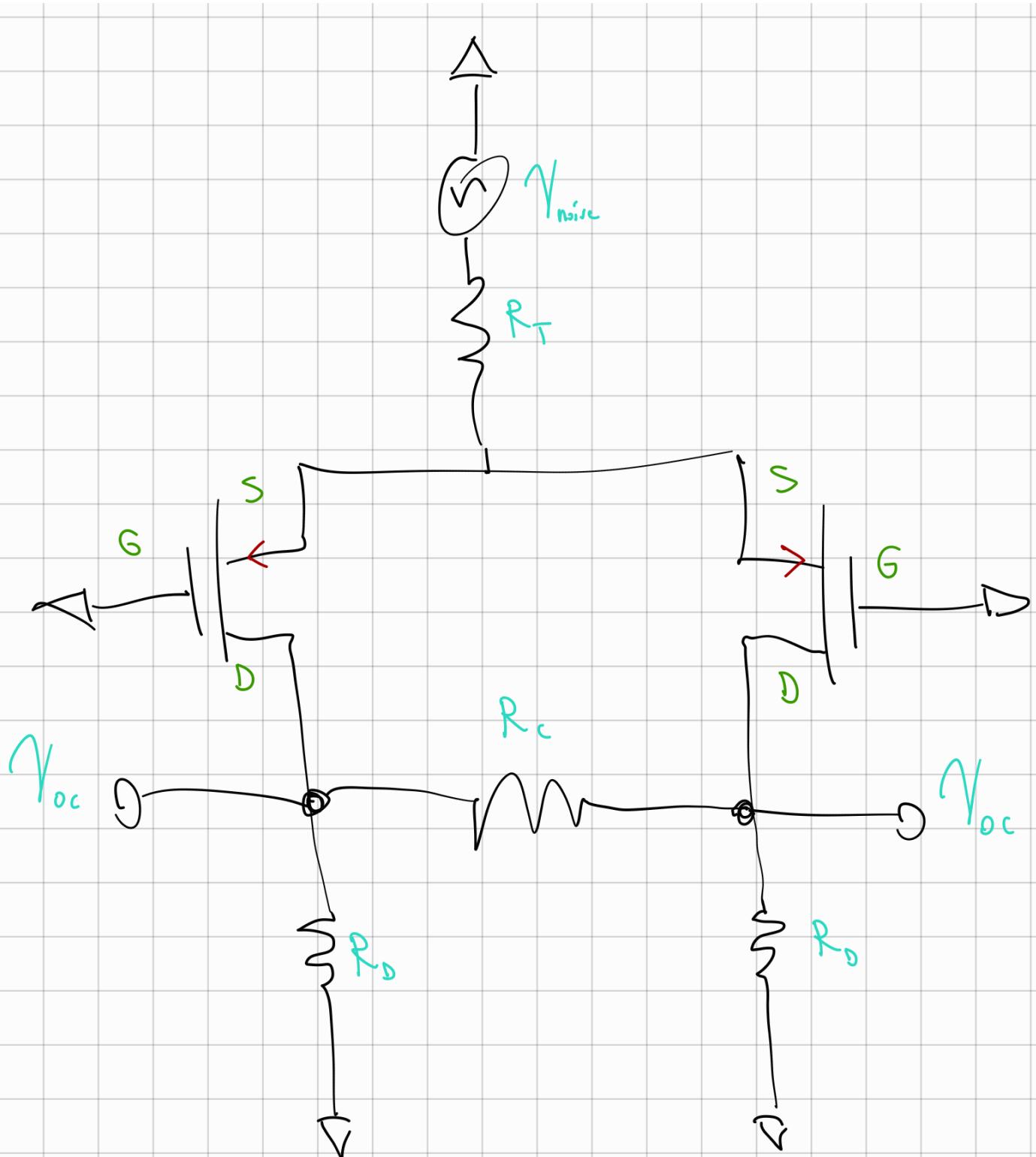- (e) Suppose the V_{DD} is taken from a noisy voltage source. Find the small signal gain for the supply noise to the common mode output. You may assume that the supply noise is a small signal AC perturbation at the V_{DD} terminal. You can refer to the figure below to see how the supply noise is modeled.



Small-signal Half-circuit

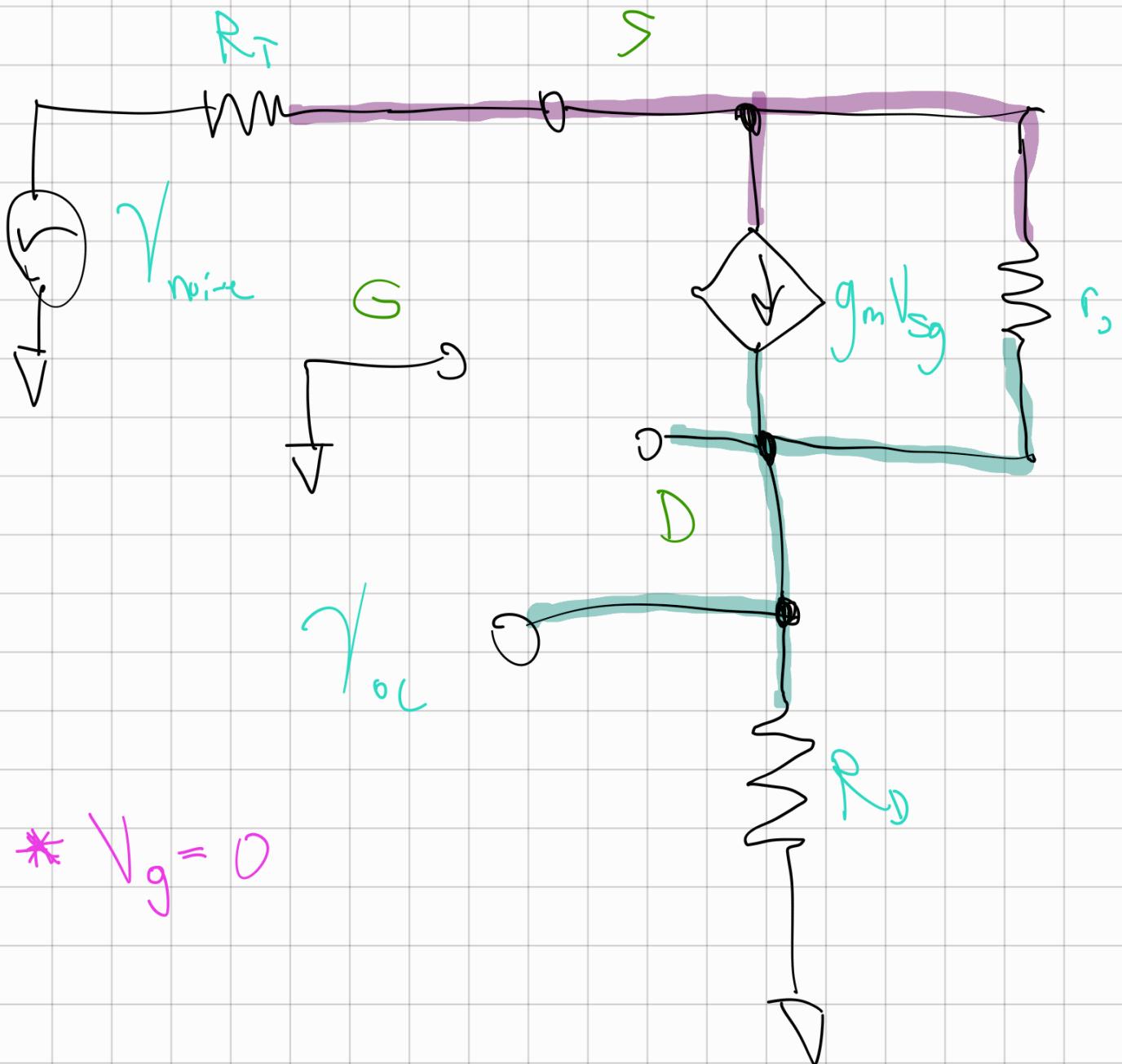

$$* V_g = 0$$

KCL Analysis: $\frac{V_{oc}}{R_D} + \frac{V_{oc}}{r_o} = g_m V_{sg}$

$$\Rightarrow V_{oc} \left(\frac{1}{R_D} + \frac{1}{r_o} \right) = g_m V_s$$

(1)

$$\frac{V_s - V_{\text{noise}}}{R_T} + \frac{V_s - V_{\text{oc}}}{r_o} + g_m V_s = 0$$

$$\Rightarrow V_s \left(\frac{1}{R_T} + \frac{1}{r_o} + g_m \right) = \frac{V_{\text{oc}}}{r_o} + \frac{V_{\text{noise}}}{R_T}$$

$$\Rightarrow V_s = \left(r_o \parallel R_T \parallel \frac{1}{g_m} \right) \cdot r_o \cdot V_{\text{oc}} + \frac{V_{\text{noise}}}{R_T} \quad (2)$$

(2) into (1) ↗

$$V_{\text{oc}} \left(\frac{1}{R_D} + \frac{1}{r_o} \right) = g_m \left[\left(r_o \parallel R_T \parallel \frac{1}{g_m} \right) \cdot r_o \cdot V_{\text{oc}} + \frac{V_{\text{noise}}}{R_T} \right]$$

$$V_{\text{oc}} = V_{\text{oc}} \left(r_o \parallel R_D \right) \left(r_o \parallel R_T \parallel \frac{1}{g_m} \right) g_m r_o + V_{\text{noise}} \left(\frac{r_o \parallel R_D}{R_T} \right)$$

$$V_{\text{oc}} \left(1 - \left(r_o \parallel R_D \right) \left(r_o \parallel R_T \parallel \frac{1}{g_m} \right) g_m r_o \right) = V_{\text{noise}} \left(\frac{r_o \parallel R_D}{R_T} \right)$$

$$\begin{aligned}
 & \frac{\sqrt{V_{o.c}}}{\sqrt{V_{noise}}} = \frac{\frac{r_o \parallel R_D}{R_T}}{1 - \left(r_o \parallel R_D \right) \left(r_o \parallel R_T \parallel \frac{1}{g_m} \right) g_m r_o} \\
 & = \frac{\frac{1}{R_T}}{\frac{1}{r_o \parallel R_D} - g_m r_o \left(r_o \parallel R_T \parallel \frac{1}{g_m} \right)} \\
 & = \frac{\frac{1}{R_T}}{\frac{r_o + R_D}{r_o R_D} - g_m r_o \left(\frac{1}{r_o} + \frac{1}{R_T} + g_m \right)} \\
 & = \frac{\frac{1}{R_T}}{\frac{r_o + R_D}{r_o R_D} - g_m r_o \left(\frac{r_o + R_T + g_m r_o R_T}{r_o R_T} \right)}
 \end{aligned}$$

$$= \frac{\frac{1}{R_T}}{\frac{r_o + R_D}{r_o R_D} - \frac{g_m r_o^2 R_T}{r_o + R_T + g_m r_o R_T}}$$

$$= \frac{\frac{1}{R_T}}{\frac{(r_o + R_D)(r_o + R_T + g_m r_o R_T) - r_o R_D(g_m r_o^2 R_T)}{r_o R_D(r_o + R_T + g_m r_o R_T)}}$$

$$= \frac{R_T}{\left[(r_o + R_D)(r_o + R_T + g_m r_o R_T) - r_o R_D(g_m r_o^2 R_T) \right]}$$

$$= \frac{\frac{r_o R_o}{R_T} \left(r_o + R_T + g_m r_o R_T \right)}{\left(r_o + R_D \right) \left(r_o + R_T + g_m r_o R_T \right) - r_o R_D \left(g_m r_o^2 R_T \right)}$$

~~$r_o R_T$~~

• $\frac{\gamma_{o.c}}{\gamma_{noise}} = \frac{\frac{r_o R_o}{R_T} \left(r_o + R_T + g_m r_o R_T \right)}{\left(r_o + R_D \right) \left(r_o + R_T + g_m r_o R_T \right) - r_o R_D \left(g_m r_o^2 R_T \right)}$