

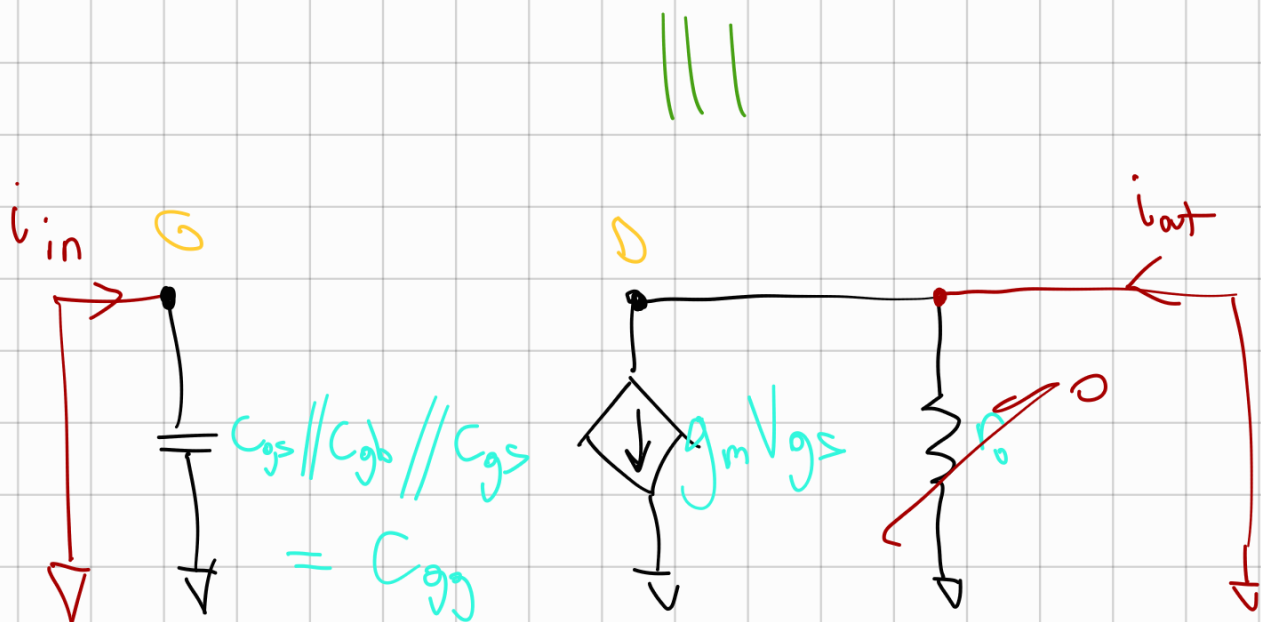


# Small-signal Model

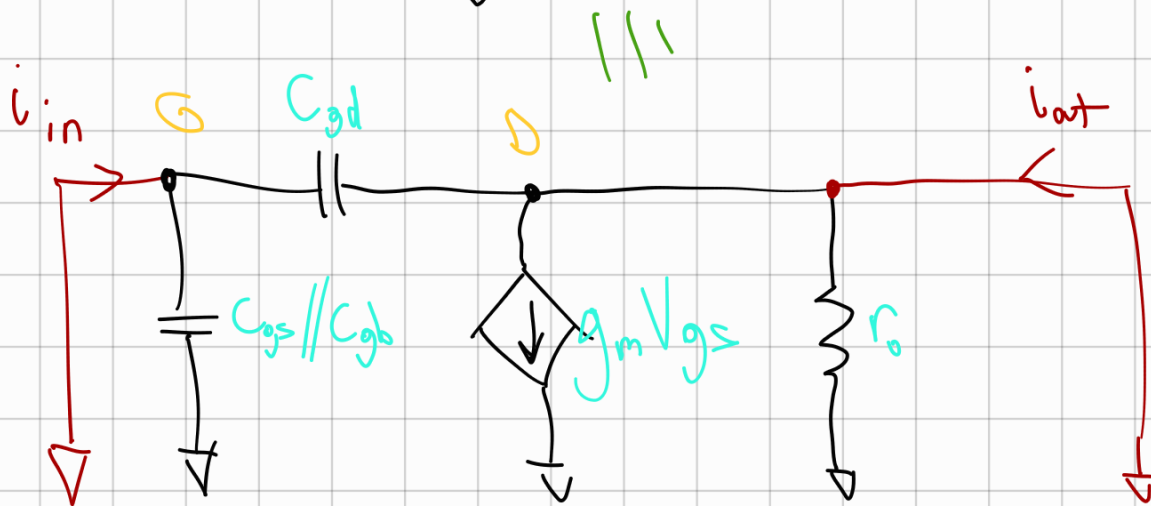

# Simplified Small-signal Model

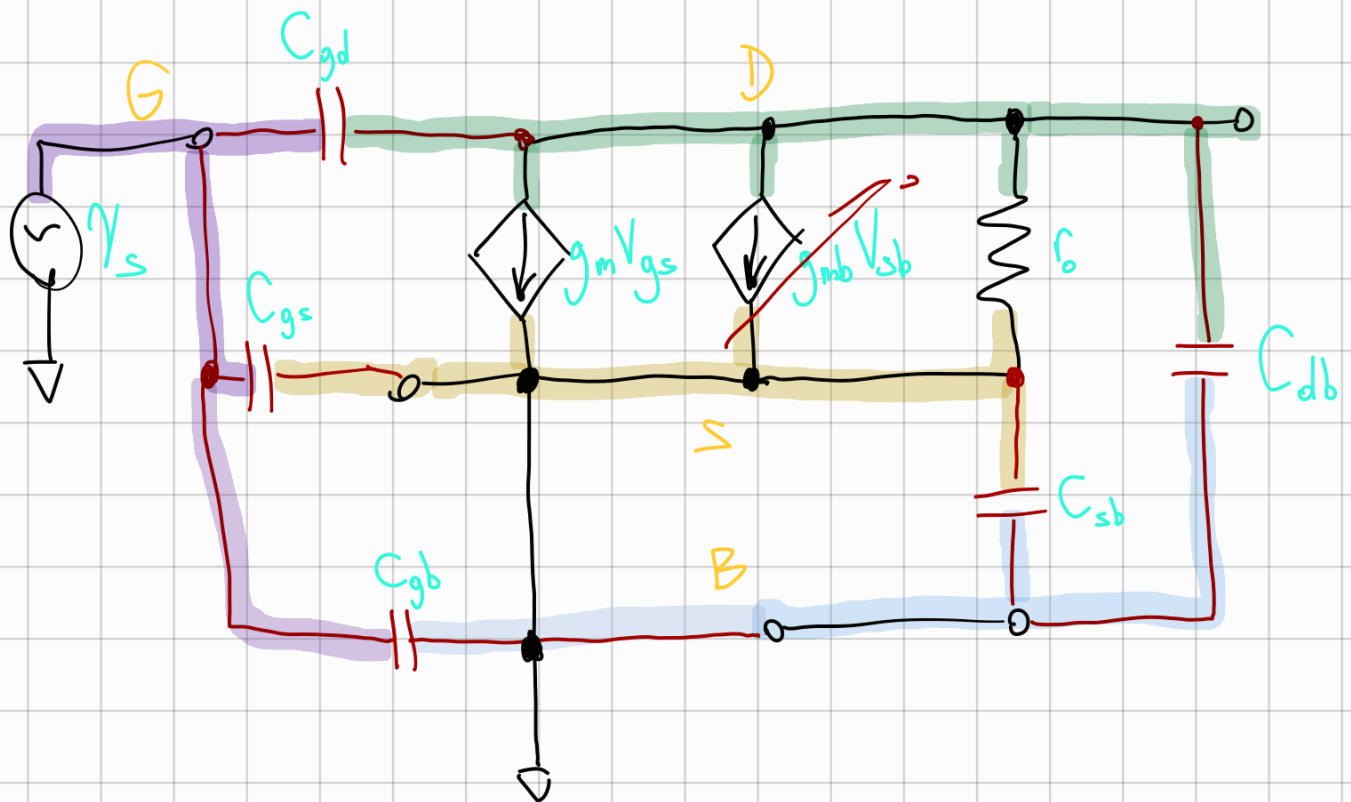

$$* \quad i_{in} = \frac{V_g}{sC_{gg}} \quad \& \quad i_{out} = g_m V_g$$

$$\Rightarrow \frac{i_{out}}{i_{in}} = \frac{g_m \cancel{V_g}}{\frac{\cancel{V_g}}{sC_{gg}}} = \frac{g_m}{sC_{gg}}$$

$$\Rightarrow \left| \frac{g_m}{sC_{gg}} \right| = \frac{g_m}{2\pi f C_{gg}} = 1 = f_T$$



# $g_m/I_D$ Systematic Design Methodology

- 1) From the design specs and constraints, determine  $g_m$ .
- 2) Pick  $L$ :
  - (a) Short-channel  $\rightarrow$  high  $f_T$ , small area
  - (b) Long-channel  $\rightarrow$  high  $A_v$ , large area
- 3) Pick  $g_m/I_D$ :
  - (a) Large  $g_m/I_D \rightarrow$  Low power, high  $A_v$
  - (b) Small  $g_m/I_D \rightarrow$  High  $f_T$ , small area
- 4) Determine  $I_D$  using steps 1 and 3.
- 5) Determine  $W$  using  $I_D/w$  denormalization.

$$g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \quad r_o = \frac{1}{\lambda I_D}$$

$$A = g_m \cdot r_o = \frac{1}{\lambda} \sqrt{\frac{2\mu C_{ox} \frac{W}{L}}{I_D}}$$