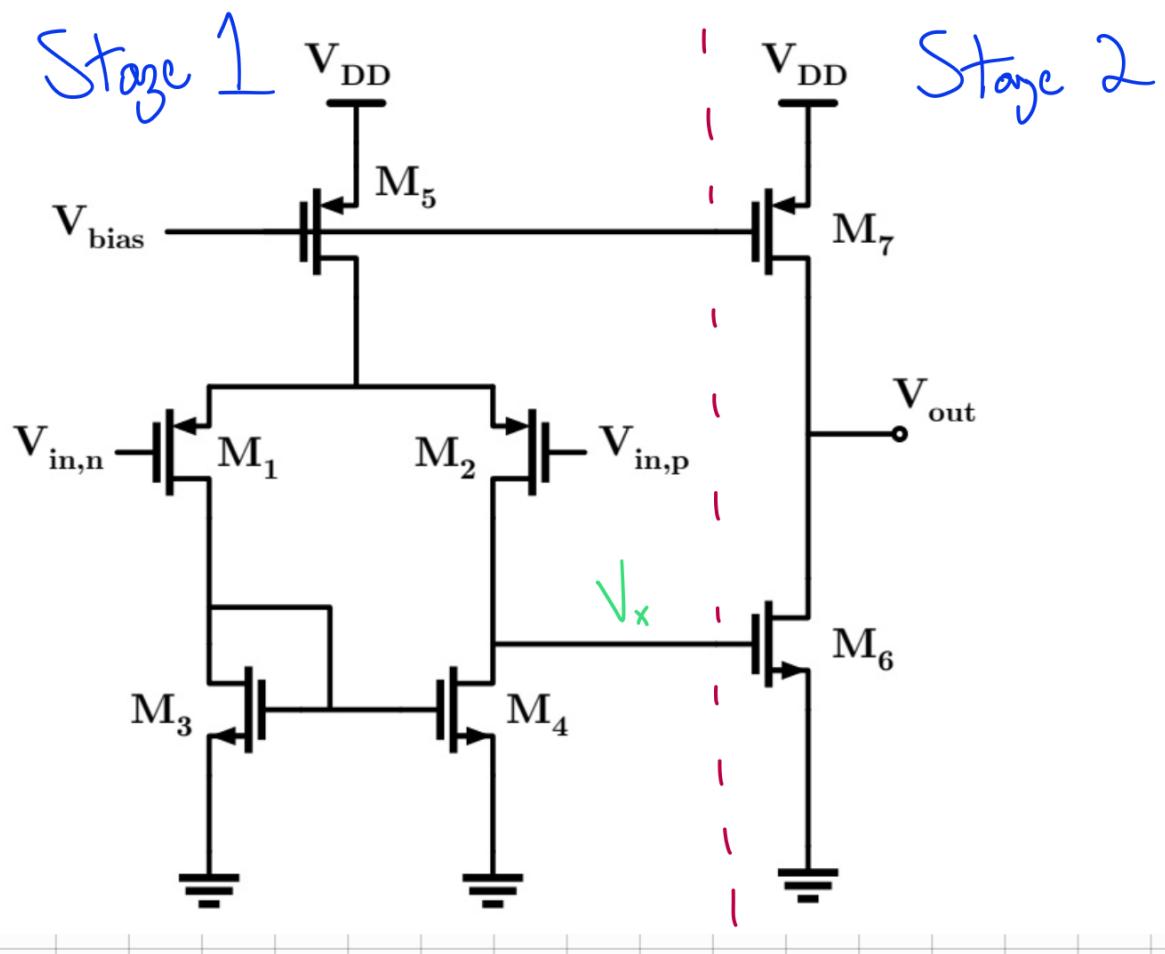


# Problem 1 - PSRR of the Two-Stage Amplifier


In this problem, we will calculate the PSRR+ of the workhorse two-stage amplifier. In such amplifiers, when  $V_{bias}$  is not created in a particular manner such that it tracks the changes in  $V_{DD}$ , we may experience a degraded PSRR+ performance. Express all your answers in terms of small-signal parameters of the devices ( $g_m$  and  $r_o$  of each transistor). Assume that symmetric transistors in the differential amplifier share the same small signal parameters.



(a) Calculate the differential mode gain of the circuit:  $A_{vd} = \frac{v_{out}}{v_{in,p} - v_{in,n}}$

$$\Rightarrow A_{vd} = \frac{\sqrt{X}}{\sqrt{v_{in,p}} - \sqrt{v_{in,n}}} \cdot \frac{v_{out}}{\sqrt{X}}$$

# Small-signal Model (Stage 1)

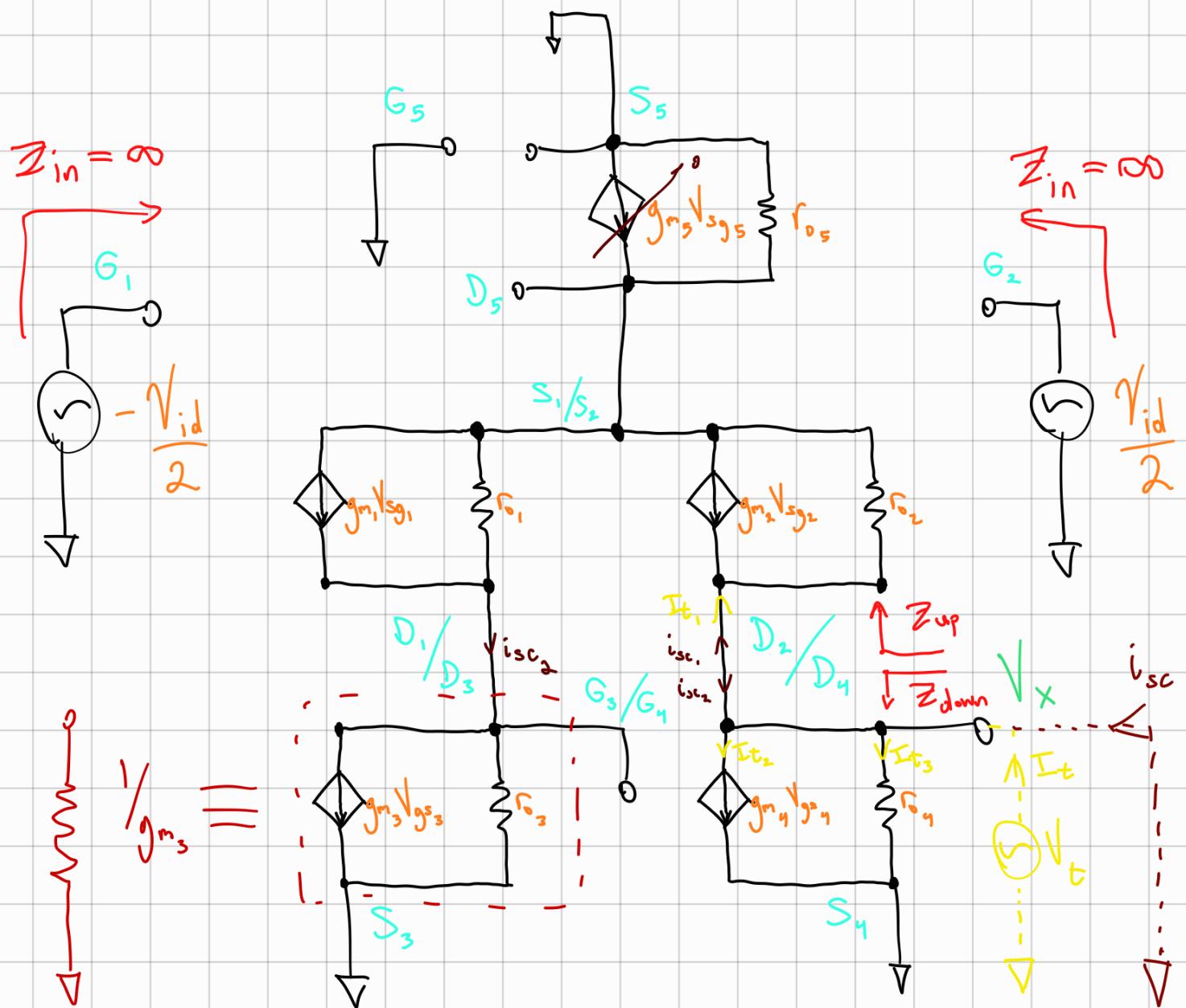

## Output Resistance

$$I_{t1} = \frac{V_t}{R_{th1}d_2}$$

$$I_{t2} = \frac{V_t}{r_{o3}}$$

$$I_{t3} = g_{m4}V_{gs4}$$

$$R_{th, d_2} = r_{o_2} \left( 1 + g_{m_2} R_s \right) + R_s$$

$$\Rightarrow R_s = \cancel{r_{o_2}} \parallel \frac{1}{g_{m_1}} + \frac{1}{g_{m_3}}$$

$$r_{o_2} \gg \frac{1}{g_{m_1}}$$

$$= \frac{1}{g_{m_1}} + \frac{1}{g_{m_3}} \quad \frac{1}{g_{m_3}} \text{ negligible}$$

$$\approx \frac{1}{g_{m_1}}$$

$$\Rightarrow R_{th, d_2} = r_{o_2} \left( 1 + \frac{g_{m_1}}{g_{m_2}} \right) + \frac{1}{g_{m_1}}$$

$* g_{m_1} = g_{m_2}$

$$= 2r_{o_2} + \frac{1}{g_{m_1}} \approx 0$$

$\therefore R_{th, d_2} \approx 2r_{o_2}$

$$\Rightarrow V_{O_3} = I_{t_1} \cdot \frac{1}{g_{m_3}} \Rightarrow I_{t_3} = g_{m_4} \cdot \frac{I_{t_1}}{g_{m_3}}$$

$$\Rightarrow I_t = I_{t_1} + I_{t_2} + I_{t_3}$$

$$= \frac{V_t}{2r_{o_2}} + \frac{V_t}{r_{o_4}} + I_{t_1} \left( \frac{g_{m_4}}{g_{m_3}} \right)$$

$$= V_t \left( \frac{1}{2r_{o_2}} + \frac{1}{r_{o_4}} + \frac{1}{2r_{o_2}} \right)$$

∴  $R_{out} = \frac{V_t}{I_t} = r_{o_2} \parallel r_{o_4}$

## Transconductance

For differential analysis,  $\gamma_{in,p} = \frac{\gamma_{id}}{2}$  &  $\gamma_{in,n} = -\frac{\gamma_{id}}{2}$

$$\Rightarrow i_{sc_1} = g_{m_1} \cdot \frac{\gamma_{id}}{2} = g_{m_2} \cdot \frac{\gamma_{id}}{2}$$



$$\begin{aligned}\Rightarrow V_{gs_1} &= 1/g_{m_3} \cdot g_{m_1} \cdot V_{sg_1} \\ &= \frac{g_{m_1}}{g_{m_3}} \cdot -\left(-\frac{\gamma_{id}}{2}\right) = \frac{\gamma_{id}}{2} \cdot \frac{g_{m_1}}{g_{m_3}}\end{aligned}$$

$$\Rightarrow i_{sc_2} = g_{m_3} V_{gs_1} = \frac{g_{m_3}}{g_{m_3}} \cdot \frac{\gamma_{id} \cdot g_{m_1}}{2}$$

$$\begin{aligned}\Rightarrow i_{sc} &= i_{sc_1} + i_{sc_2} = g_{m_1} \cdot \frac{\gamma_{id}}{2} + \frac{\gamma_{id} \cdot g_{m_1}}{2} \\ &= \gamma_{id} \left( \frac{g_{m_1}}{2} + \frac{g_{m_1}}{2} \right)\end{aligned}$$

$$\therefore i_{sc} = \gamma_{id} \cdot g_{m_1}$$

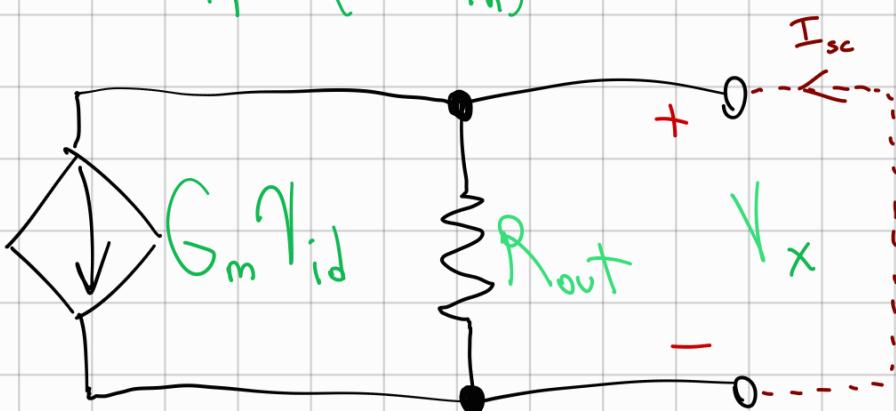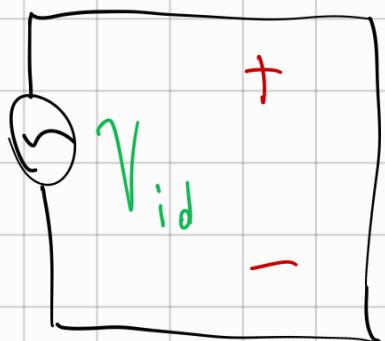Two-port Model \*  $\gamma_{in,p} - \{-\gamma_{in,n}\} = \gamma_{id}$




$$\Rightarrow I_{sc} = G_m V_{id} = g_{m1} V_{id} = i_{sc}$$

$$\Rightarrow G_m = g_{m1} \quad \& \quad R_{out} = r_{o2} \parallel r_{o4}$$

$$\Rightarrow V_x = -G_m V_{id} \cdot R_{out}$$

$$\Rightarrow \frac{V_x}{V_{id}} = -g_{m1} \cdot r_{o2} \parallel r_{o4}$$



## Small-signal Model (Stage 2)

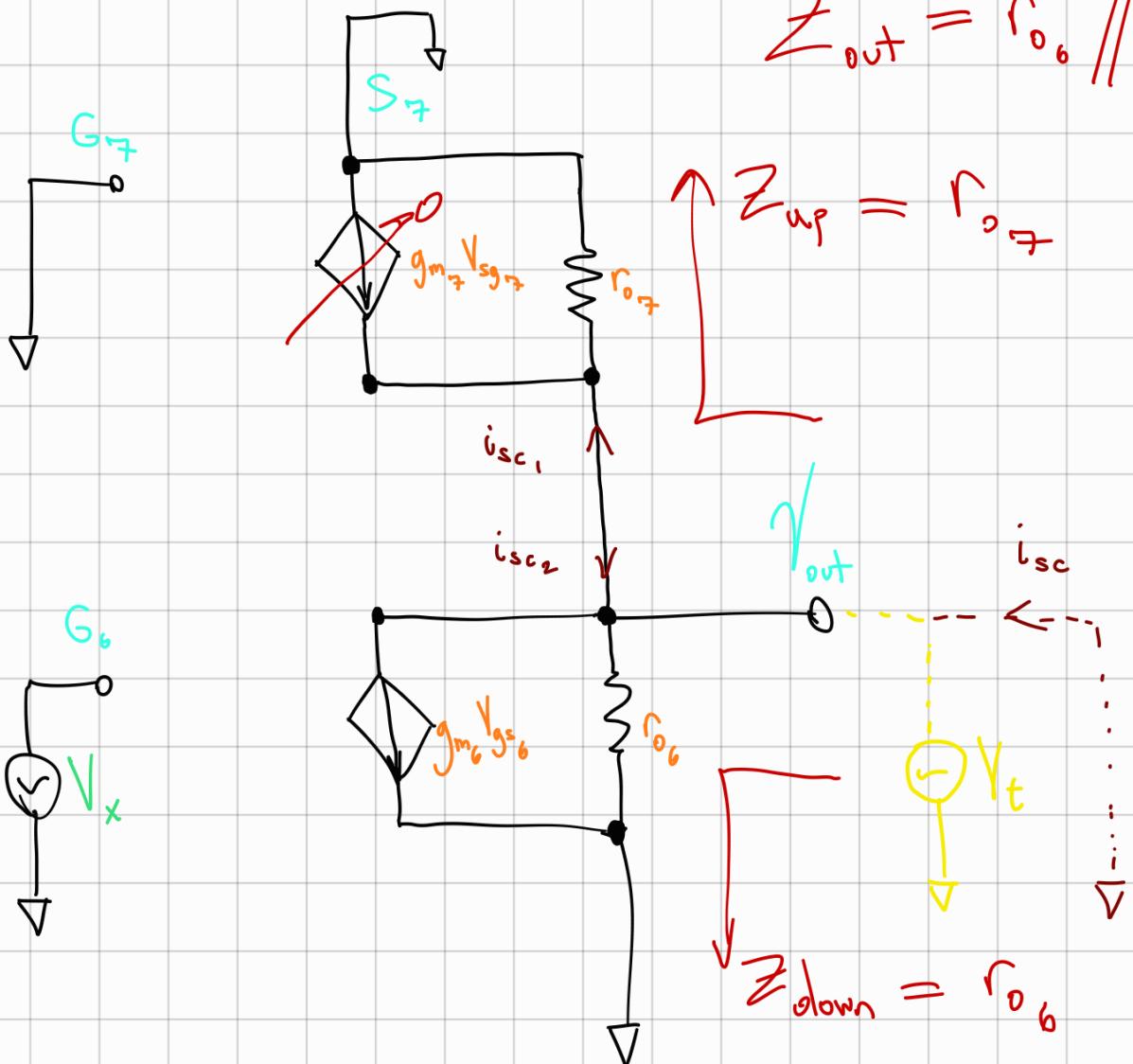

$$i_{sc1} = \frac{V_{out}}{r_{o_6}} + g_{m_6} V_x$$

$$i_{sc2} = \frac{V_{out}}{r_{o_7}} \Rightarrow i_{sc} = g_{m_6} V_x$$

## Two-port Model

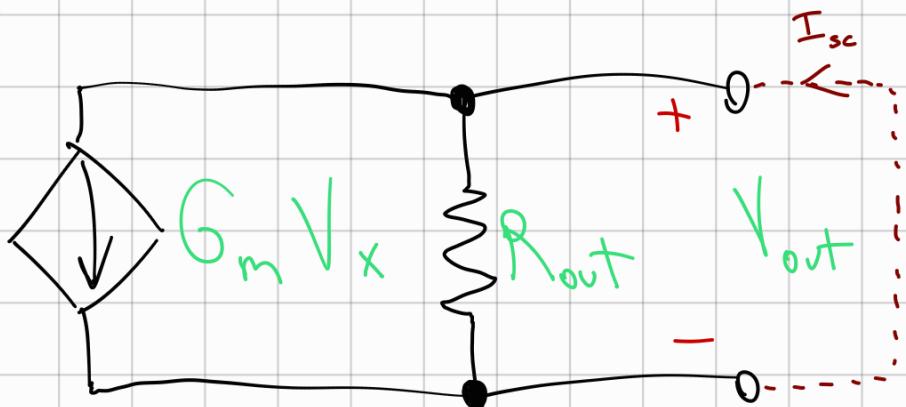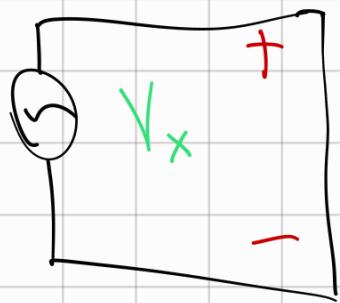


$$\Rightarrow I_{sc} = G_m V_x = g_{m_6} V_x = i_{sc}$$

$$\Rightarrow G_m = g_{m_6} \quad \& \quad R_{out} = r_{o_6} \parallel r_{o_7}$$

$$\Rightarrow V_{out} = -G_m V_x \cdot R_{out}$$

$$\Rightarrow \frac{V_{out}}{V_x} = -g_{m_6} \cdot r_{o_6} \parallel r_{o_7}$$

## Full Two-port Model

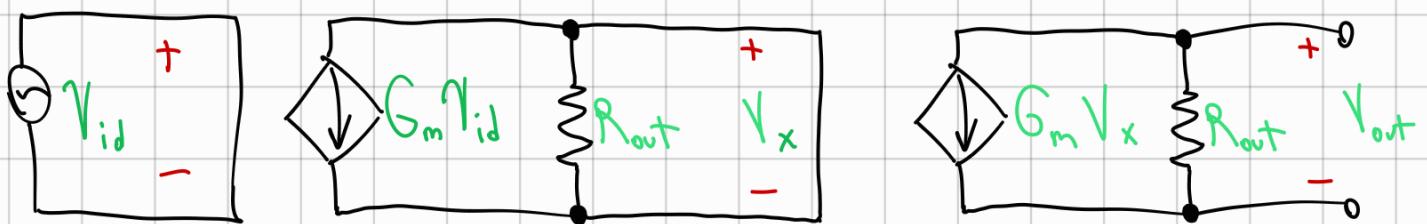

$$\Rightarrow A_{V_d} = \frac{V_x}{V_{in,p} - V_{in,n}} \cdot \frac{V_{out}}{V_x}$$


$$= \frac{V_x}{V_{id}} \cdot \frac{V_{out}}{V_x}$$


$$= (-g_{m1} \cdot r_{o2} \parallel r_{on}) \left( -g_{m6} \cdot r_{o6} \parallel r_{o7} \right)$$

$\therefore A_{V_d} = g_{m1} g_{m6} \left( r_{o2} \parallel r_{on} \right) \left( r_{o6} \parallel r_{o7} \right)$

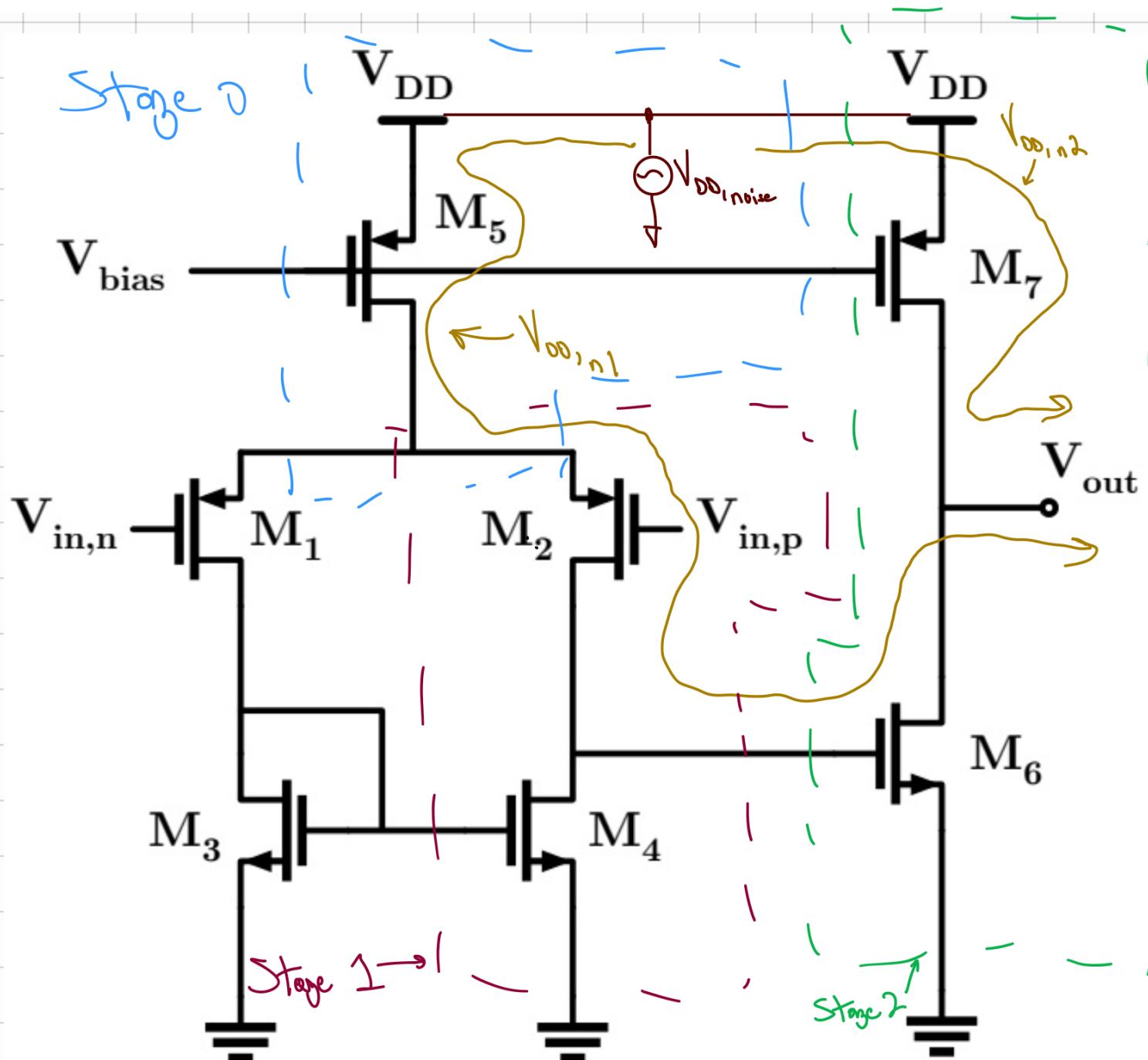- (b) Now consider that  $V_{DD}$  has a noise associated with it, i.e. a small-signal AC source of  $v_{dd,n}$  in series with the DC  $V_{DD}$ . Calculate the gain from  $v_{dd,n}$  to the output,  $A_{vp+} = \frac{v_{out}}{v_{dd,n}}$ .

Hints: Noise has two paths to reach the output: through  $M_7$  and through  $M_5$ . Consider them separately and add them up with the correct sign later. When considering the path through  $M_5$ , notice that  $M_2$  is acting as a common gate amplifier. Recall from our discussions that  $V_{DS}$  values of  $M_3$  and  $M_4$  track each other in common mode excitations.



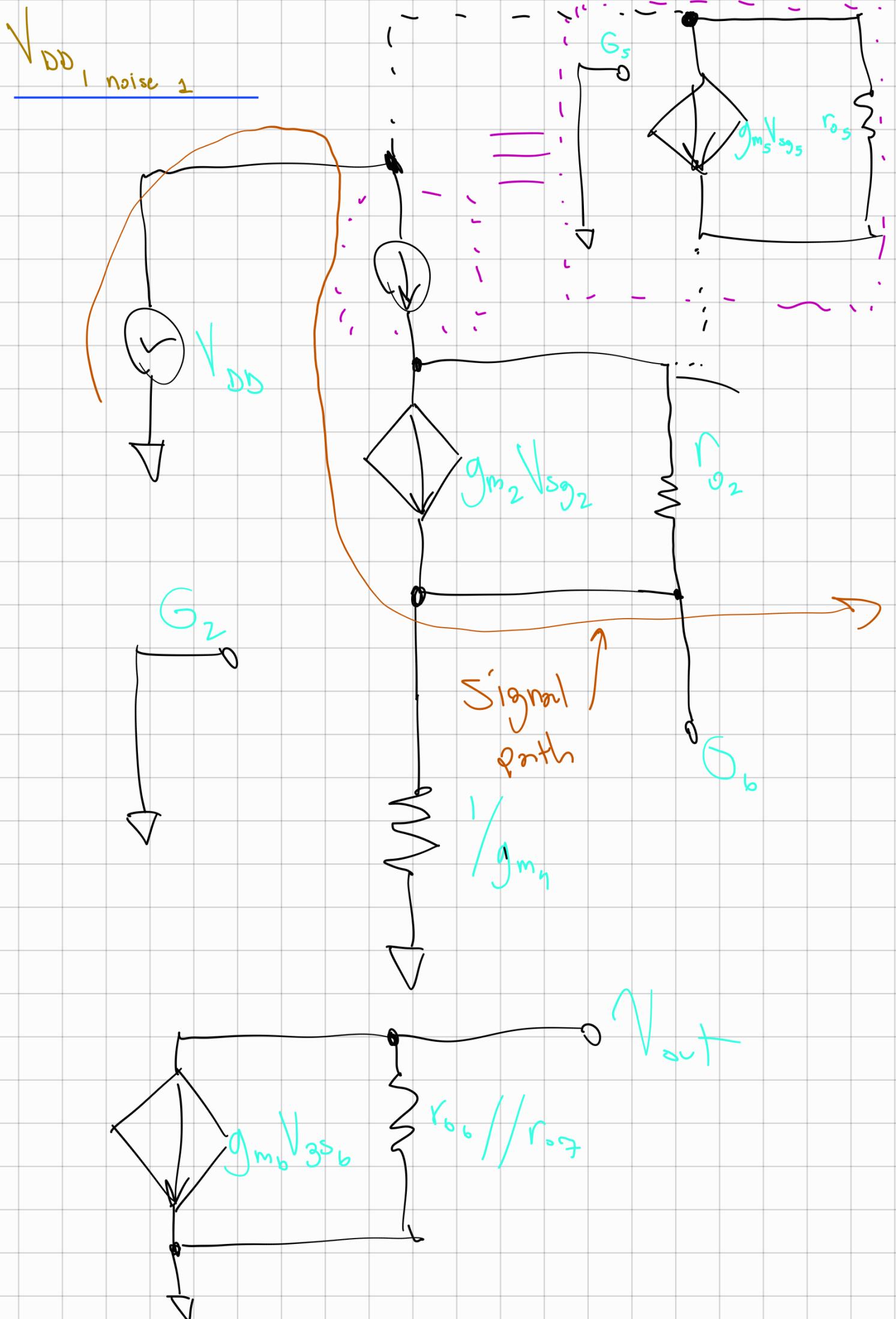

$$A_{V_0} = g_{m_5} \cdot \left( r_{o_5} \parallel \frac{1}{g_{m_2}} \right)$$


$$A_{V_1} = g_{m_2} \cdot \left( r_{o_2} \parallel \frac{1}{g_{m_3}} \right)$$

$$A_{V_2} = -g_{m_6} \cdot \left( r_{o_6} \parallel r_{o_7} \right)$$

\* Assume  $r_{o_5}, r_{o_2} \gg g_{m_2}, g_{m_3}$

$$A_V = -\cancel{g_{m_2} g_{m_5} g_{m_6}} \cdot \frac{1}{\cancel{g_{m_2} g_{m_3}}} \cdot r_{o_6} \parallel r_{o_7}$$

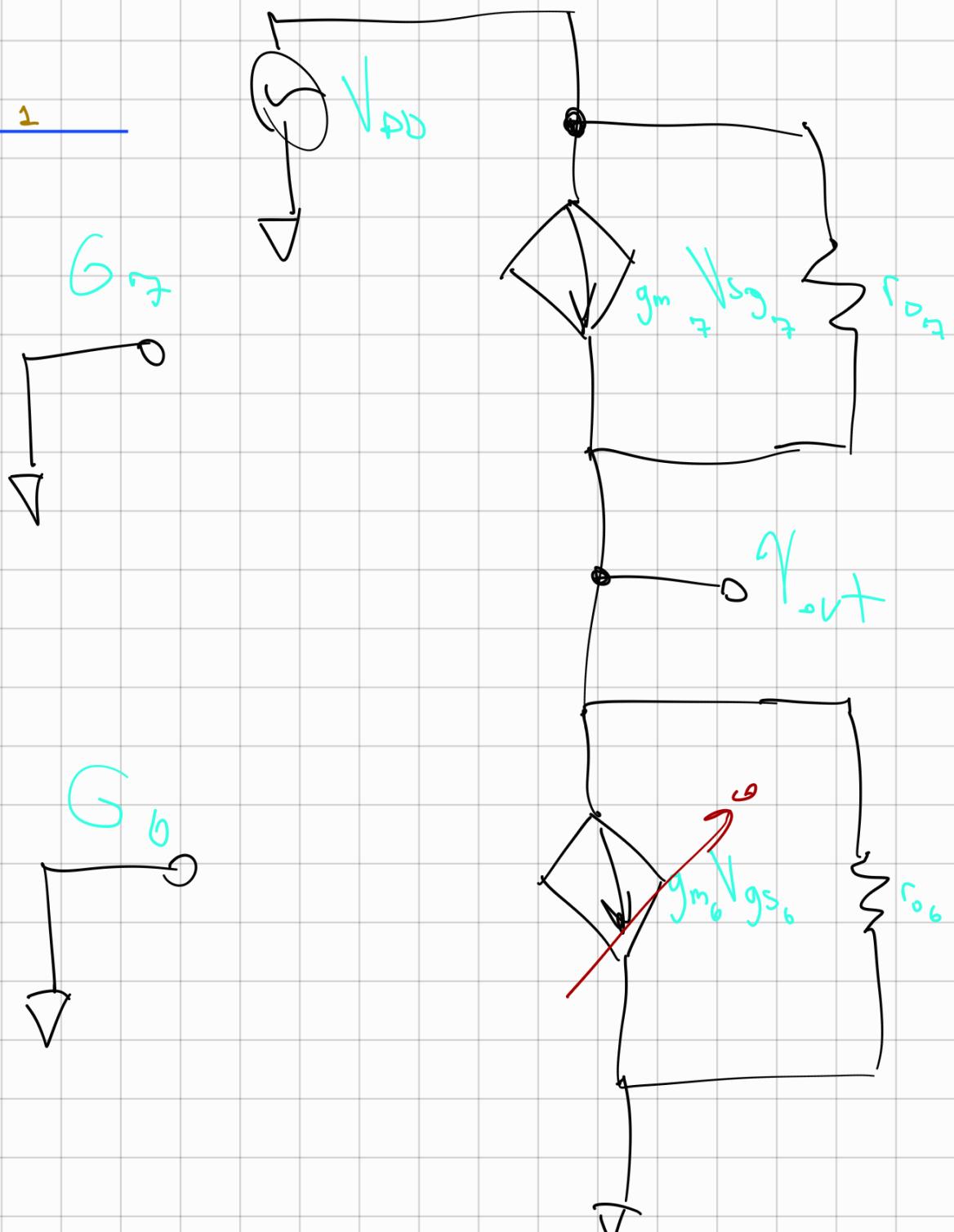∴  $A_{V_{cm_1}} = -\frac{g_{m_5} g_{m_6}}{g_{m_3}} \cdot r_{o_6} \parallel r_{o_7}$



$$\Rightarrow A_{V_{CM2}} = g_{m7} \cdot r_{o7} // r_{o6}$$

$$\Rightarrow A_{V_{CM}} = A_{V_{CM_1}} + A_{V_{CM_2}}$$

$$= \frac{-g_{m_5} g_{m_6}}{g_{m_7}} \left( r_{o_6} // r_{o_7} \right) + g_{m_7} \left( r_{o_7} // r_{o_6} \right)$$

• •

$$A_{V_{f+}} = \left[ \frac{\left( -g_{m_5} g_{m_6} \right)}{g_{m_7}} + g_{m_7} \right] \circ r_{o_7} // r_{o_6}$$

(c) Using your previous results, what is the PSRR+ of this amplifier?


$$\text{PSRR}^+ = \left| \frac{A_{V_{DM}}}{A_{V_P^+}} \right|$$

$$= \frac{g_{m_1} g_{m_6} \left( r_{o_2} \parallel r_{o_4} \right) \left( r_{o_6} \parallel r_{o_7} \right)}{\left( -\frac{g_{m_5} g_{m_6}}{g_{m_4}} + g_{m_7} \cdot r_{o_7} \parallel r_{o_6} \right)}$$

D. PSRR<sup>+</sup> =  $\frac{\left( -g_{m_5} g_{m_6} \right)}{g_{m_4}} + g_{m_7} \cdot r_{o_2} \parallel r_{o_4}$
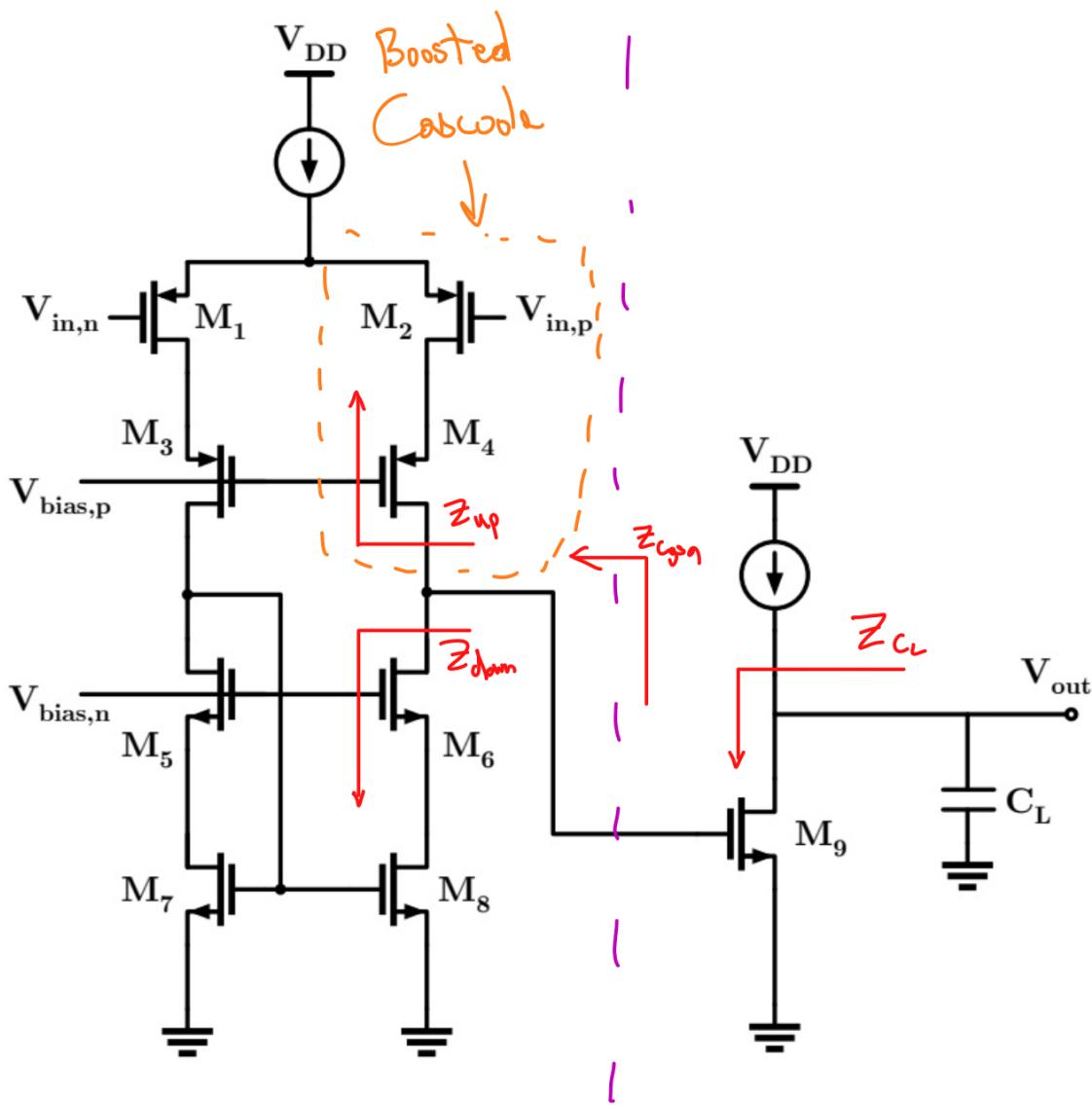
# Problem 2 - Miller Compensation of Two-Stage Amplifiers

There are applications we want a really high DC gain, and in those cases the workhorse amplifier in Problem 1 doesn't always cut it. One idea to improve the gain is to make the first stage gain higher by moving to the "telescopic cascode" topology, which is a power efficient topology that provides a high gain. In this problem we will analyze the Miller compensation of this two-stage amplifier. Assume that symmetric transistors in the differential amplifier share the same small signal parameters.



We want to use this amplifier in a feedback loop with feedback factor  $\beta = 1/2$ . The load capacitor  $C_L$  is very large ( $C_L > g_m r_o C_{gs}$ ). Other than  $C_L$ , only consider the  $C_{gs}$  of the transistors, ignore any other capacitance. You may approximate  $g_m r_o \gg 1$  wherever appropriate. Assume all current sources are ideal.

$$\text{Boosted Cascode } R_{out} \approx g_m r_o^2$$

- (a) Find the DC loop gain  $H\beta$ . Estimate the dominant pole frequency and the first non-dominant pole frequency.

Because of the virtual ground,  
 we only need the transconductance  
 of the first stage, and the  
 output resistance.

$$\Rightarrow Z_{\text{up}} \approx R_{\text{th}, d_4} \times Z_{\text{down}} \approx R_{\text{th}, d_6}$$

$$\Rightarrow R_{\text{th}, d_4} = r_{o_4} \left( 1 + g_m r_{o_2} \right) + r_{o_2} \\ \approx g_m r_{o_2} r_{o_4}$$

$$\Rightarrow R_{\text{th}, d_6} = r_{o_6} \left( 1 + \frac{g_m 6}{g_m 8} \right) + \frac{1}{g_m 8} \\ \approx 2 r_{o_6}$$

$$\Rightarrow R_{\text{out}} = 2 r_{o_6} // g_m r_{o_2} r_{o_4}$$

$$\Rightarrow A_{V_1} = - \frac{g_{m_2}^0}{2} \left( r_{06} \parallel g_{m_y} r_{02} r_{04} \right)$$

$$\Rightarrow A_{V_1} = - g_{m_2} \left( r_{06} \parallel g_{m_y} r_{02} r_{04} \right)$$

$$\Leftarrow - g_{m_2} r_{06}$$

$$\Rightarrow A_{V_2} = - g_{m_g} r_{0g}$$

$$B^0(s) = \frac{g_{m_2} g_{m_g} r_{06} r_{0g}}{2}$$

The dominant pole is  $C_L$ .

The first non-dominant pole  
is  $C_{gsq}$ .


$$\Rightarrow Z_{C_L} = R_{th, dg} \approx r_{oq}$$

$$W_{P_1} \approx \frac{1}{r_{oq} C_L}$$


$$W_{P_2} \approx \frac{1}{2r_{oq} // g_{m_y} r_{o2} r_{o4} \cdot C_{gsq}}$$

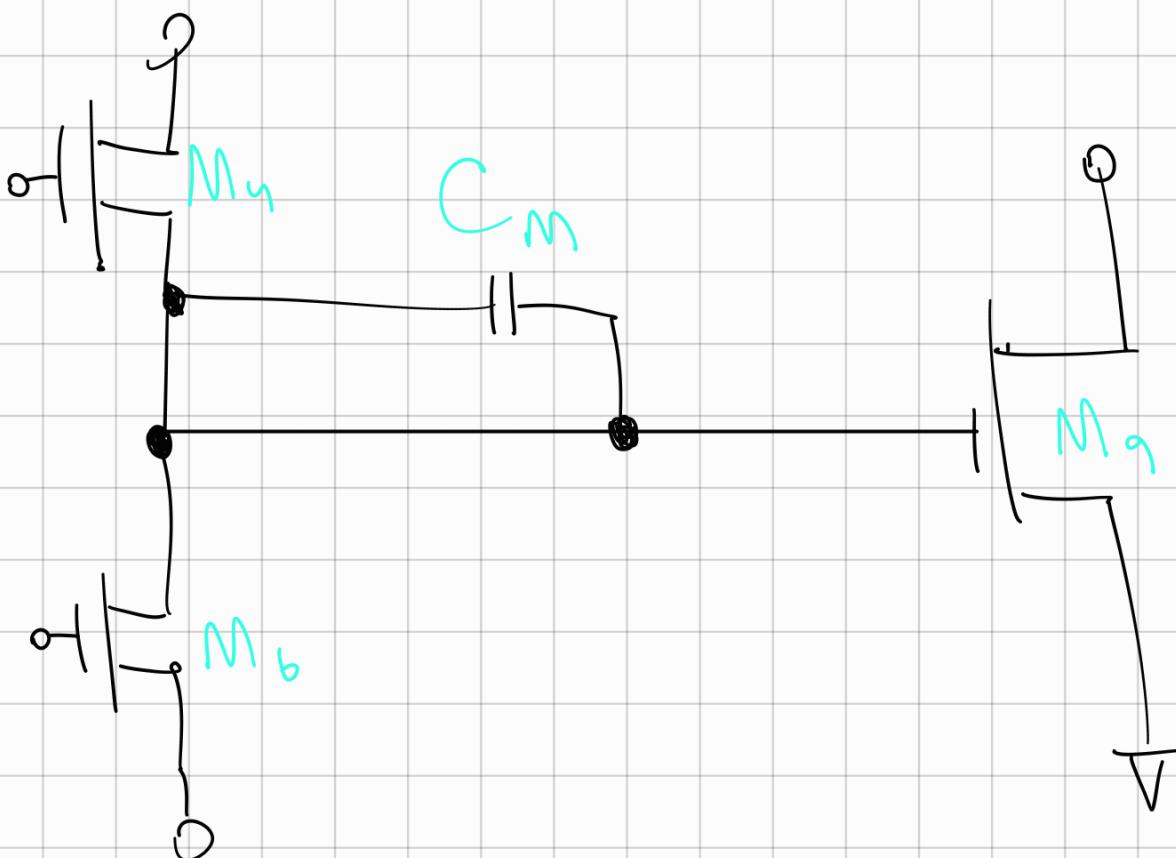(b) To Miller compensate this amplifier, where would you add a capacitor?

We would split the poles between the output of the differential stage and the input stage of the common source stage.



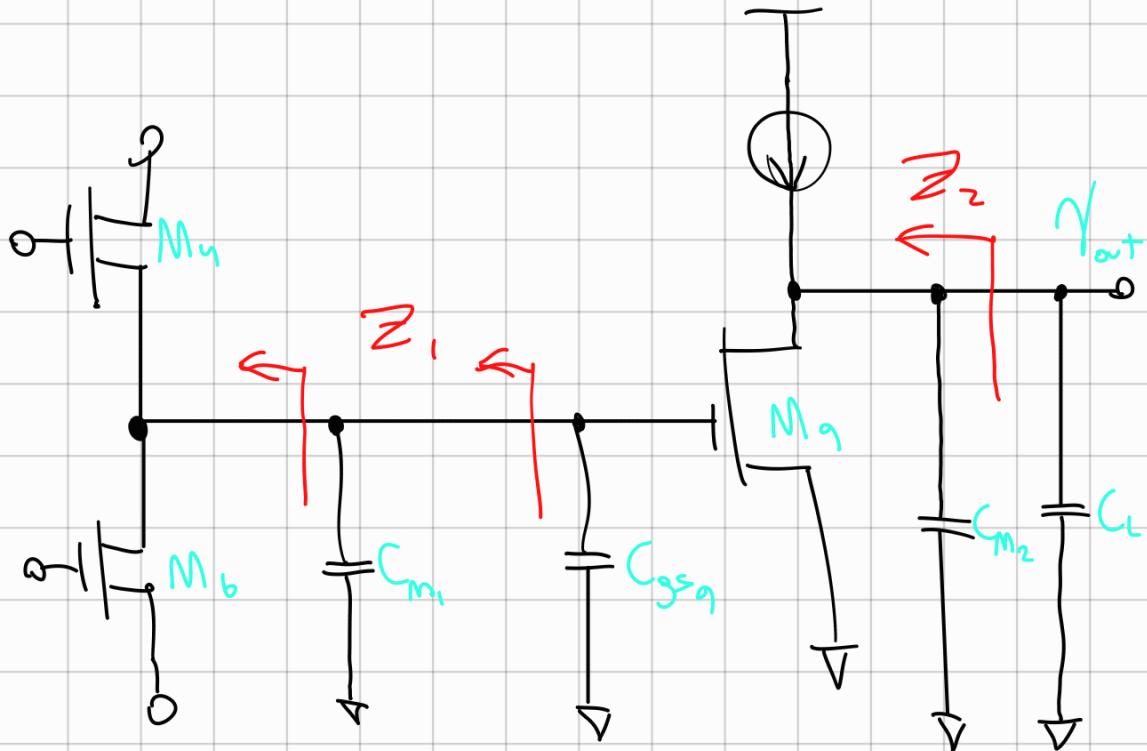- (c) Considering the capacitor you added, estimate the locations of the new dominant pole, first non-dominant pole, and the zero. Assume the dominant pole results from the added compensation capacitor.



$$Z_1 \approx 2r_{o_1}$$

$$Z_2 \approx r_{o_2}$$

$$\Rightarrow C_{m_1} = C_m \left( 1 - (-g_{m_1}r_{o_1}) \right)$$

$$= C_m \left( 1 + g_{m_1}r_{o_1} \right)$$

$$\Rightarrow C_{m_2} = C_m \left( 1 - \left( \frac{1}{-g_{m_2}r_{o_2}} \right) \right)$$

$$= C_m \left( 1 + \frac{1}{g_{m_2}r_{o_2}} \right) \approx C_m$$

$$W_{P_1} = \frac{-1}{Z_1(C_m + C_{gs})}$$

$$= \frac{-1}{2r_{o_6}(C_m + C_{gs})}$$

$$W_{P_2} = \frac{-1}{Z_2(C_{m_2} + C_L)}$$

$$= \frac{-1}{r_{o_9}(C_{m_2} + C_L)}$$


\*  $C_{m_1} \gg C_{m_2}$

• New Dominant Pole =  $W_{P_1}$

• • First Non-Dominant Pole =  $W_{P_2}$

$$Z_{ero} \equiv \frac{g_m g}{C_m}$$

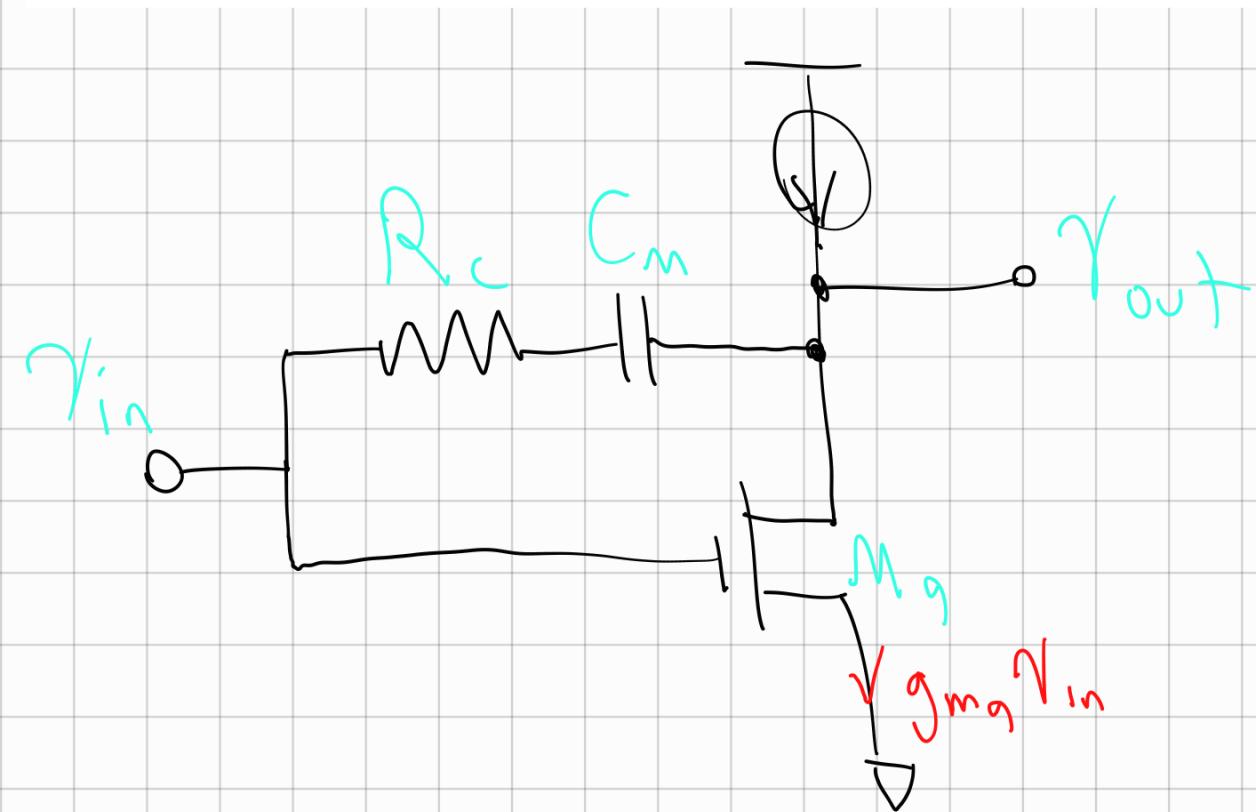- (d) To move the RHP zero to infinity, we could add a resistor in series with the capacitor. What would its value be?



KCL

$$g_{m9} \cdot V_{in} = \frac{V_{out} - V_{in}}{Z_C + Z_m}$$

$$= \frac{V_{out} - V_{in}}{R_C + \frac{1}{sC_m}}$$

$$\Rightarrow V_{out} = V_{in} \left( 1 - g_{m9} \left( R_C + \frac{1}{sC_m} \right) \right)$$

$$\Rightarrow \frac{\gamma_{\text{out}}}{\gamma_{\text{in}}} = \frac{sC_m - g_{mg}(1 + sR_c C_m)}{sC_m}$$

$\Rightarrow$  Want  $g_{mg} - sR_c C_m g_{mg} = g_{mg}$

$$\Rightarrow \text{Set } R_c = \frac{1}{g_{mg}}$$

$$\Rightarrow sC_m - g_{mg} R_c C_m s - g_{mg}$$

$$\Rightarrow sC_m - g_{mg} \frac{1}{g_{mg}} C_m s - g_{mg}$$

$$= sC_m - 1 \cdot sC_m s - g_{mg}$$

$\Rightarrow$  Zero cancels / moves  $\rightarrow \infty$

?	?
---	---

$$R_c = \frac{1}{g_{mg}}$$

- (e) Your colleague suggests that you can actually fine tune the value of the resistor to cancel your non-dominant pole to extend your bandwidth and improve your stability! What would be the value of the resistor in this case?

With the resistor, the zero becomes:

$$W_z = \left( \frac{g_{m9}}{C_m} \right) \left( \frac{1}{1 - g_{m9} R_C} \right)$$

$\Rightarrow$  Set equal to non-dominant pole  
and solve for  $R_C$ .

$$\frac{g_{m9}}{C_m(1 - g_{m9} R_C)} = \frac{-1}{r_{o9}(C_m + C_L)}$$

$$\begin{aligned} -C_m + C_m g_{m9} R_C &= g_{m9} r_{o9} (C_m + C_L) \\ &= g_{m9} r_{o9} C_m + g_{m9} r_{o9} C_L \end{aligned}$$

$$\Rightarrow C_m g_{mg} R_L = C_m + g_{mg} r_0 g C_m + g_{mg} r_0 g C_L$$

$$= C_m \left( 1 + g_{mg} r_0 g \right) + g_{mg} r_0 g C_L$$

$\therefore R_L = \frac{C_m \left( 1 + g_{mg} r_0 g \right) + g_{mg} r_0 g C_L}{C_m g_{mg}}$

# Problem 3 - Calculating Settling Errors

For this problem, you should use MATLAB/Python for all parts. No hand calculation is necessary. Provide your code alongside your solution.

*Hint: For Python, **control** package is your friend for this assignment. MATLAB has the **Control System Toolbox**. You can take the following Python code snippet as a starting point if you'll use Python:*

```
1 import control
2 import numpy as np
3 s = control.TransferFunction.s
4 wp1 = 2*np.pi*10e6
5 A0 = 1e4
6 t = np.linspace(0, 100e-12 , num =5000)
7 AOL = A0 / (1 + s/wp1)
8 ACL = AOL / (1+ AOL )
9 t, y = control.step_response(ACL , t)
```

- (a) Assume an amplifier has an open loop response containing a single pole at 10MHz and a DC gain of  $10^4$ . The amplifier is placed in unity gain feedback ( $\beta = 1$ ). Plot the step response of the closed loop system. Then create a plot of settling error (log scale) vs time, and find the times needed to settle to within 10%, 1%, and 0.1% of the final value.

$$V_o(t) = V \left( 1 - e^{-t/\tau} \right)$$

$$\Rightarrow |Error| = \left| e^{-t/\tau} \right|$$

$$\text{Error \%} = e^{-t/v} \times 100 \%$$

$$\text{Set } t = 7 \rightarrow E = e^{-1} \times 100\% = 36.7\% \text{ cm}$$

$$t = 5^\circ C \rightarrow E = e^{-5} \times 100\% = 0.7\% \text{ cm}$$

For every 10x  $\Rightarrow 2.3^\circ C$



- (b) Repeat the previous part using the same amplifier, except now with a DC gain of 999.



- (c) Compare the settling times from part (a) with those from part (b). Did they change significantly? If so, explain why.

$$1 \cdot W_{nny} = A \cdot W_{3dB}$$

$$\begin{aligned} W_0 &= 10k \cdot 2\pi \cdot 10^6 \\ &= 6.28 \times 10^{10} \text{ Hz} \\ &\approx 63 \text{ GHz} \end{aligned}$$

$$\log W_0 = 180^\circ$$

$$1 + \frac{s}{W_p} + A_0 = 0$$

Find the BW by setting  $C_c$  pole to 0.  $\Rightarrow$  Find break point,

$$s = W_p \cdot - (A_0 + 1)$$




$$W_{C_c} = W_p \cdot - (A_0 + 1)$$


- (d) Now use the amplifier from part (a), except that the amplifier now has a second pole. Plot the closed loop step responses if the second pole is chosen to give  $30^\circ$ ,  $45^\circ$ ,  $60^\circ$ ,  $80^\circ$  of phase margin.



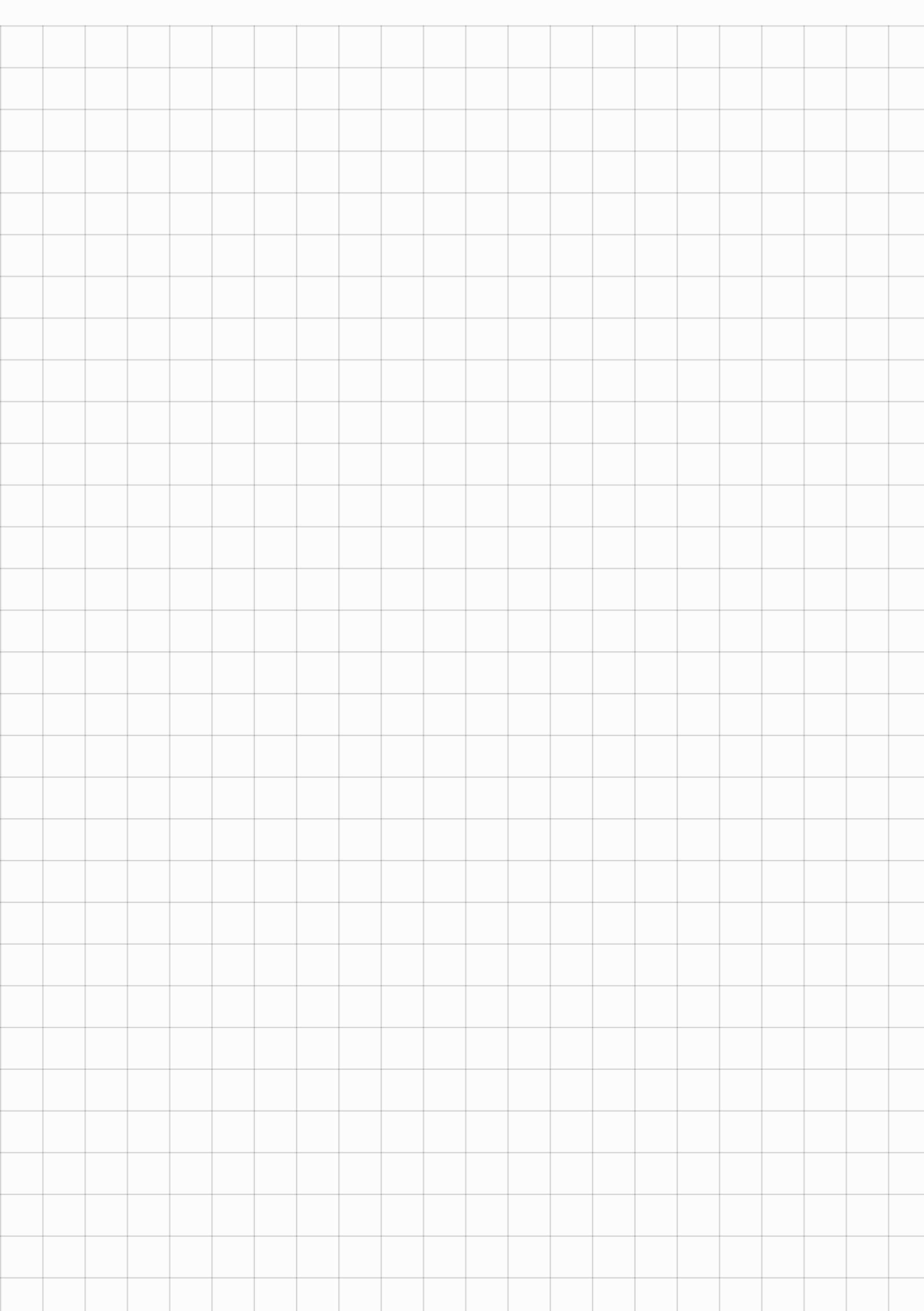- (e) Using the same amplifier as the previous part, find the phase margin that gives the best settling time if your settling error margin is 10%. Repeat for 1% and 0.1%. Comment on your results. In particular, focus on the shape of the optimal step response as settling error margin decreases.





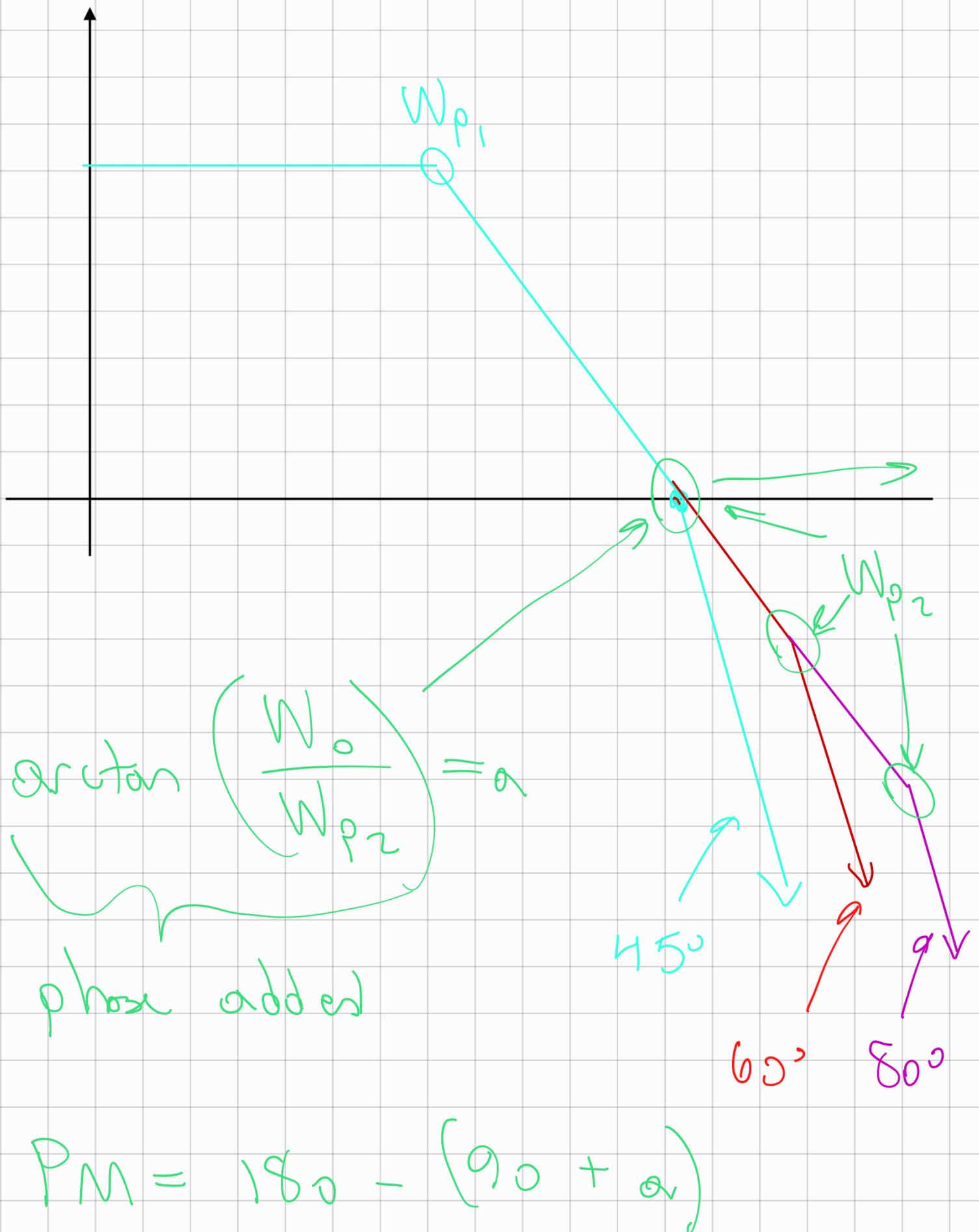

\*  $B \cdot H(s) \uparrow \Rightarrow$  static error ↓

